



Daniel DZAHINI

LPSC => TIMA / Xdigit  
ATLAS / ILC etc..

[dzahini@univ-grenoble-alpes.fr](mailto:dzahini@univ-grenoble-alpes.fr)

Xdigit is a start-up for specific ADC design

Mainly for sensors' array like pixels

[www.xdigit.fr](http://www.xdigit.fr)

OVERVIEW FOR SIGNAL READOUT  
FOR CAPACITIVE DETECTOR PULSE  
PROCESSING

THANKS to many who provide slides and other documents online that I use for this lecturer

- Angelo Rivetti: *Front end electronics for radiation sensors*
- *Emilio Gatti & Manfredi (INFN)*
- Yan Kaplon (CERN)
- Christophe de la Taille (Omega lab)
- Glenn F. Knoll: *Radiation detection & measurement*
- Chiara Guazzoni; <http://home.dei.polimi.it/guazzoni>



# What signal processing means?



**Sculpturing!**  
**Designing?**



**signal**  
**processing**

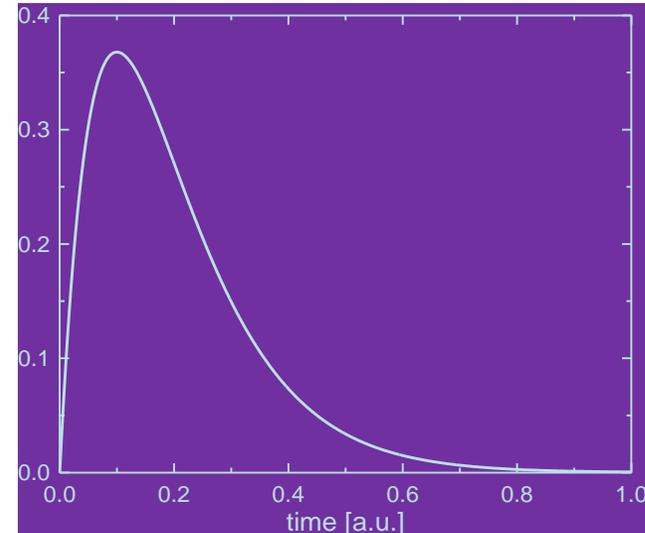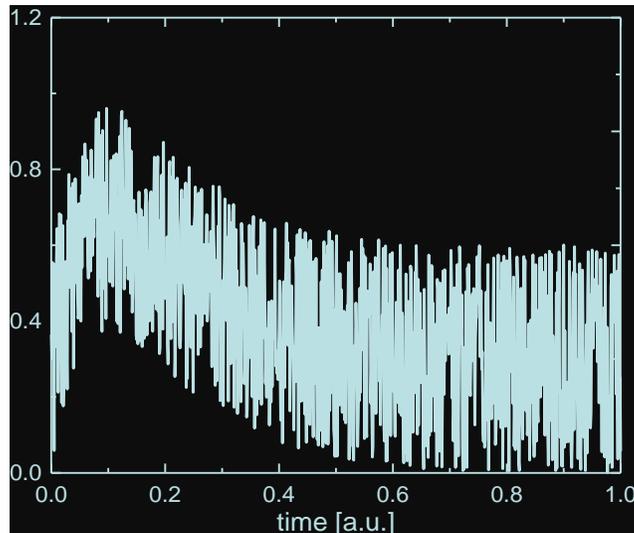

How noisy are flowers in your garden





www.shutterstock.com · 82175482


**If plants can grow  
without ?? noise,**

**Why can't I amplify  
without adding noise**

# Actual system is unfortunately noisy

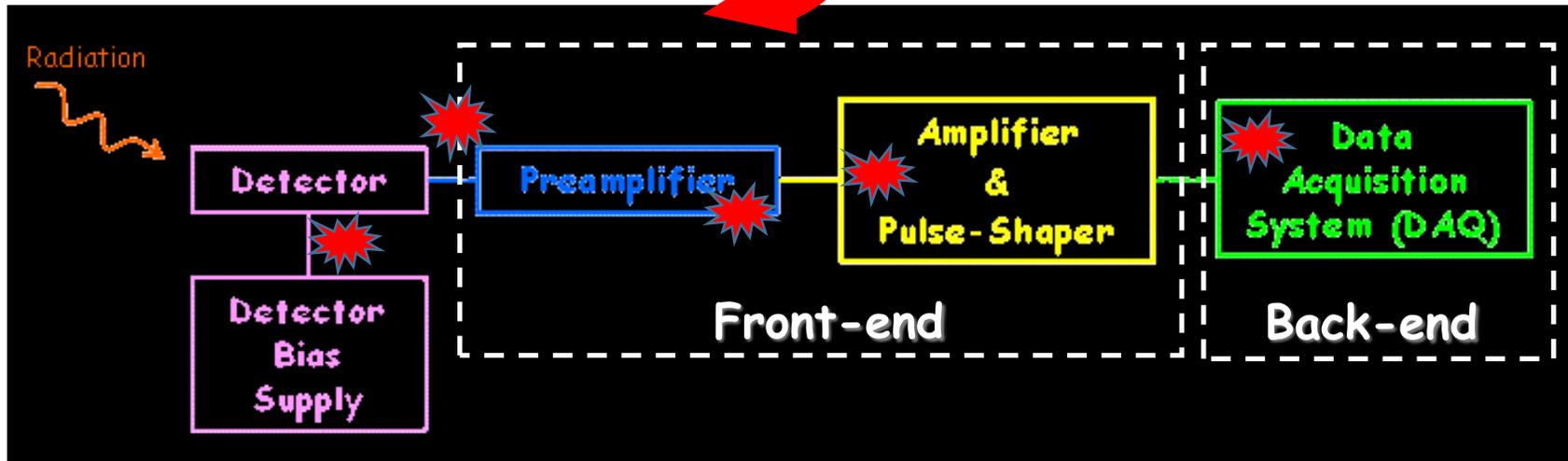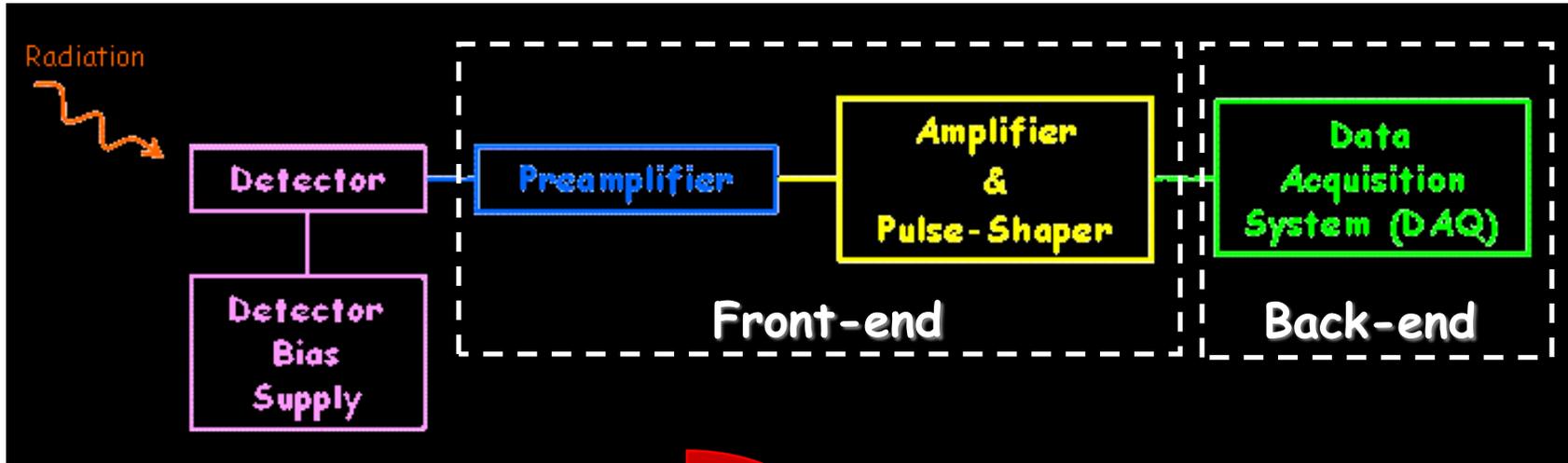
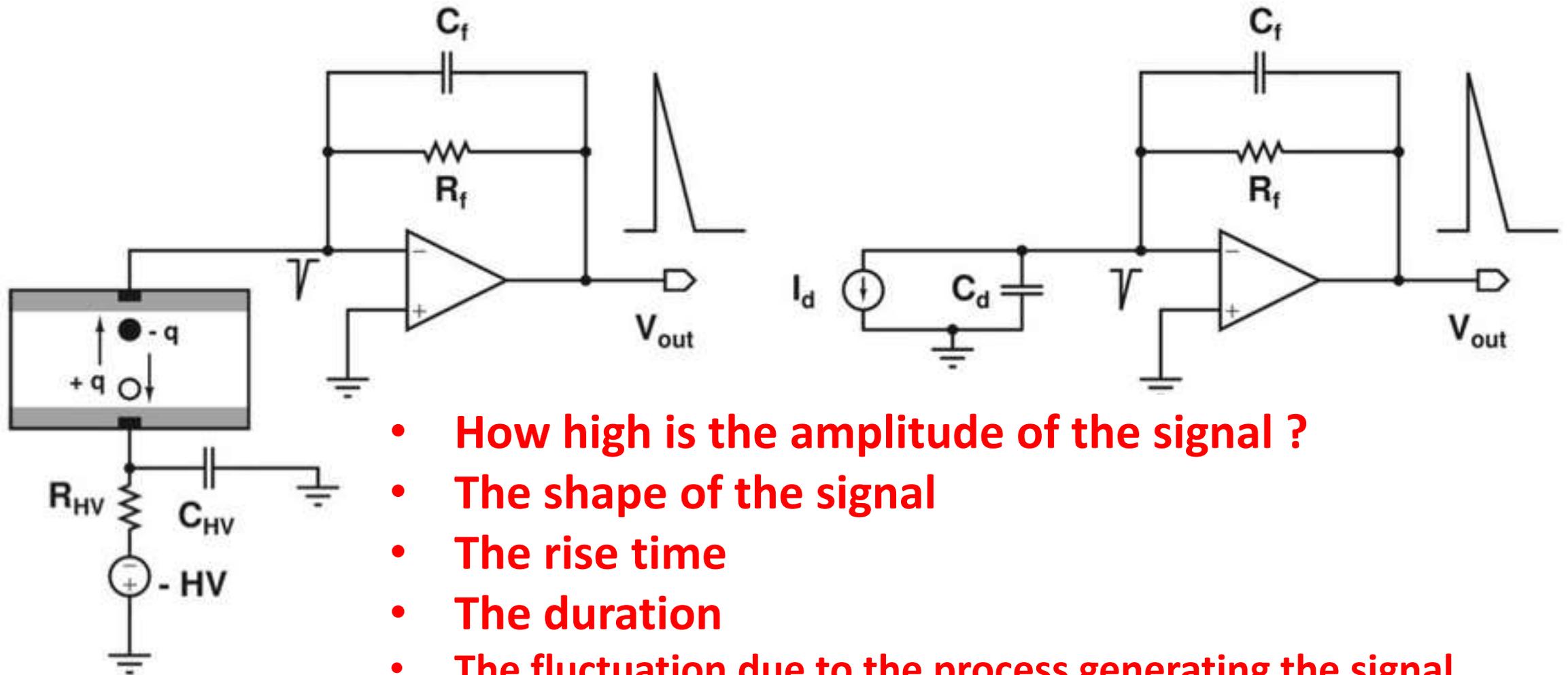
# Signal polarity with negative High voltage



- How high is the amplitude of the signal ?
- The shape of the signal
- The rise time
- The duration
- The fluctuation due to the process generating the signal

# Detector signal duration: how short?

The signal generally is a **short** current pulse

- thin silicon detector (10 –300  $\mu\text{m}$ ): 100 ps–30 ns
- thick ( $\sim\text{cm}$ ) Si or Ge detector: 1 –10  $\mu\text{s}$
- proportional chamber: 10 ns –10  $\mu\text{s}$
- Microstrip Gas Chamber: 10 –50 ns
- Scintillator+ PMT/APD: 100 ps–10  $\mu\text{s}$


$$\mathbf{Energy} \sim \int \mathbf{i}(t) dt$$

# What Information can one extract from a pulse?

Various measurements of this signal are possible

Depending on information required:

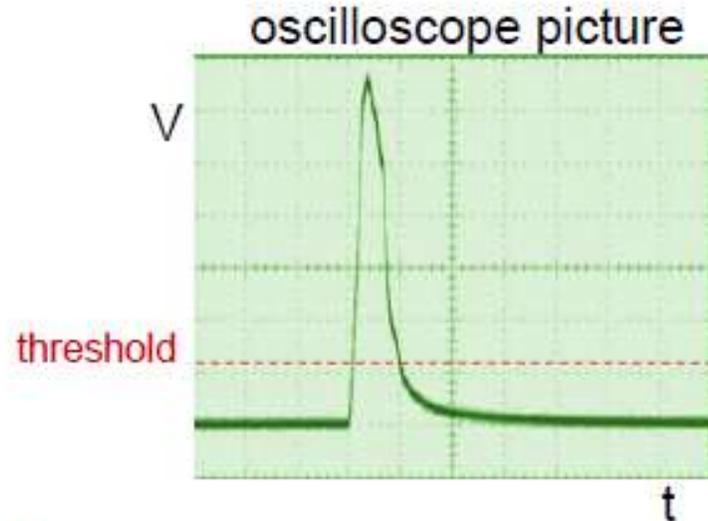- Signal above threshold  
digital response / event count
- Integral of current = charge  
→ energy deposited
- Time of leading edge  
→ time of arrival (ToA) or time of flight (ToF)
- Time of signal above threshold  
→ energy deposited by TOT





and many more ...
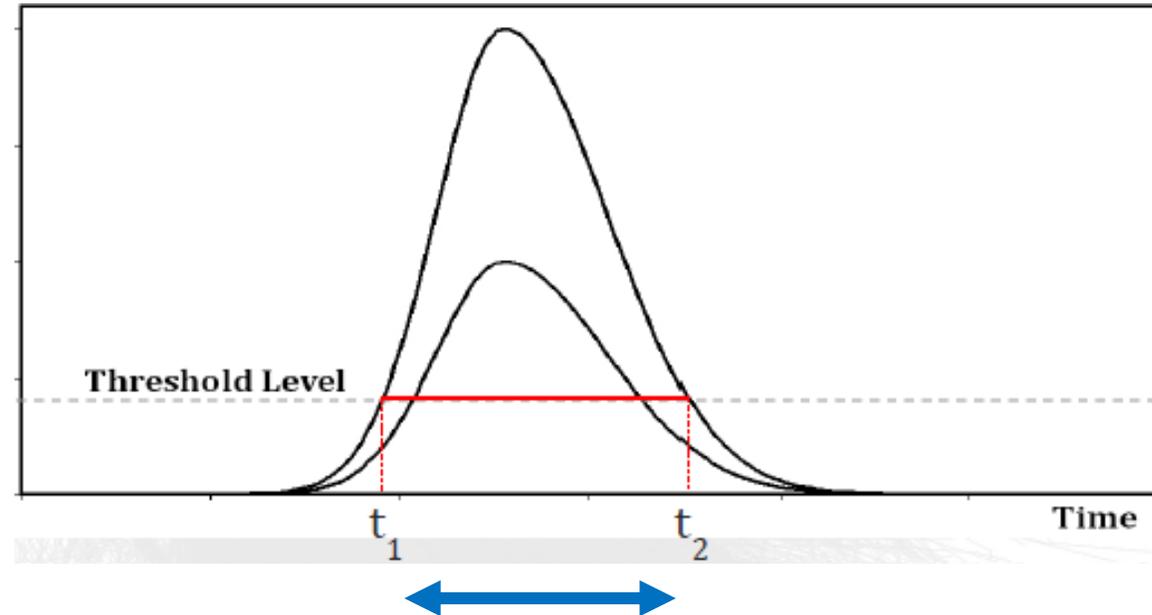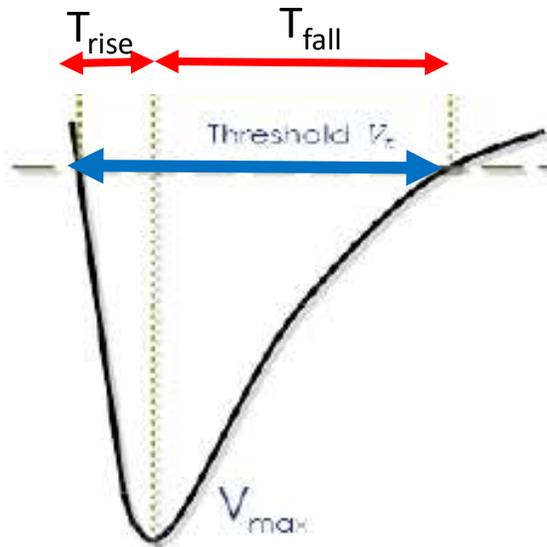
# Counting and time over threshold

For **digital imaging** a counter is used after the comparator  
Then one proceed by counting the number of events in a frame rate.

**The comparator system** could be used also to quatify the amplitude of an incoming signal.  
The time spent over threshold by the amplifier output is somehow proportional to the amplitude of the incoming signal: TOT





# Parameter impacting the pulse **amplitude**:

**E<sub>i</sub>** = Minimum **ionization** energy (depends on the detector cristal, gaz, or liquide)

**E<sub>p</sub>** (> E<sub>i</sub>): *average* energy to generate a charges **pair**

**E** : Energy lost by an incoming particle =>

**N<sub>p</sub>**: *Average Number* of generated **Pairs**

**N<sub>p</sub> = E/E<sub>p</sub>** => an *average* number

But instantly, the number follows a probabilistic law with a fluctuation from one event to another displaying a standard

deviation  $\sigma_{N_p} = \sqrt{F * N_p}$  ; F is the Fano factor

In many material  $F < 1$  then  $\sigma_{N_p}$  is better than one could expect from the Poisson statistics ( $\sqrt{N_p}$  );


# Detector's equivalent circuit: $C_D$ and $I_L$

Detector = capacitance  $C_D$

- Pixels : 0.1-10 pF
- PMs : 3-30 pF
- Ionization chambers: 10-1000 pF
- Sometimes effect of transmission line

Signal : current source

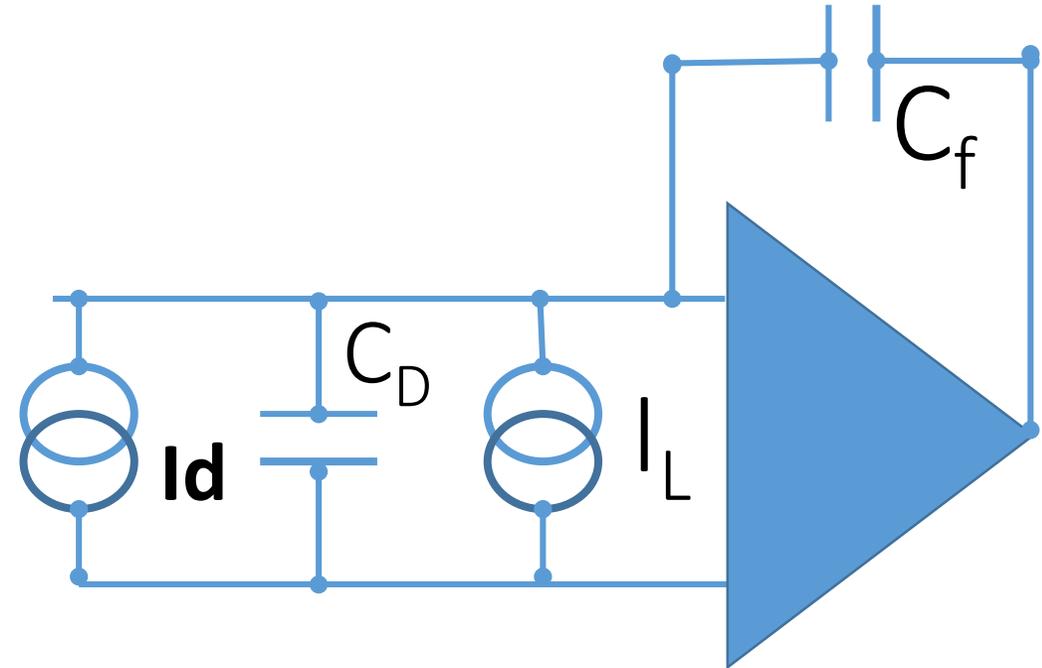- Pixels :  $\sim 100 e^-/\mu m$
- PMs : 1 photoelectron  $\rightarrow 10^5-10^7 e^-$
- Modeled as an impulse (Dirac) :  
 $i(t) = Q_0 \delta(t)$



- $C_D$  impact on **speed** and **noise** figures
- $I_L$  impact output **DC level**, and on **noise**

# Charge sensitive preamplifier

Active Integrator (“charge-sensitive amplifier”)

Start with inverting voltage amplifier

Voltage gain  $dv_o/dv_i = -A \Rightarrow v_o = -Av_i$

Input impedance =  $\infty$   
(no signal current flows into amplifier input)

Connect feedback capacitor  $C_f$  between output and input.


Voltage difference across  $C_f$ :

$\Rightarrow$  Charge deposited on  $C_f$ :

$\Rightarrow$  Effective input capacitance  $C_i = \frac{Q_i}{v_i} = C_f(A+1)$  (“dynamic” input capacitance)

Gain  $A_Q = \frac{dV_o}{dQ_i} = \frac{A \cdot v_i}{C_i \cdot v_i} = \frac{A}{C_i} = \frac{A}{A+1} \cdot \frac{1}{C_f} \approx \frac{1}{C_f} \quad (A \gg 1)$

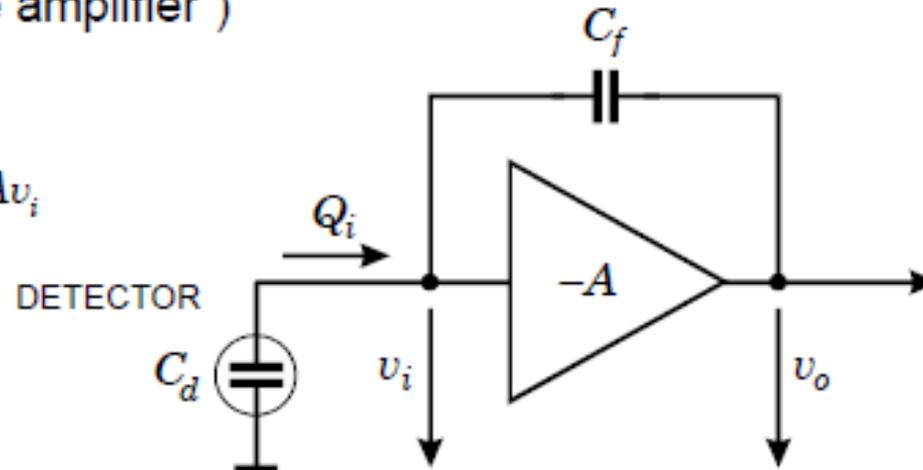Set by a well-controlled quantity, the feedback capacitance.



$$\text{so } v_o - v_i = -Av_i - v_i = -(A+1)v_i = -v_f$$

$$v_f = (A+1)v_i$$

$$Q_f = C_f v_f = C_f(A+1)v_i$$

$$Q_i = Q_f \quad (\text{since } Z_i = \infty)$$

# Charge preamplifier: exemple of typical values

So finally the fraction of charge signal measured by the amplifier is:

$$\frac{Q_i}{Q_s} = \frac{C_i v_i}{v_i (C_i + C_{det})} = \frac{1}{1 + C_{det} / C_i} \quad C_f \approx \frac{A}{C_i} \quad (A \gg 1)$$

Example:

$$A = 10^3$$

$$C_f = 1 \text{ pF}$$



$$C_i = 1 \text{ nF}$$

$$C_{det} = 10 \text{ pF}$$



$$Q_i/Q_s = 0.99$$

$$(C_i \gg C_{det})$$

$$C_{det} = 500 \text{ pF}$$




$$Q_i/Q_s = 0.67$$


$$(C_i \sim C_{det})$$

$\uparrow$   
Si det: 50um thick, 500mm<sup>2</sup> area


# Front end amplifier and shaper circuit

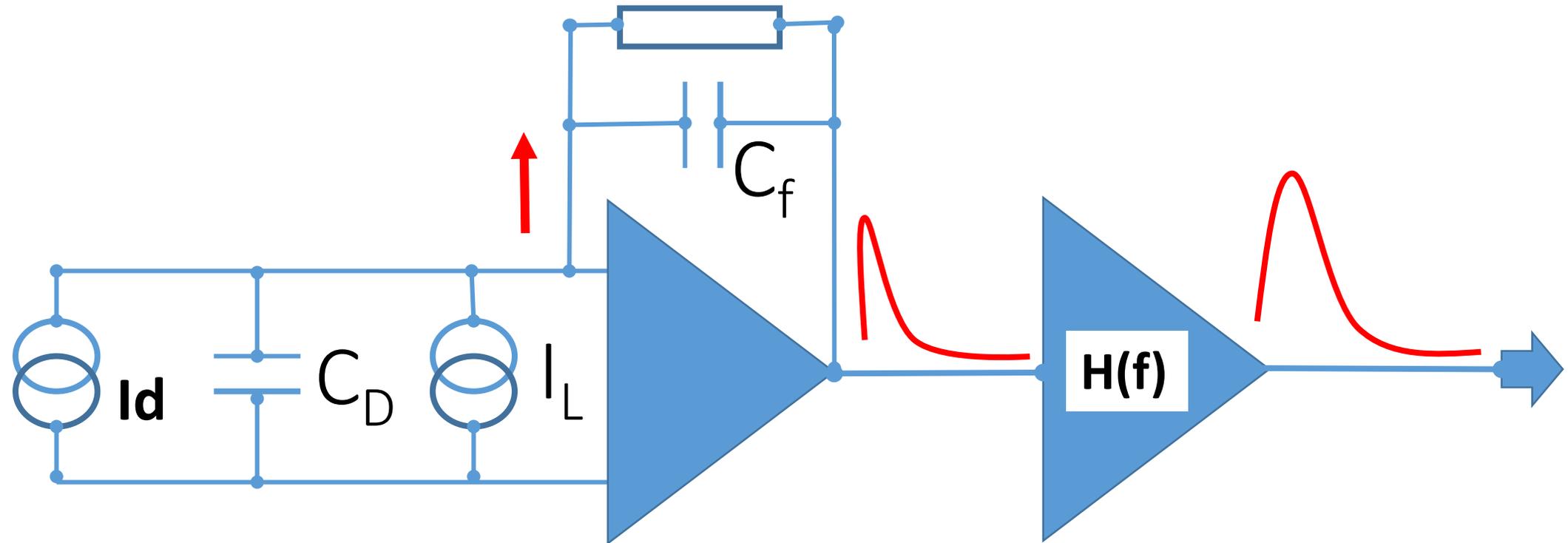

# Noise and Front end amplifiers

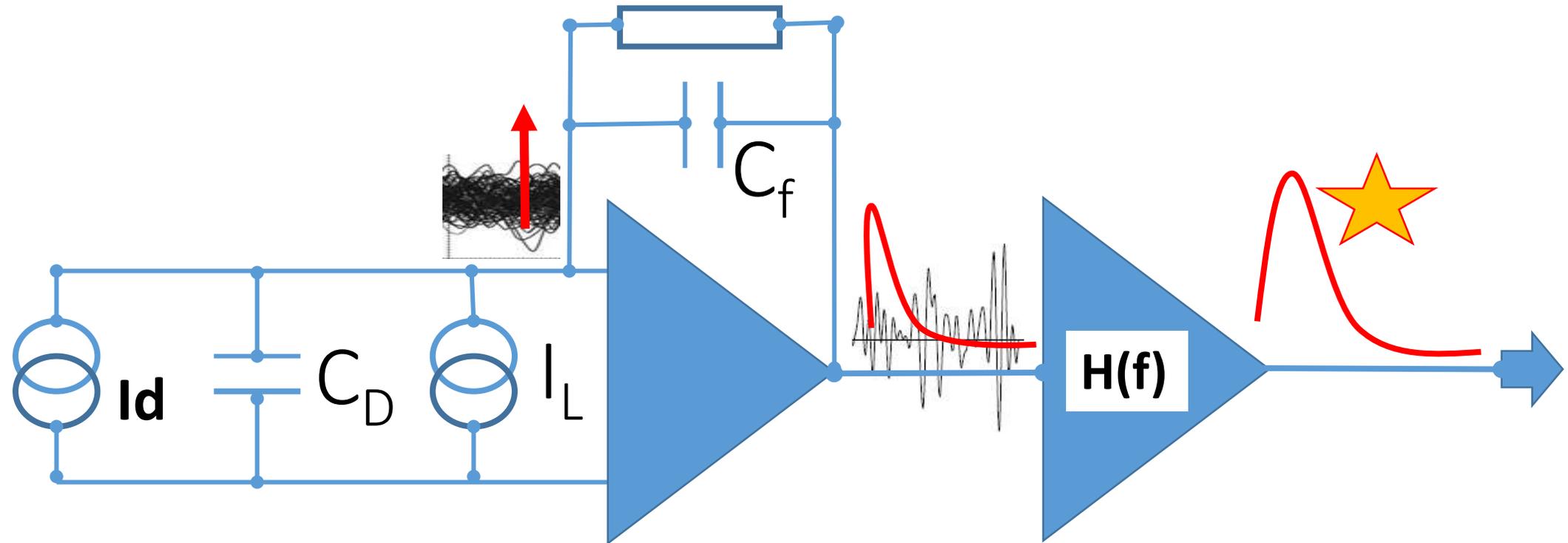


# Signal & noise bandwidth

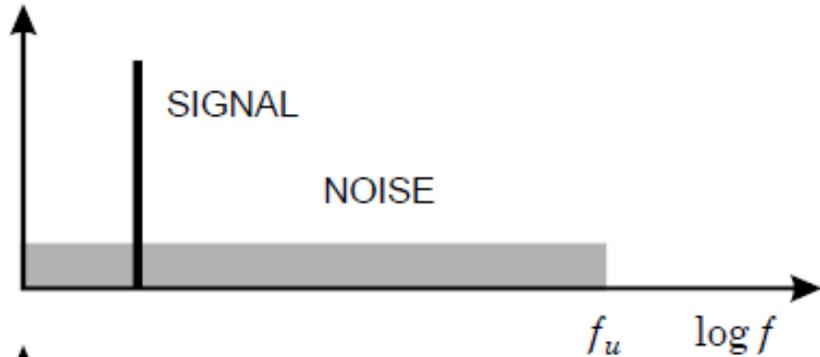


The total noise will be the integral over the bandwidth

Then Signal/Noise could be improved by  
« optimizing » the noise bande close to the signal's.



# Different options of reset systems

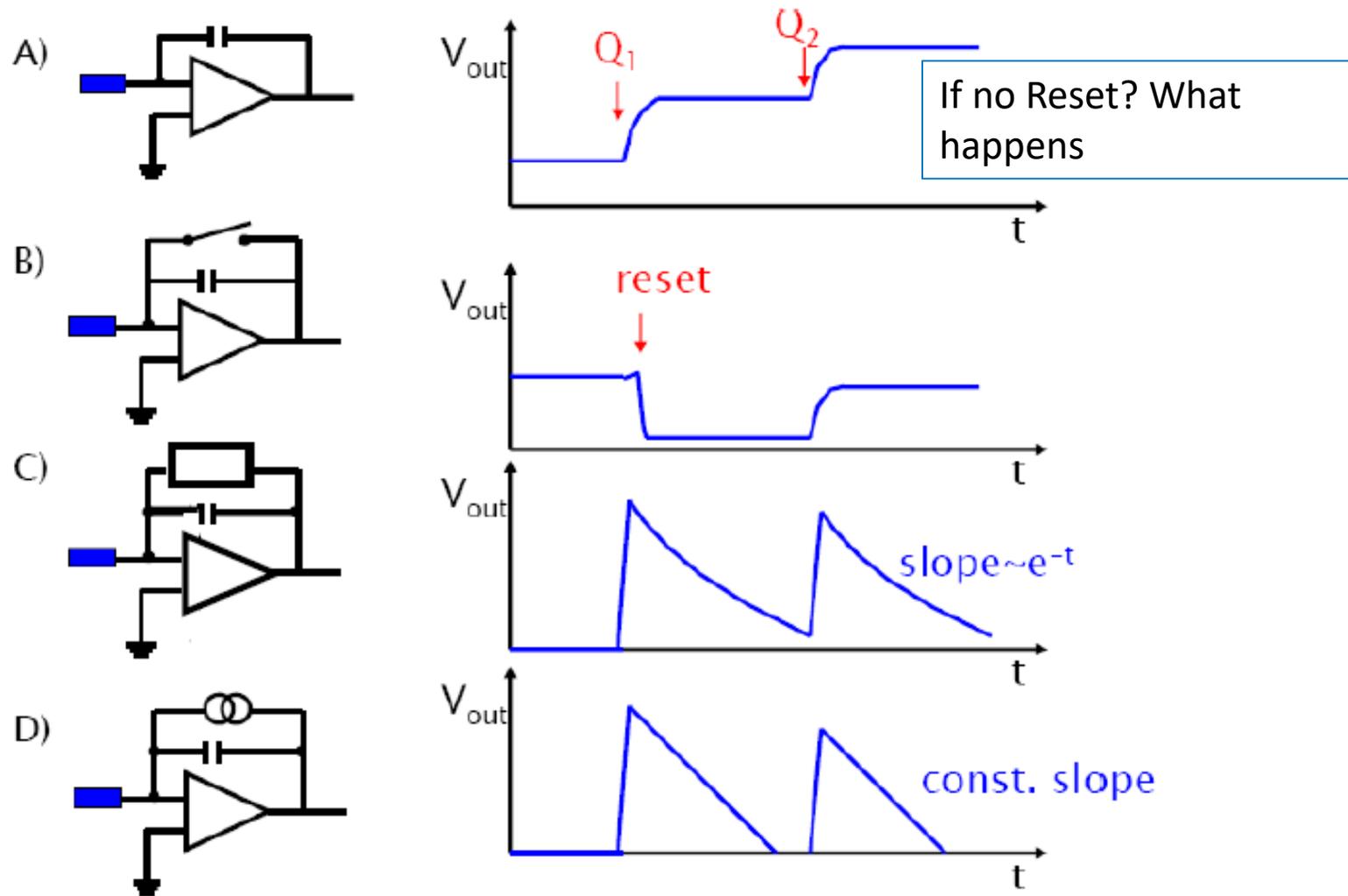

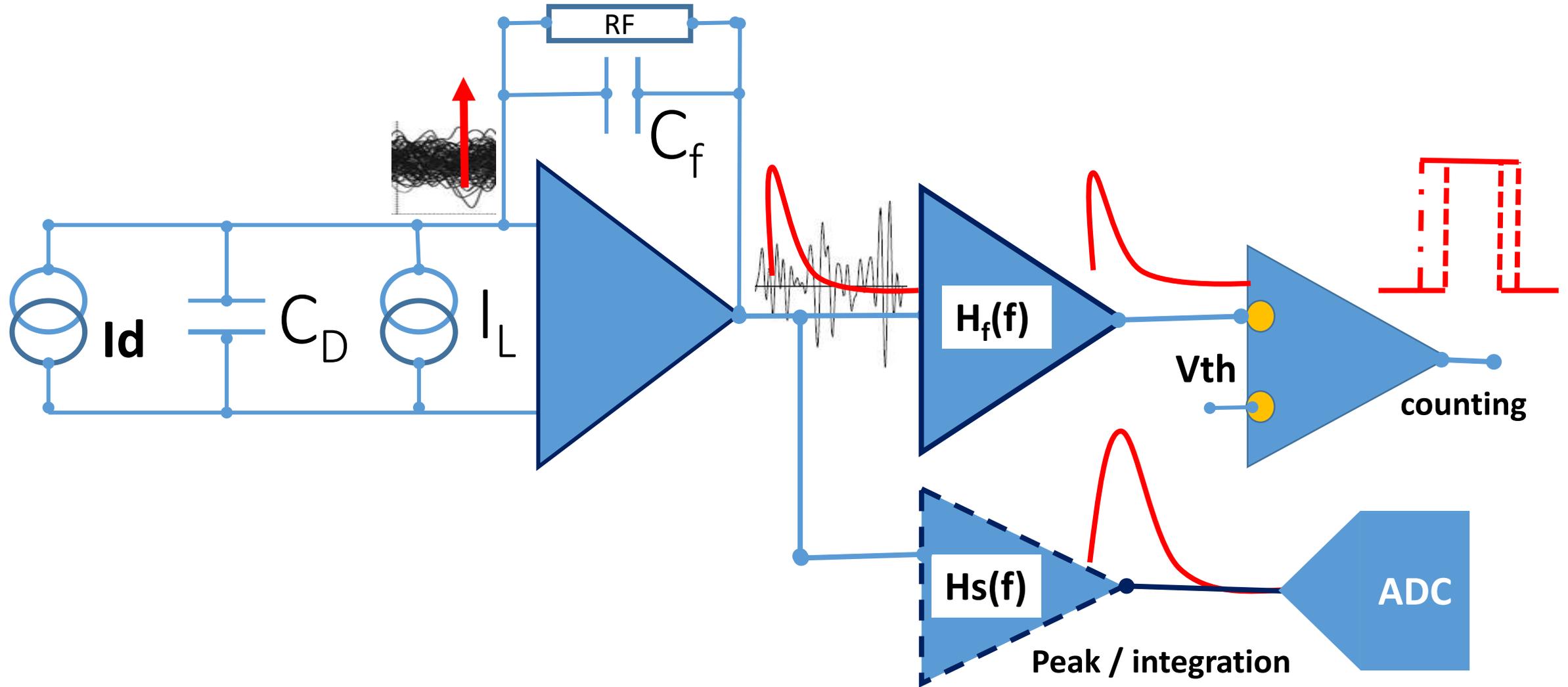
# Noise and Front end amplifiers and comparators



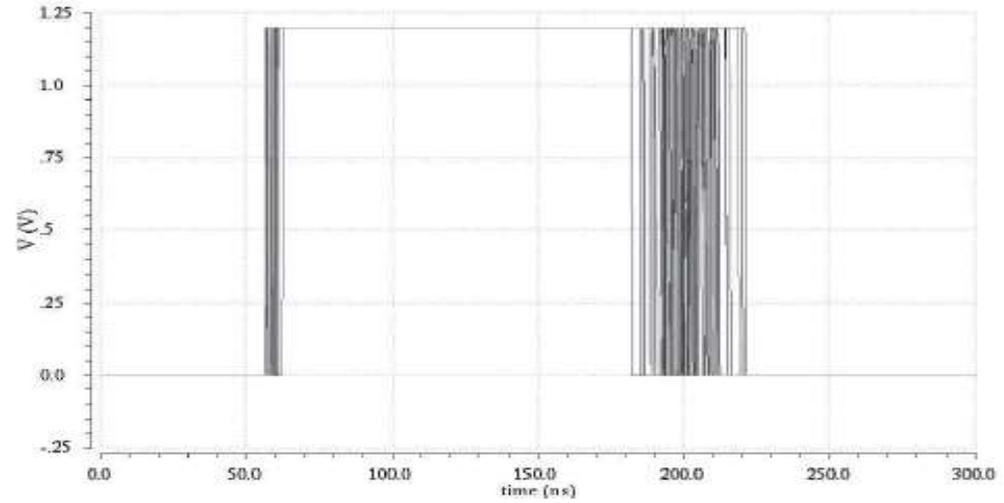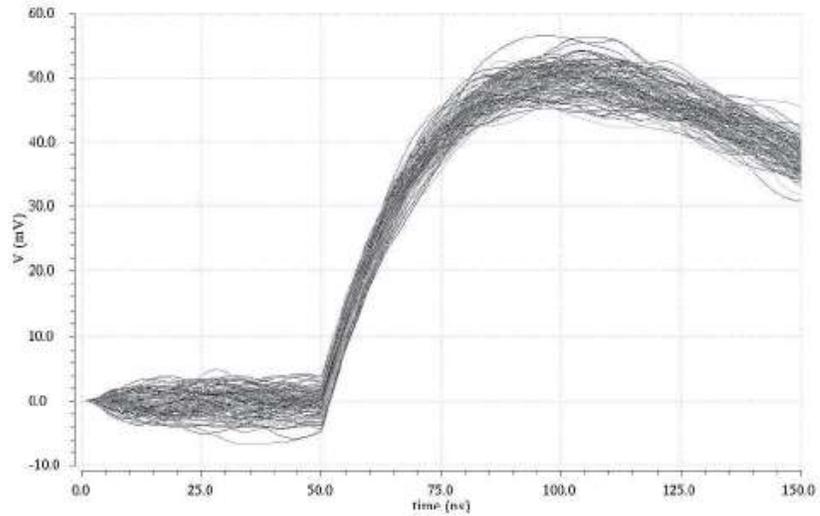Even for counting, beware of the noise: why using a shorter peaking time for counting readout?




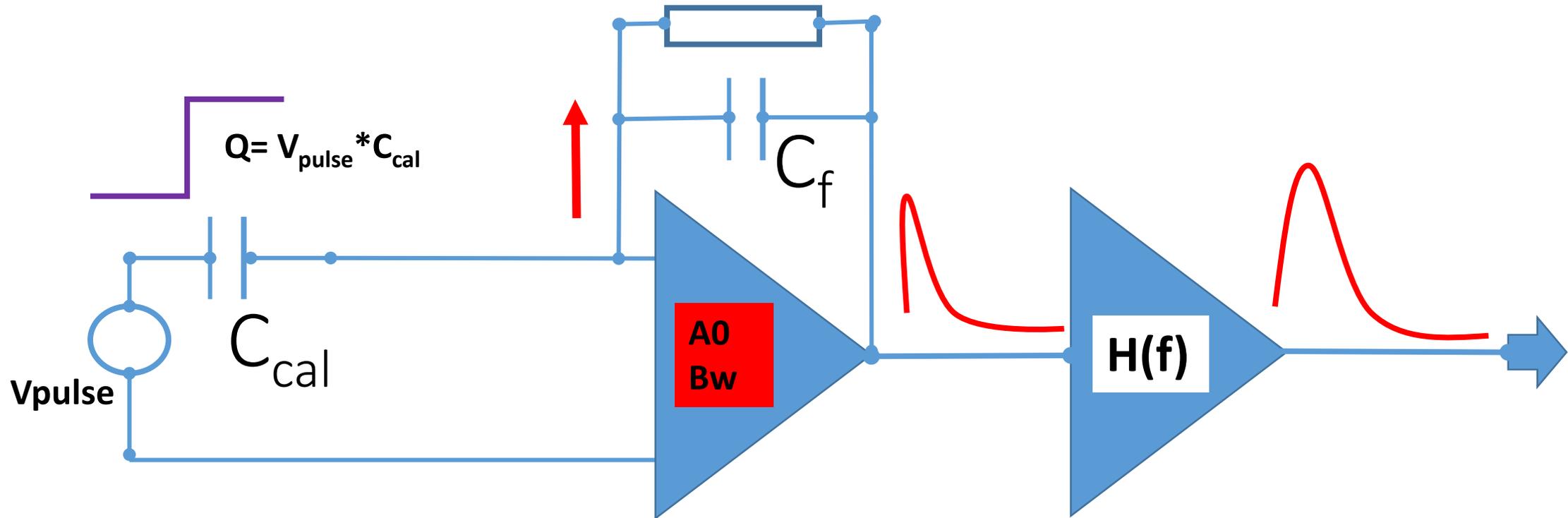
# Calibration and simulation of Front end amplifiers



Before been so happy that you find a noise very low!!,  
*make sure your circuit is still amplifying the signal*

# CR RC shapers (filters)

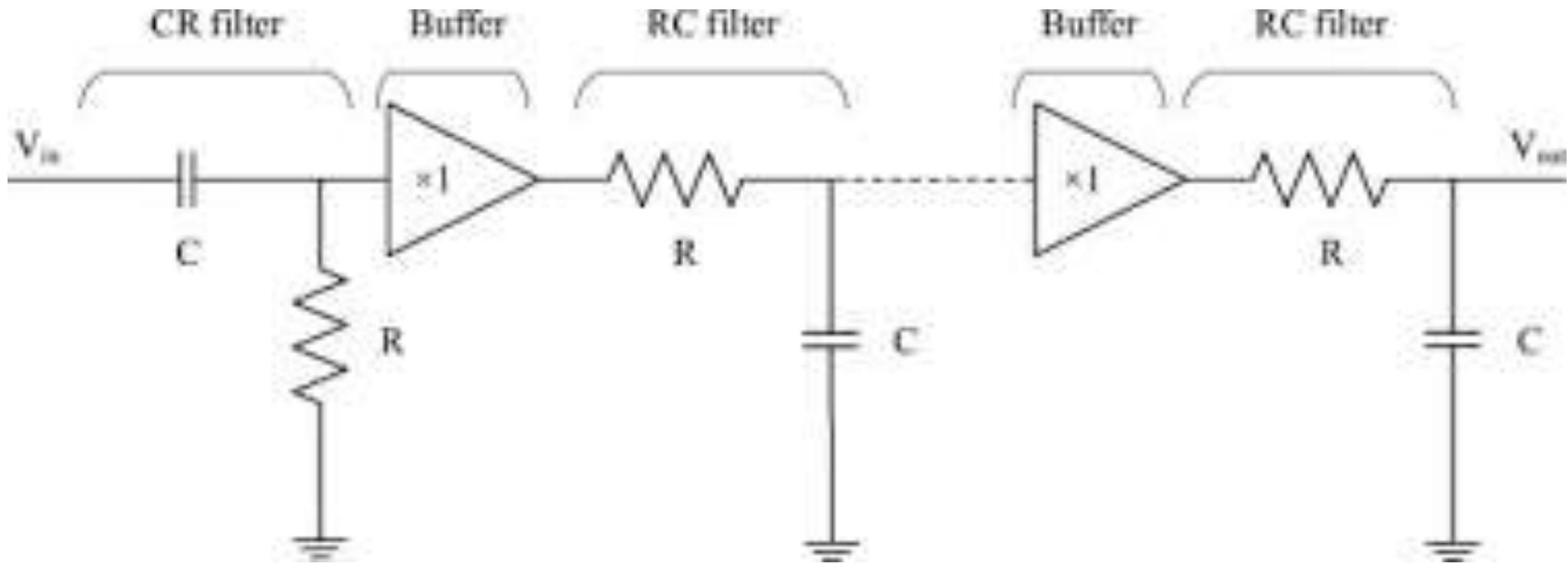

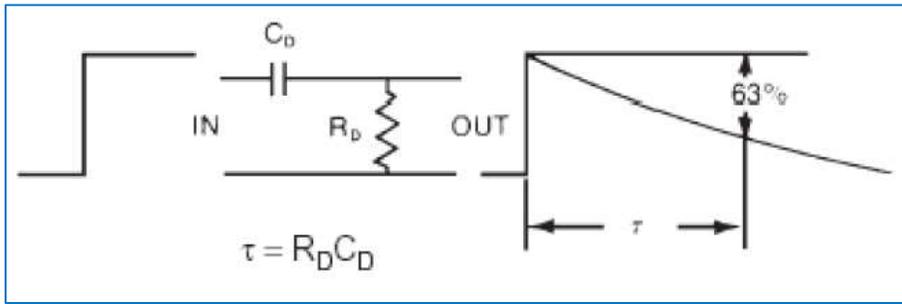

# CR Filter after the preamp

$$V_{in}(t) = \frac{Q(t)}{C} + V_{out}(t) \quad \Rightarrow \quad \frac{dV_{in}(t)}{dt} = \frac{i(t)}{C} + \frac{dV_{out}(t)}{dt}$$

by  $V_{out}(t) = i(t)R$  and  $\tau = RC$ ,  $\tau \frac{dV_{in}(t)}{dt} = V_{out}(t) + \tau \frac{dV_{out}(t)}{dt}$

Assuming the zero initial condition, taking Laplace transform leads to

$$V_{out}(s) = \frac{\tau s}{1 + \tau s} V_{in}(s) = G_{CR}(s) V_{in}(s)$$

For the step function input


$$V_{in}(t) = \begin{cases} V_0 & (t > 0) \\ 0 & (t \leq 0) \end{cases} \quad \Rightarrow \quad V_{in}(s) = L[V_{in}(t)] = \frac{V_0}{s}$$

the output signal becomes

$$V_{out}(s) = \frac{\tau}{1 + \tau s} V_0 \quad \Rightarrow \quad V_{out}(t) = V_0 e^{-t/\tau}$$

$$G_{CR}(i\omega) = \frac{i\omega\tau}{1 + i\omega\tau} \quad \Rightarrow \quad |G_{CR}(i\omega)| = \frac{\omega\tau}{\sqrt{1 + \omega^2\tau^2}}$$

# RC stage of the shaper

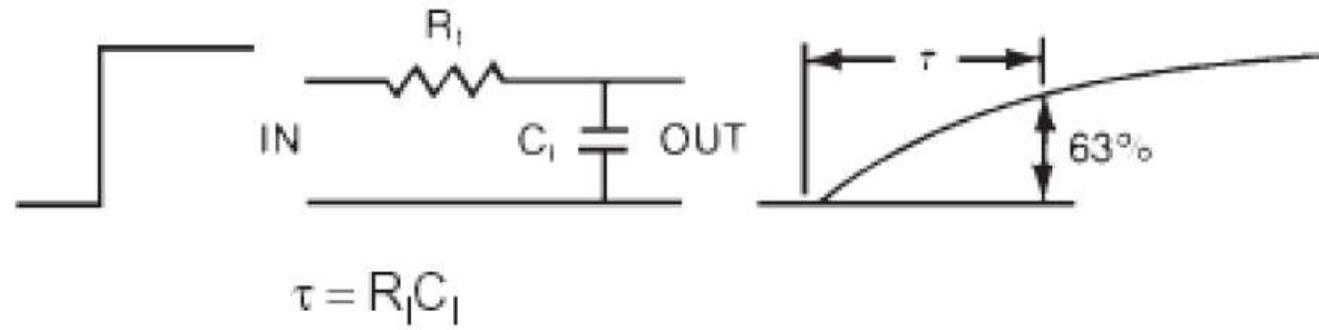

$$V_{in}(t) = i(t)R + V_{out}(t) \quad \text{and} \quad i(t) = \frac{dQ(t)}{dt} = C \frac{dV_{out}(t)}{dt}$$

$$\Rightarrow V_{in}(t) = \tau \frac{dV_{out}(t)}{dt} + V_{out}(t) \quad \Rightarrow \quad V_{out}(s) = \frac{1}{1 + \tau s} V_{in}(s) = G_{RC}(s) V_{in}(s)$$

Output signal for the step function input:


$$V_{out}(s) = \frac{1}{1 + \tau s} \frac{V_0}{s} \quad \Rightarrow \quad V_{out}(t) = V_0(1 - e^{-t/\tau})$$

Frequency domain transfer function:

$$G_{RC}(i\omega) = \frac{1}{1 + i\omega\tau} \quad \Rightarrow \quad |G_{RC}(i\omega)| = \frac{1}{\sqrt{1 + \omega^2\tau^2}}$$
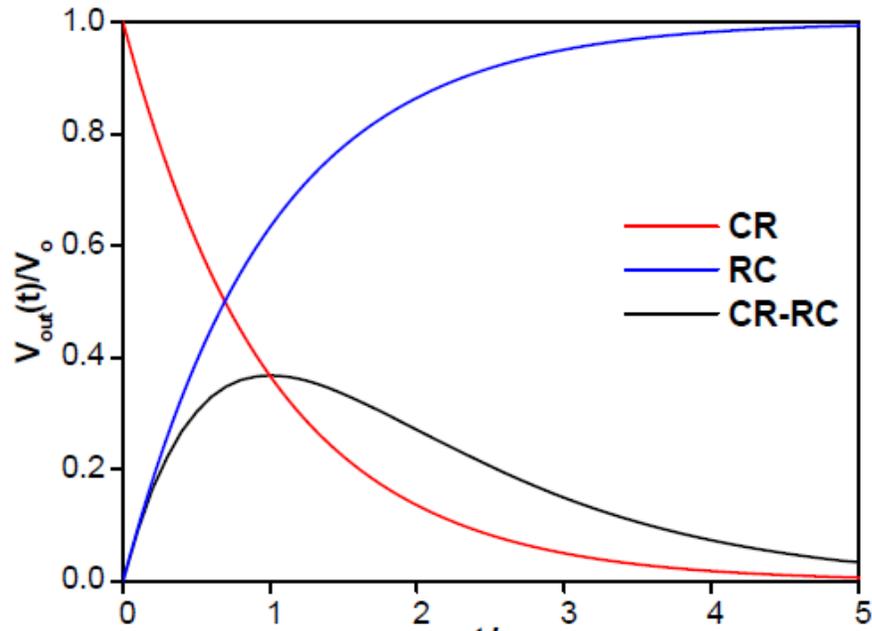
# CR+RC transfert functions for a step input


This step stand for the integrator output signal



time domaine

$$V_{out}(t) = \frac{V_0 \tau_1}{\tau_1 - \tau_2} (e^{-t/\tau_1} - e^{-t/\tau_2})$$

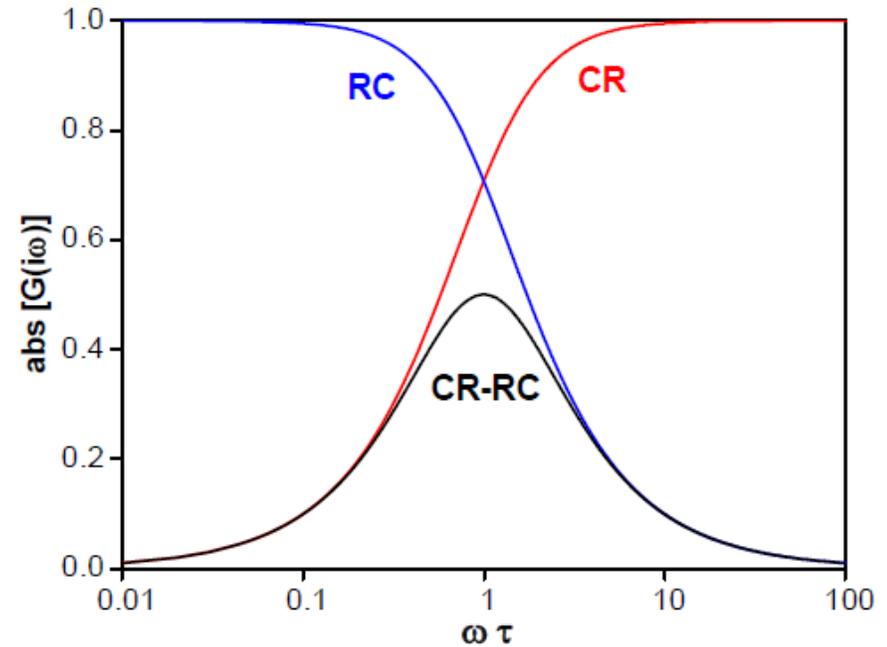if  $\tau_1 = \tau_2$   $\rightarrow$   $V_{out}(t) = \frac{V_0}{\tau} t e^{-t/\tau}$




Frequency domaine:  
Pass high \* pass low

$$G_{CR-RC}(s) = \frac{1}{(1 + \tau_2 s)} \frac{\tau_1 s}{(1 + \tau_1 s)}$$

# Filter / Shaper

## first order? second? Why
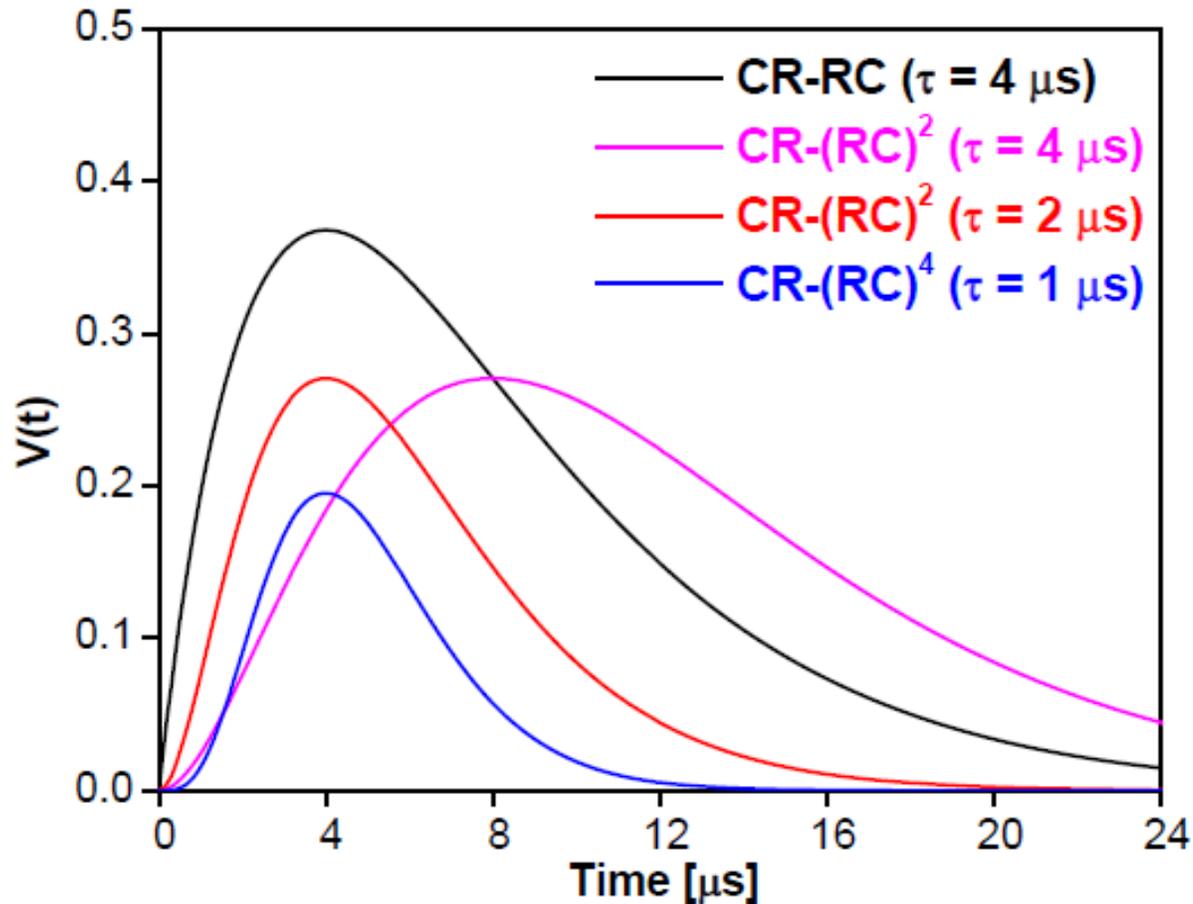
# CR\*RC<sup>n</sup> filters or Semi-Gaussian pulse shaping




If a single CR high-pass filter is followed by several stages of RC integration, the output pulse shape becomes close to Gaussian amplifiers shaping, in this way are called **semi-Gaussian shaper**. Its output pulse is given by:

$$V_{out}(t) \propto \left(\frac{t}{\tau}\right)^n e^{-t/\tau}$$

The peaking time in this case is equal to  $n*\tau$ .
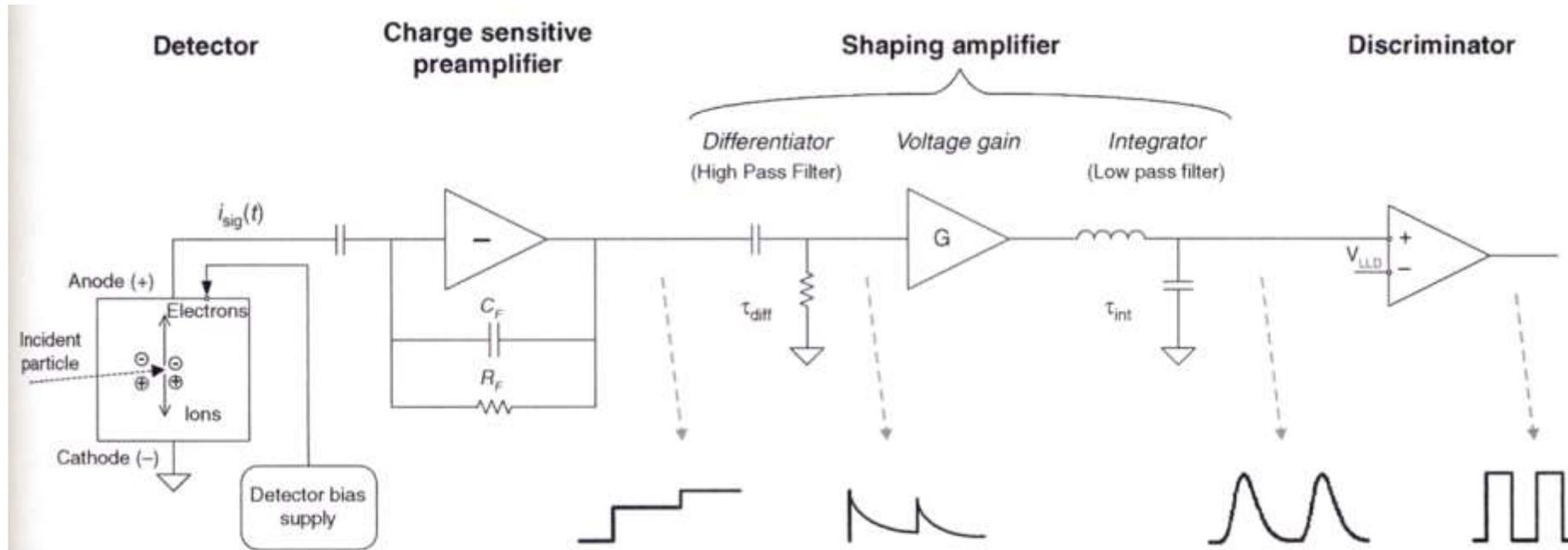
# Signal shape following read out steps when 2 successive pulses (II)




Schematic of simple signal processing electronics. This circuit is suitable for use, as shown, in many applications and is conceptually similar to more complex circuits. These elements are discussed in greater detail in Chapter 17. (Courtesy of R. Redus, Amptek, Inc.)


Courtesy, Glenn F. « radiation detection »
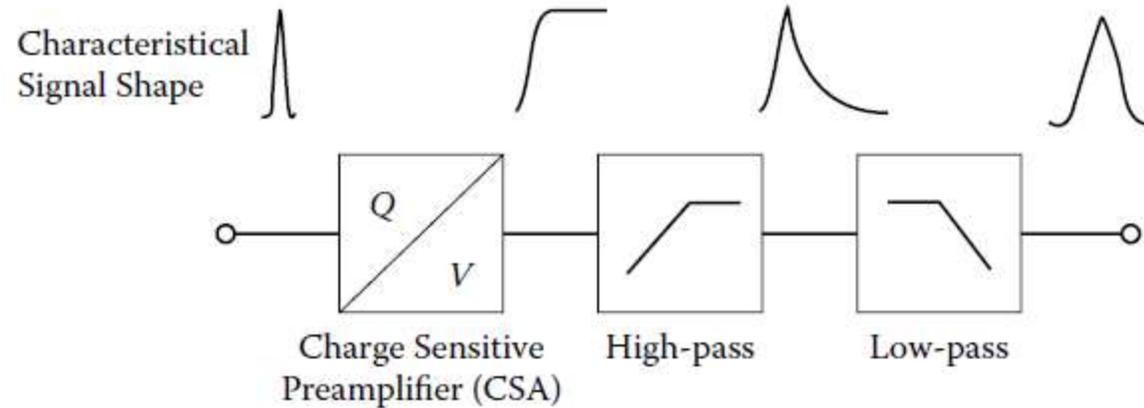
# Simplified Signal shape throughout electronic readout

**Charge sensitive**  
Signal conditioning



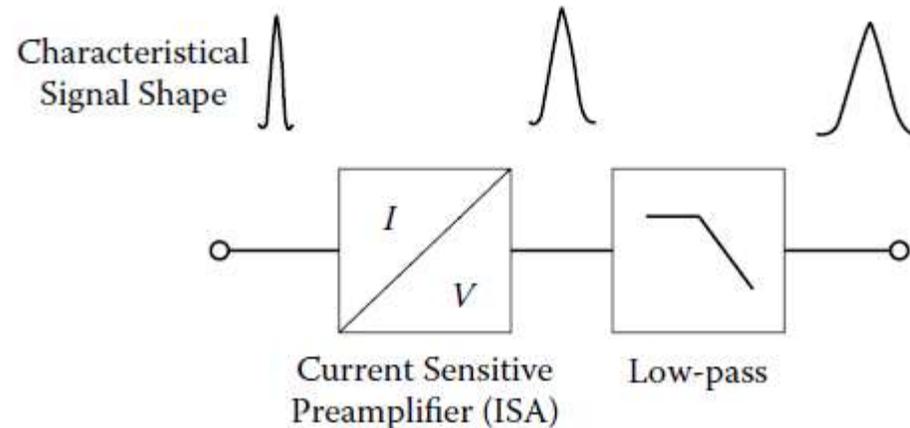**Current sensitive**  
Signal conditioning



# WHAT IS NOISE ?



## ◆ What is noise?

- **Noise is any undesired signal that masks the signal of interest.**
  - Unwanted disturbance that interferes with a desired signal
  - External: power supply & substrate coupling, crosstalk, EMI, etc.
  - Internal: random fluctuations that result from the physics of the devices or materials
  - Smallest detectable signal, signal-to-noise ratio (SNR), and dynamic range are determined by noise

$$SNR = \frac{P_{signal}}{P_{noise}} = \frac{V_{rms,signal}^2}{V_{rms,noise}^2}$$


**We will look at internal noise sources and how they affect key performance metrics.**
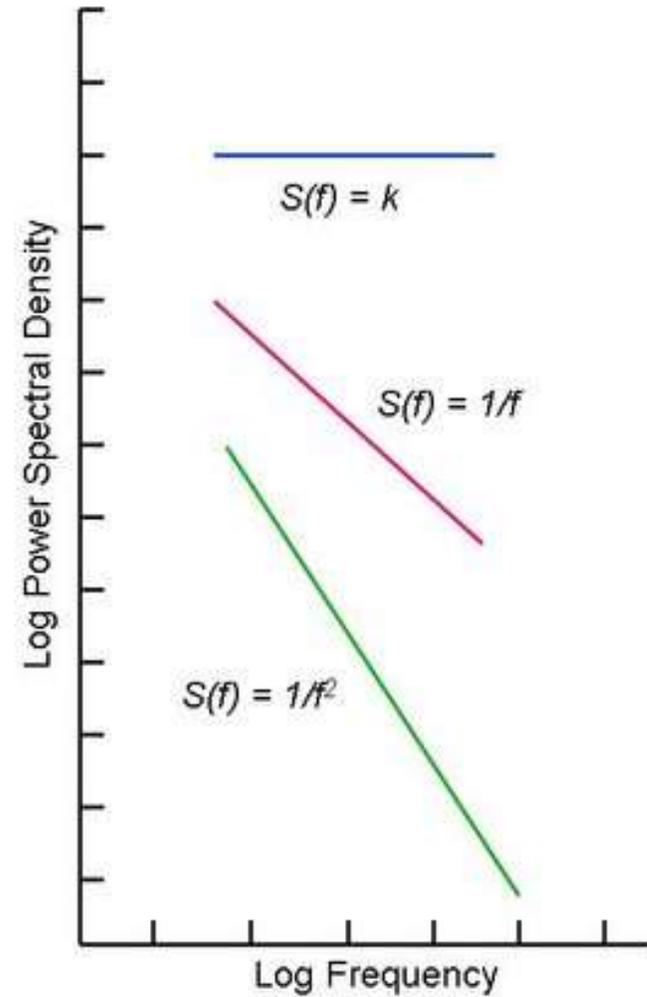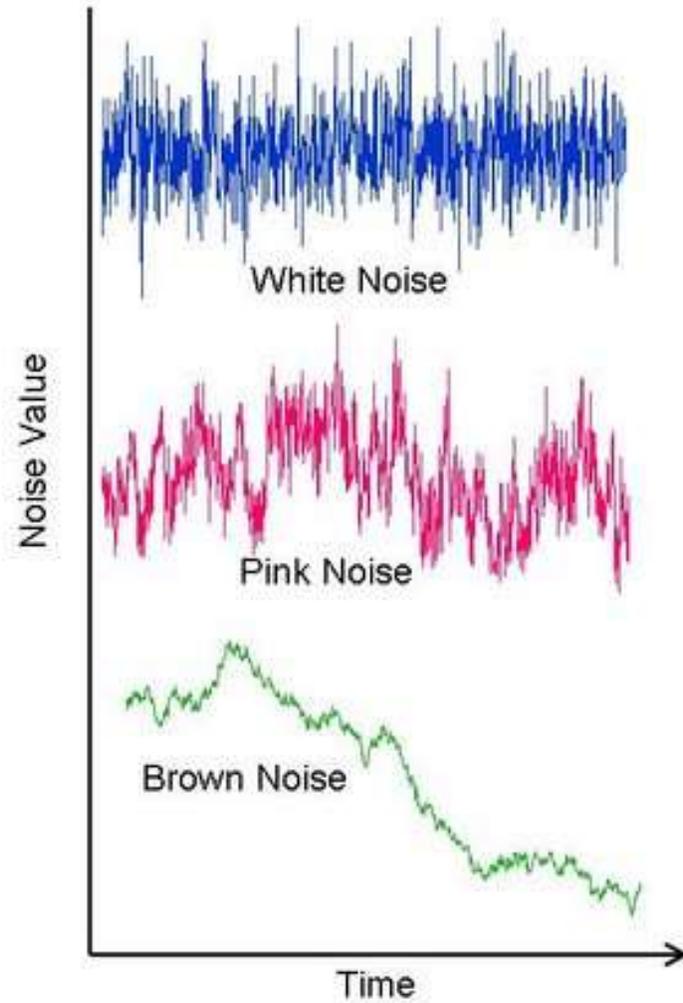
# Noise in general: time & frequency domain



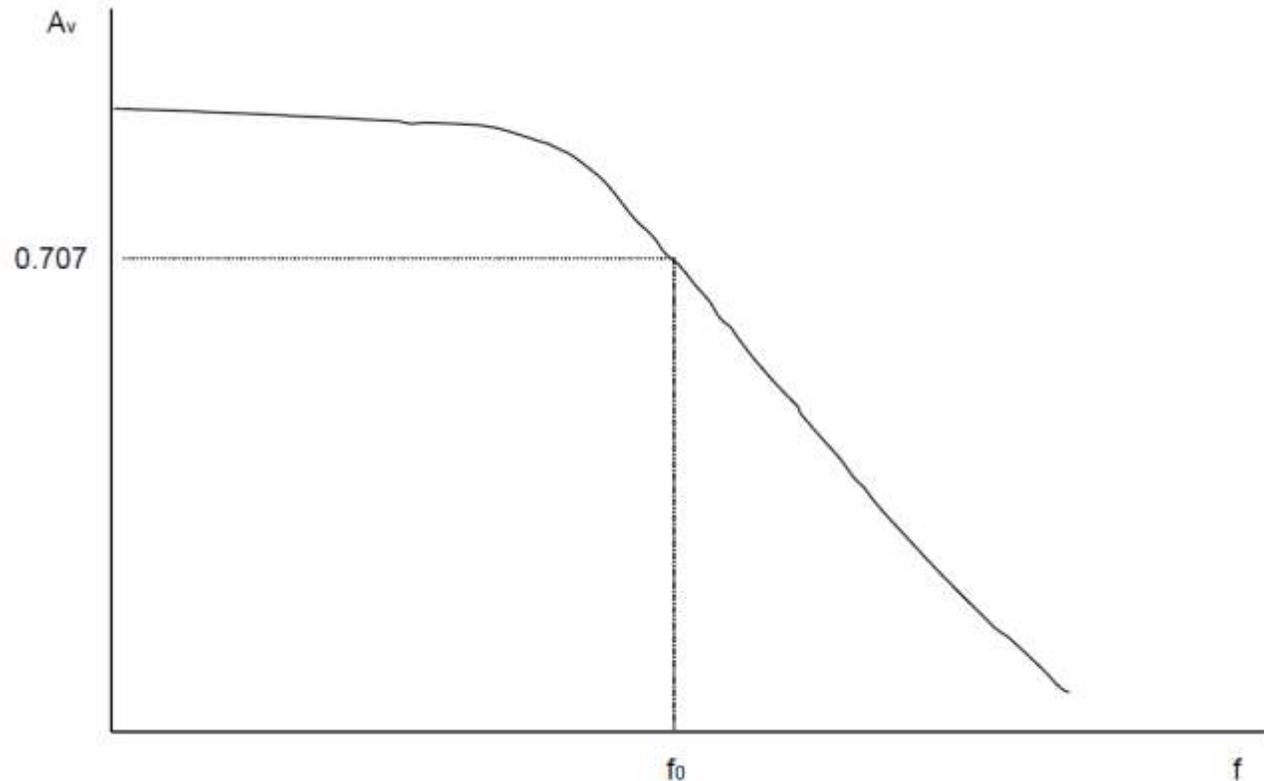
# Noise Effective BW (NEB) of an amplifier (filter)

Lets consider a general *low pass* amplification (filter) system;  
What happen to a white noise located at the input of such amplifier?  
Is it amplified exactly as the signal?



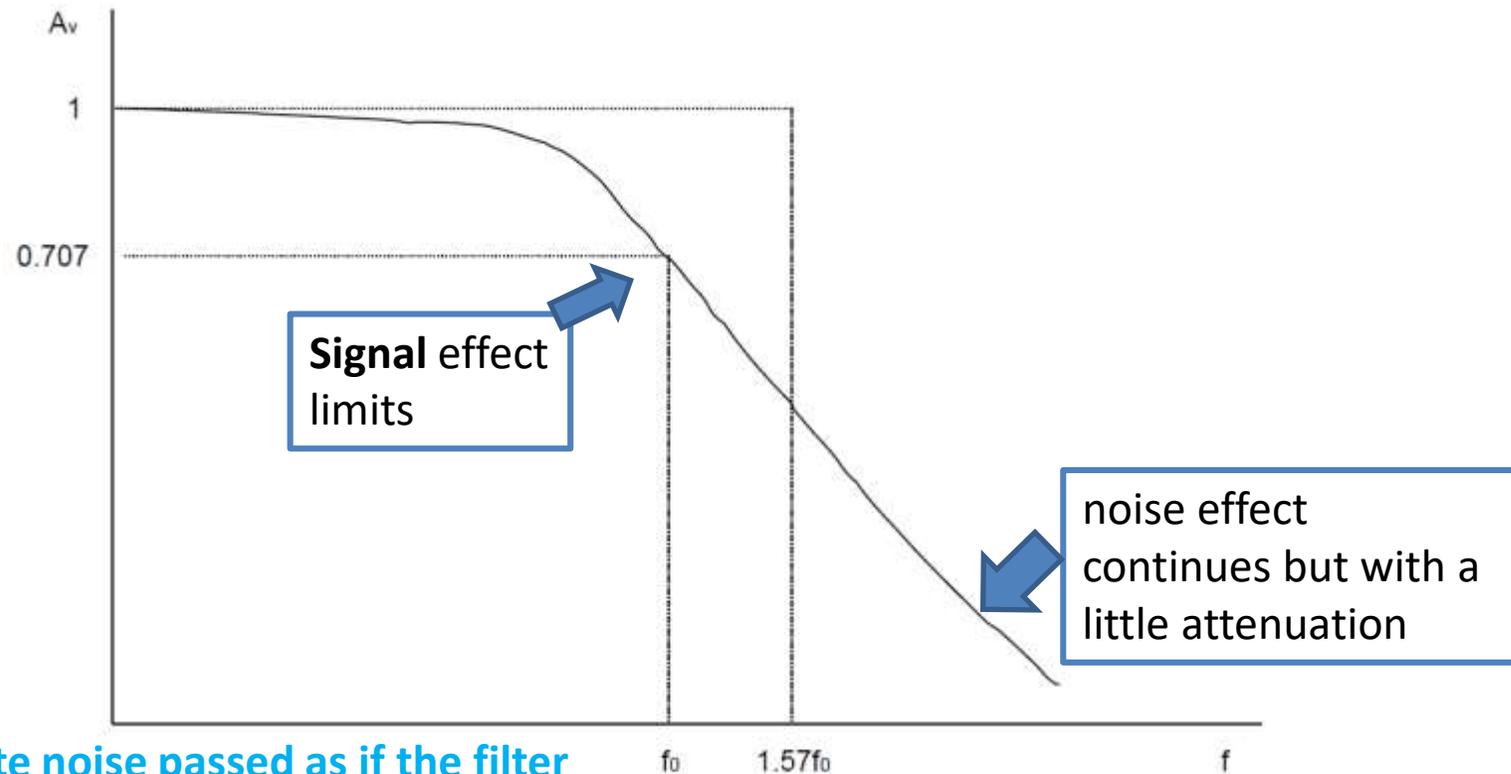
# Noise bandwidth

Lets consider a low pass amplification system;  
What is the effect of a larger bandwidth white noise located at the input of such amplifier?



The white noise passed as if the filter were a brick wall type but with a cutoff freq 1.57 times larger

# Noise Bandwidth # signal bandwidth

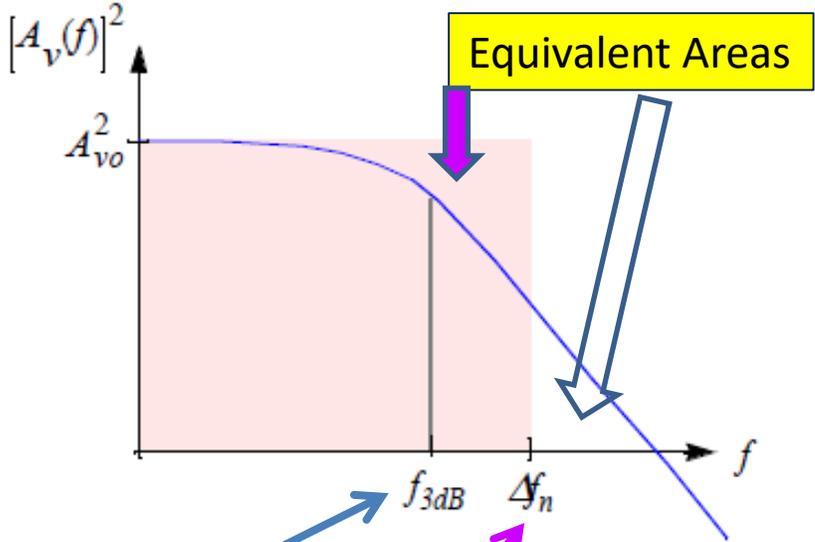

No. Poles	NOISE BW
1	$\Delta f_n = \frac{\pi}{2} \cdot \Delta f_{3dB}$
2	$\Delta f_n = 1.22 \cdot \Delta f_{3dB}$
3	$\Delta f_n = 1.16 \cdot \Delta f_{3dB}$
2nd-order BPF	$\Delta f_n = \frac{\pi}{2} \cdot \Delta f_{3dB}$

Signal concern

Noise concern

$$A_{vo}^2 \cdot \Delta f_n = \int_0^{\infty} [A_v(f)]^2 df$$

- Noise bandwidth is defined for a brickwall transfer function
- Noise bandwidth is not the same as 3dB bandwidth

Noise Bandwidth improves when number of poles increase  
 Keep it in mind and make the link later with CRRCn filtering

# Optimizing Filtering $\Leftrightarrow$ Optimize NEB

For Maximally flat (Butterworth) where  $f_0 = f_{3dB}$

$$NEB = \left( \int_0^{\infty} \frac{df}{1 + (f / f_0)^{2n}} \right)$$

**But** higher order n means:  
More complicated and/or  
more power budget


n	NEB
1	$1.57f_0$
2	$1.11f_0$
3	$1.05f_0$
4	$1.025f_0$

In spectroscopic,  
One considers  
in general **n=2**

High order filter is good(0.5dB improvement)


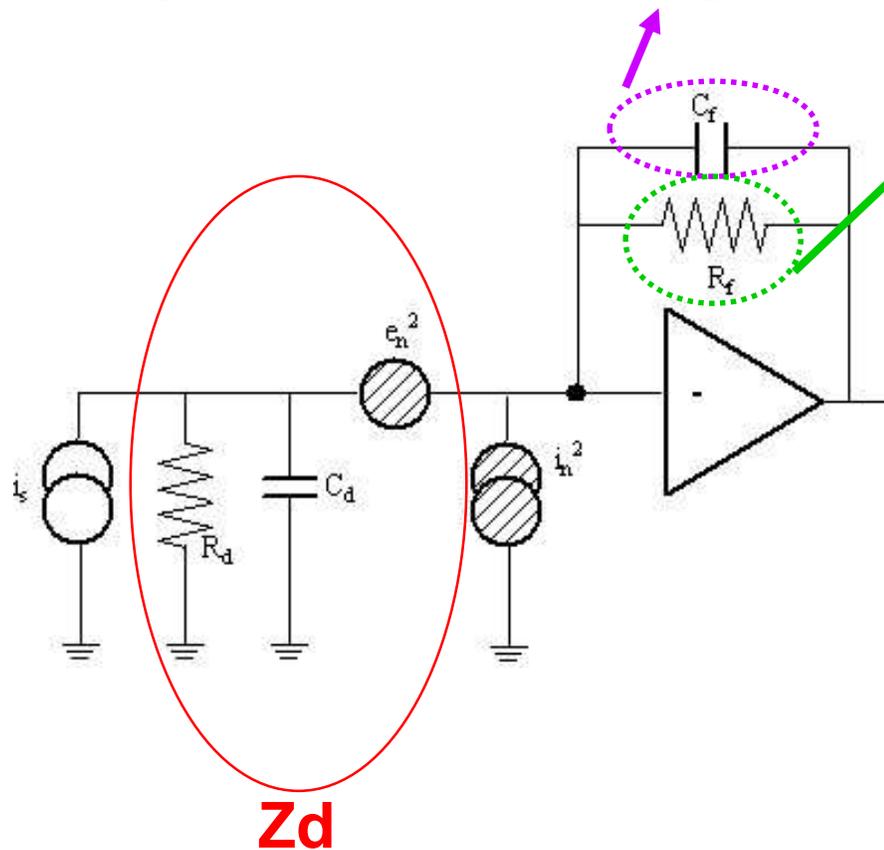
# Preamplifier: charges / Courant output noise



Noise spectrum at the output


$$S_v(\omega) = ( i_n^2 + e_n^2 / |Z_d|^2 ) / \omega^2 C_f^2$$

$$= i_n^2 / \omega^2 C_f^2 + e_n^2 C_d^2 / C_f^2$$


If we neglect  $R_d$  and we translate  $e_n$  to a current  
By doing  $e_n / Z_d$

# Noise issues for charge preamp: frequency domaine

- 2 noise generators at the input
  - Parallel noise : ( $i_n^2$ ) (leakage currents)
  - Series noise : ( $e_n^2$ ) (preamp)
- Output noise spectral density :
  - $S_v(\omega) = (i_n^2 + e_n^2/|Z_d|^2) / \omega^2 C_f^2$   
 $= i_n^2 / \omega^2 C_f^2 + e_n^2 C_d^2 / C_f^2$
  - Parallel noise in  $1/\omega^2$
  - Series noise is flat, with a « noise gain » of  $C_d/C_f$
- rms noise  $V_n$ 
  - $V_n^2 = \int S_v(\omega) d\omega/2\pi \rightarrow \infty$  (!)
  - Benefit of shaping...


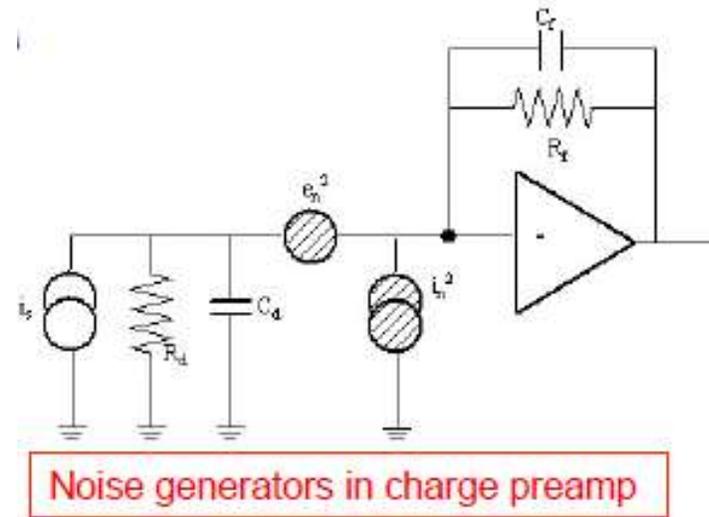


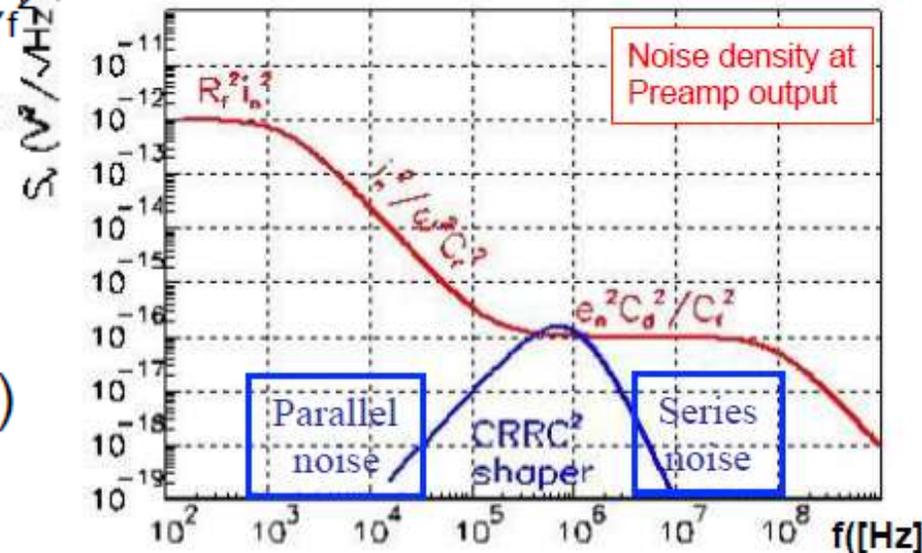*The methode here is to  
Transfert each input  
To current domain, then  
Multiply by the feedback*





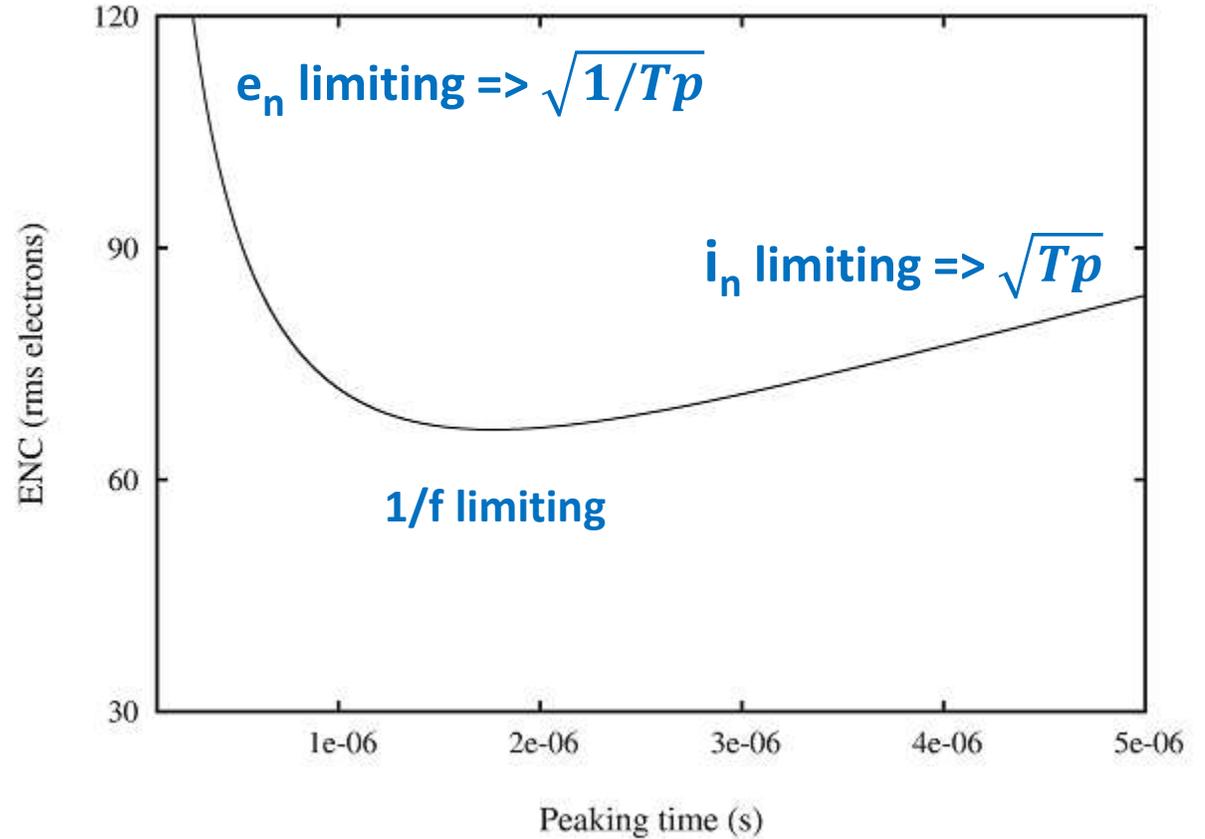
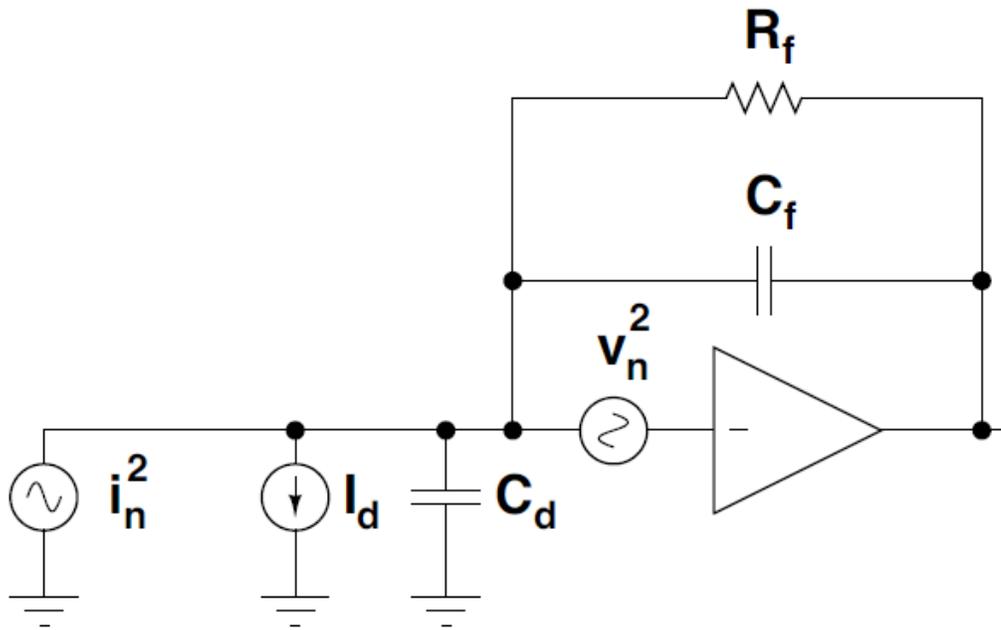
# Noise issues in charge preamp: *time domain*



$$ENC^2 = (C_d + C_{in})^2 \left( A_w v_n^2 \frac{1}{T_p} + A_f K_f \right) + A_p i_n^2 T_p$$

↑  
Increase with  $C_d$
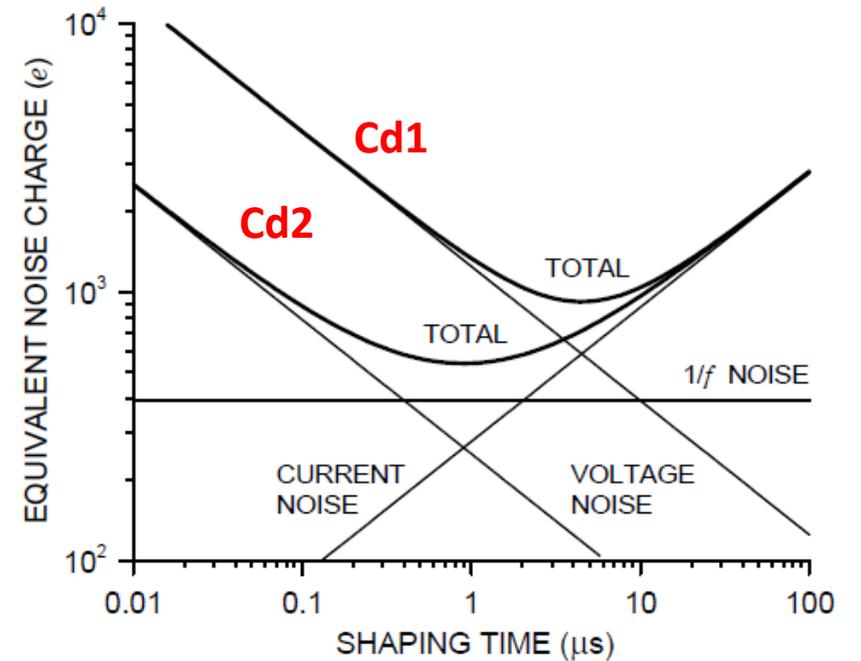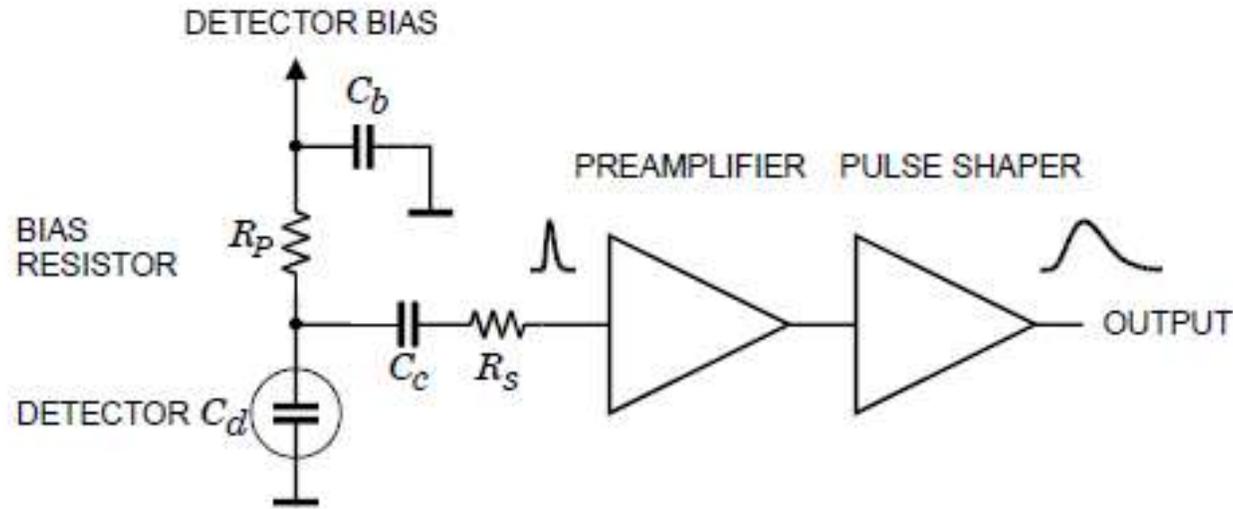
# Practical summary about noise in charge integrator



ENC using a simple CR-RC shaper with peaking time  $T$ :

$$Q_n^2 \approx \left[ \left( 2q_e I_d + \frac{4kT}{R_p} + i_{na}^2 \right) \cdot T + \left( 4kTR_s + e_{na}^2 \right) \cdot \frac{C_d^2}{T} + 4A_f C_d^2 \right]$$


↑	↑	↑
current noise	voltage noise	1/f noise
$\propto T$	$\propto 1/T$	independent of $T$
independent of $C_d$	$\propto C_d^2$	$\propto C_d^2$

# One stage preamplifier scheme

- The main contributor to the total noise is the **preamp input transistor**. We consider next the contribution of this transistor to the equivalent noise  $\mathbf{e}_n$  and  $\mathbf{i}_n$
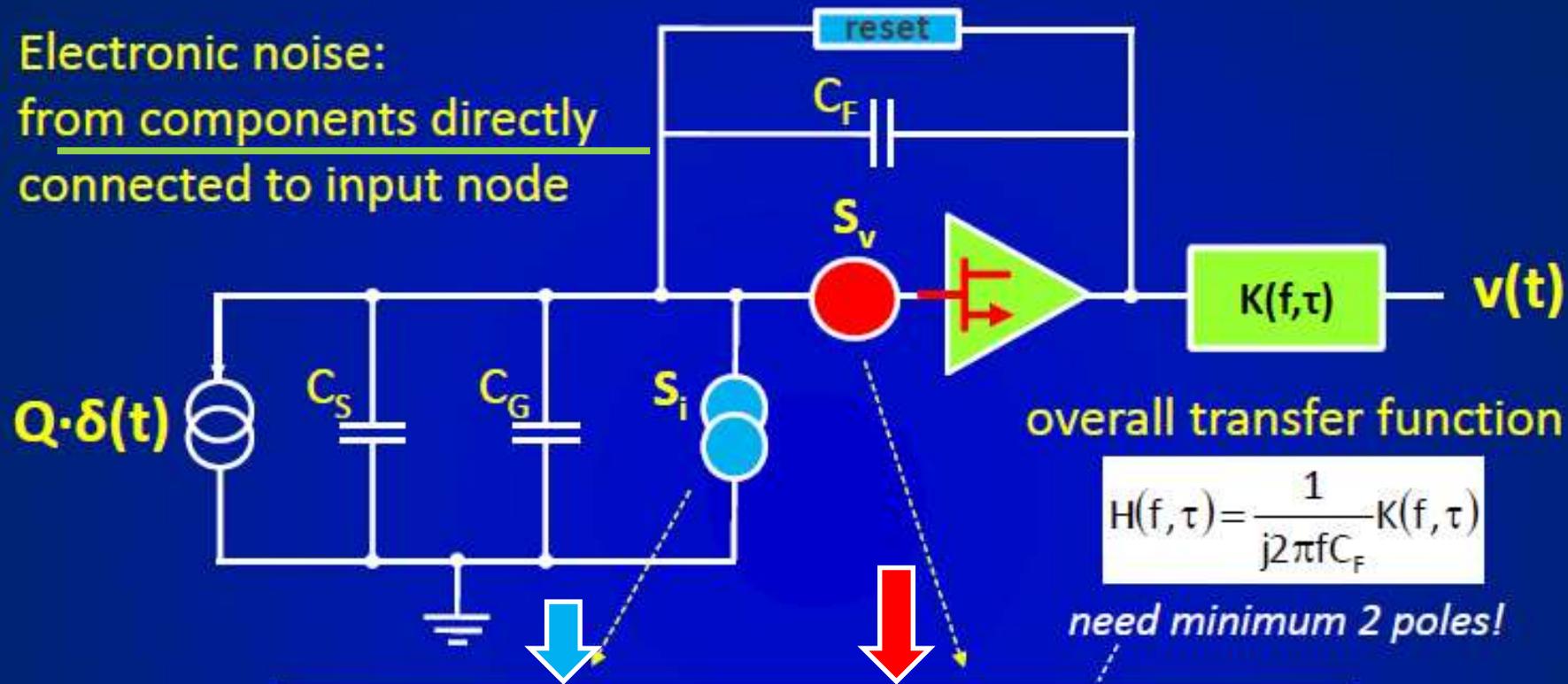
# Sources of Electronic Noise

Electronic noise:  
from components directly  
connected to input node



overall transfer function

$$H(f, \tau) = \frac{1}{j2\pi f C_F} K(f, \tau)$$


*need minimum 2 poles!*

$$ENC^2 \cong \frac{\int_0^{\infty} S_i |H(f, \tau)|^2 df + \int_0^{\infty} S_v \omega^2 (C_S + C_G)^2 |H(f)|^2 df}{h(t)_{\max}^2}$$

Here, time appears in equations

Time-variant → time-domain analysis (noise weighting function)

# Noise from Input Transistor

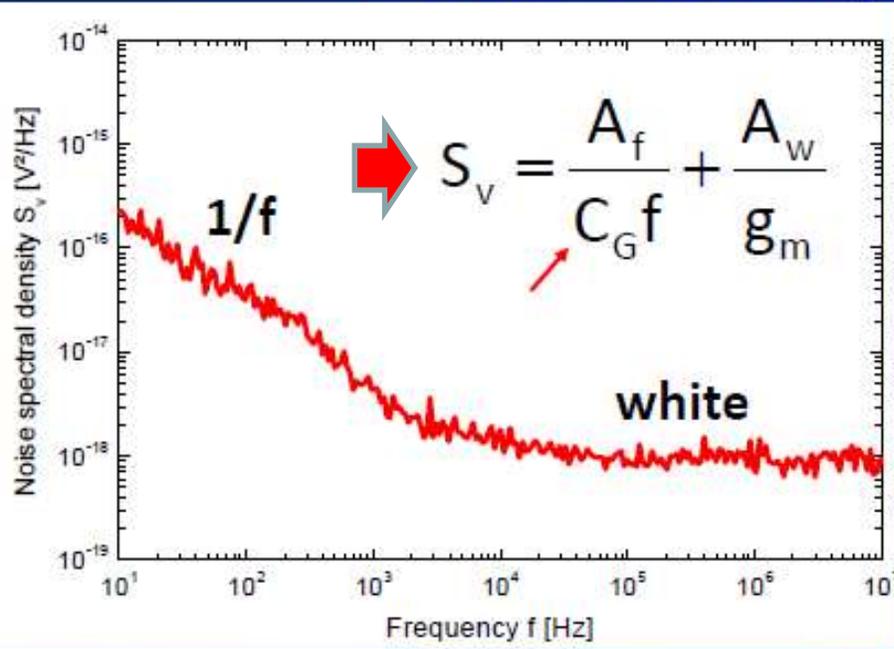

$C_G$  intrinsic gate capacitance  
proportional to the gate size

$C_G = C_S$  (capacitive matching)

From input transistor:

$$ENC_v^2 = a_f A_f \frac{(C_S + C_G)^2}{C_G} + \frac{a_w}{\tau} \frac{A_w}{g_m / C_G} \frac{(C_S + C_G)^2}{C_G}$$

**ASIC: power constraints**

$f_{Tmax} f_T$  (max current)

# Input Transistor in CMOS

From transistor's white noise:

$$ENC_{vw}^2 \approx \frac{a_w}{\tau} \frac{A_w}{g_m(I_D)/C_G} \frac{(C_S + C_G)^2}{C_G}$$

Fix power = fix drain current  $I_D$   
 → size (W,L) ?

$V_{GS} \gg V_{th}$  (strong inversion)

$$g_m(I_D) \approx \sqrt{\frac{2\mu C_{ox}}{n} \frac{W}{L} I_D} \propto \sqrt{\frac{C_G I_D}{L^2}}$$



$$ENC_{vw}^2 \propto \frac{L}{\sqrt{I_D}} \frac{(C_S + C_G)^2}{\sqrt{C_G}}$$

- minimum L
- $C_G = C_S/3$



$V_{GS} \ll V_{th}$  (weak inversion)

$$g_m(I_D) \approx \frac{I_D}{nV_T} \propto I_D$$




$$ENC_{vw}^2 \propto \frac{(C_S + C_G)^2}{I_D}$$

- independent of L
- $C_G = 0$  pushes back towards strong inversion

→  $V_{GS} \approx V_{th}$  (moderate inversion): model?

# Moderate Inversion

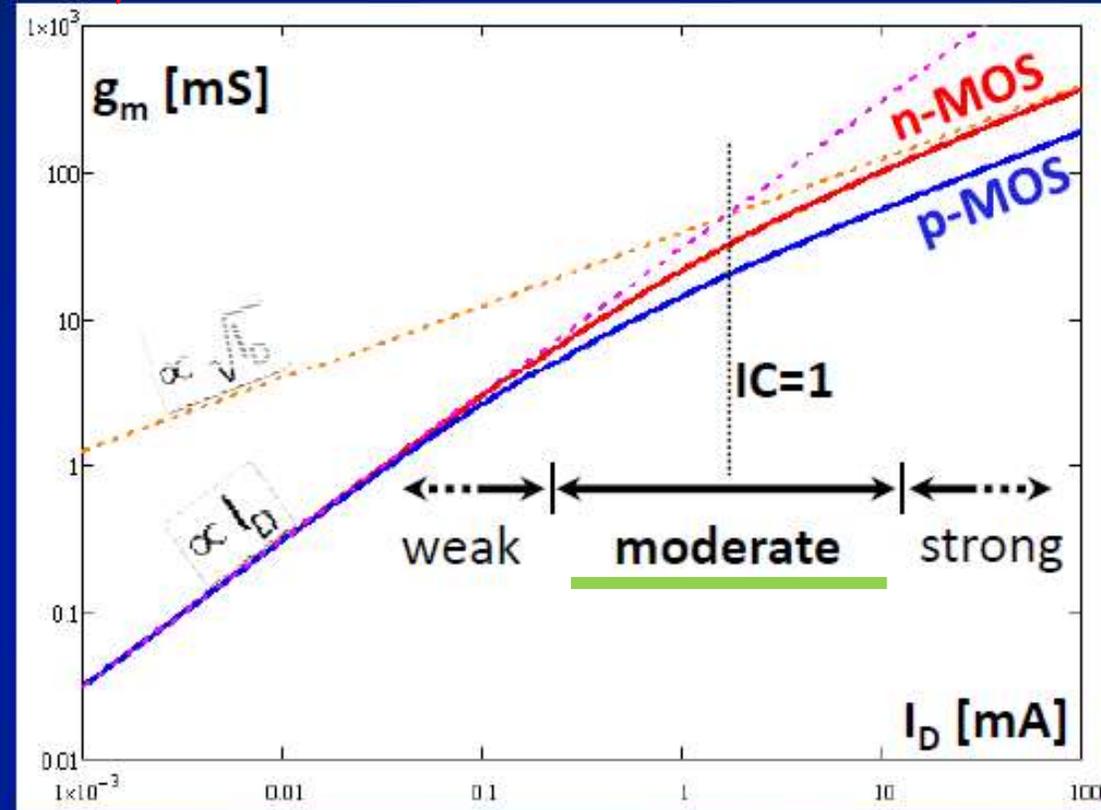

Notice  $g_m/I_D$  efficiency

From EKV model

$$g_m(I_D) \approx \frac{I_D}{nV_T} \frac{\sqrt{1+4 \cdot IC} - 1}{2 \cdot IC}$$


$$IC = \frac{L}{W} \frac{I_D}{2nV_T^2 \mu c_{ox}}$$

inversion coefficient

alternative: extract from simulators (BSIM)

De Geronimo, IEEE TNS 52, 2005

# Gate Capacitance

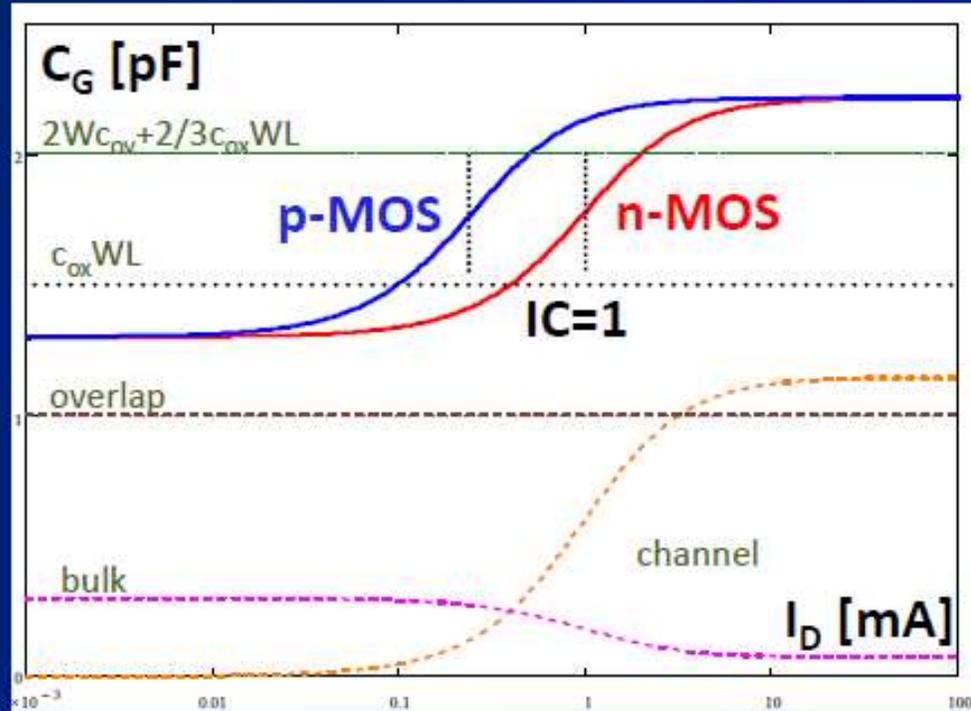

~~$\propto C_{ox} WL$~~

$$C_G(I_D) \approx 2c_{ov} W + C_{ox} WL \left( \gamma_c(IC) + \frac{n-1}{n} [1 - \gamma_c(IC)] \right)$$


$$\gamma_c(IC) \approx \left( \frac{3}{2} + \frac{1}{3} \frac{\sqrt{1+4 \cdot IC+1}}{IC^2} \right)^{-2/3}$$

➔ Both  $g_m$  and  $C_G$  push towards using n-channel and  $L = L_{min}$

Conclusion 1: considering ( $g_m$  and  $C_g$ )

**BUT,**  
now let add the  $1/f$  noise contribution

# Low-Frequency Noise

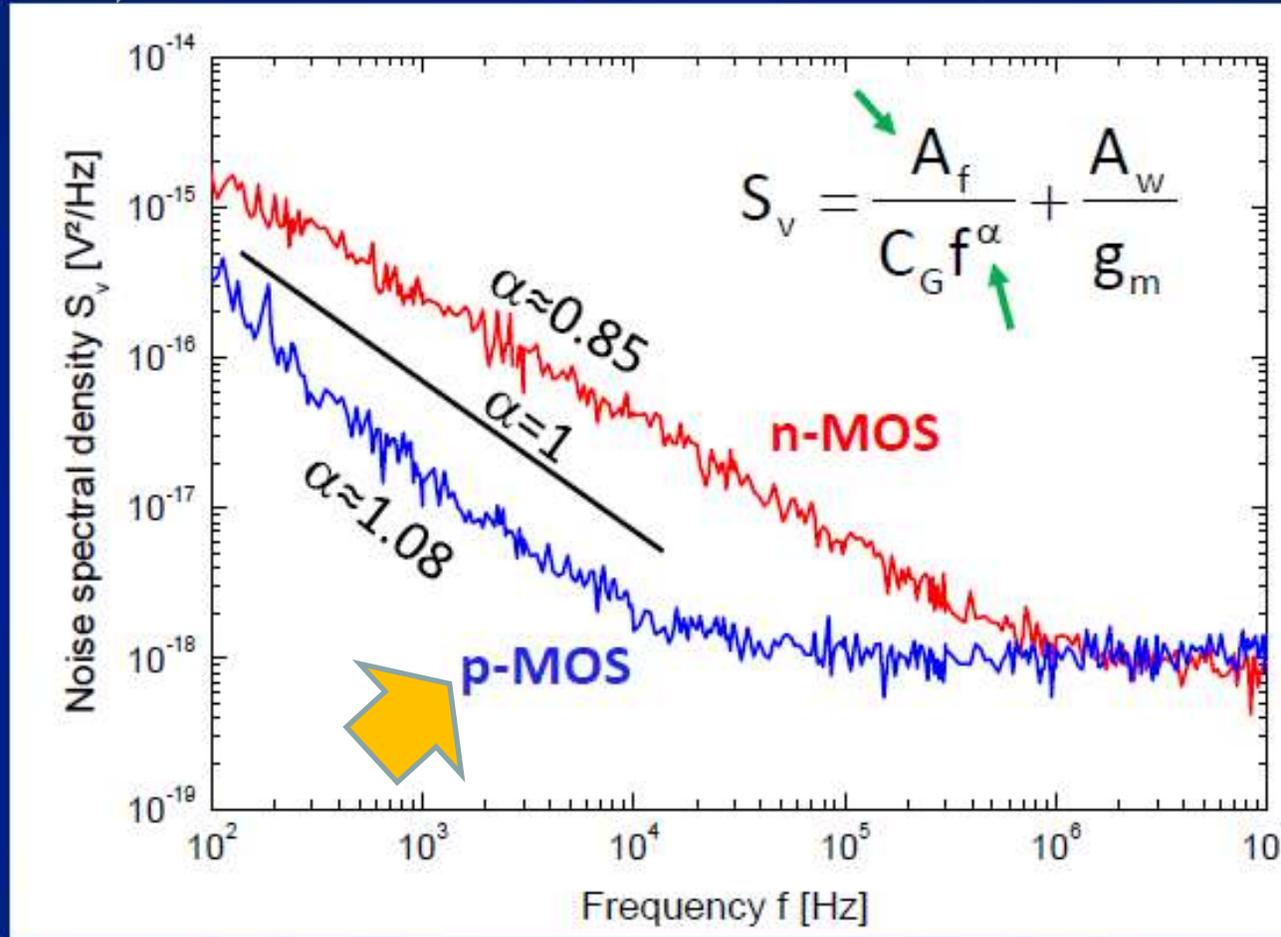


From transistor's low-freq. noise:

$$ENC_{vf}^2 = a_f(\alpha) \frac{A_f}{\tau^{1-\alpha}} \frac{(C_S + C_G)^2}{C_G}$$

depends on  $\tau$

# Low-Frequency Noise vs L

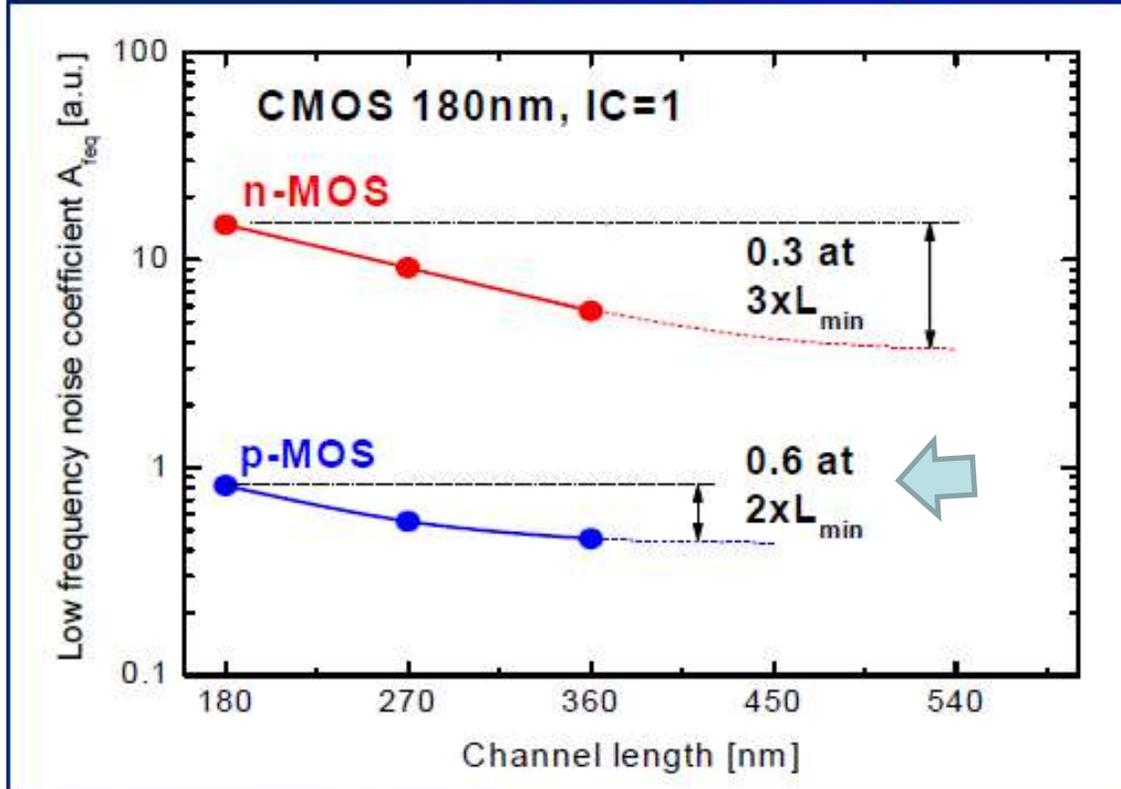

$$S_v = \frac{A_f(L)}{C_G f^\alpha} + \frac{A_w}{g_m}$$

1/f equivalent, IEEE TNS 58, 2011

From transistor's low-freq. noise:

$$ENC_{vf}^2 = a_f(\alpha) \frac{A_f(L) (C_S + C_G)^2}{\tau^{1-\alpha} C_G}$$

**Conclusion 2**

**LF noise pushes towards p-channel &  $L > L_{min}$**



# Preamp trends with aggressive process

# Preamp design & 'Scaling'

One may consider 2 prospection studies (old now !!)

1) **Paul O'Connor** => Brookhaven Lab, Upton , New York: 1,5μ au 180n

At constant power one save 23% in term of noise per generation:  $\lambda=0.7$

$$\text{ENC}' = \lambda^{3/4} * \text{ENC}$$

At constant noise: one save 60% of power per generation

$$P' = \lambda^3 * P$$

But in dynamique range, one lose 10% of SNR per generation


$$\text{SNR}' = \lambda^{1/4} * \text{SNR}$$

2) **L. Rattia** NSS 2007 => Università degli Studi di Pavia : 100n et 90n

**Next slides show some of L. Rattia' work**
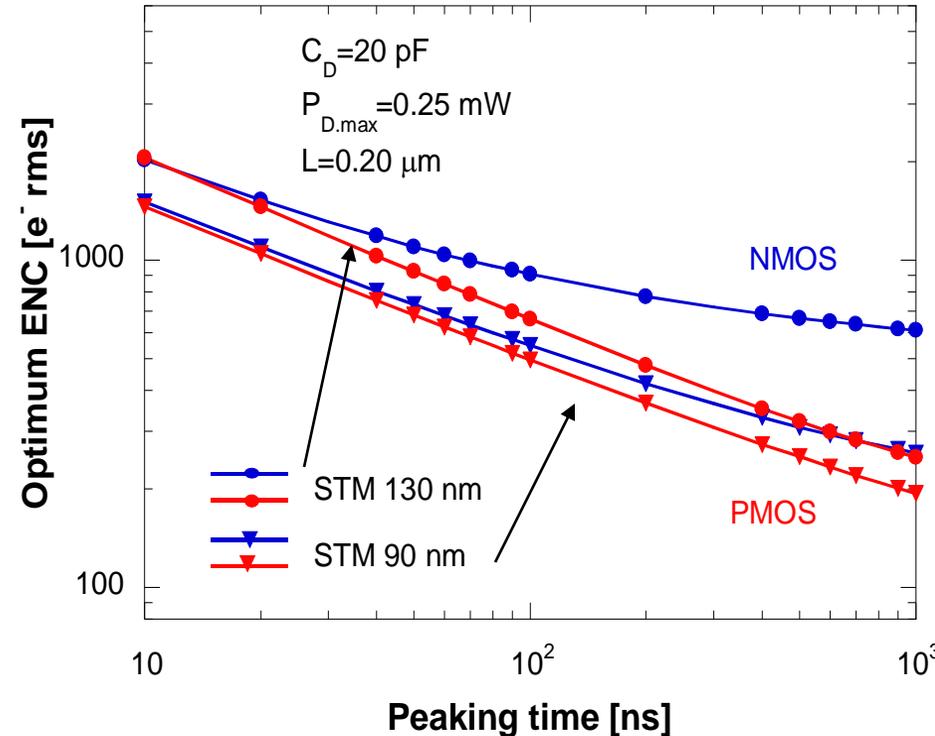
# ENC vs peaking time, @ $P_d = cte$

L. Rattia NSS 2007 =>The 90nm leads to less ENC (noise) than the 130nm





ENC was evaluated in the case of a second order, unipolar (RC<sup>2</sup>-CR) shaping processor


- In the explored peaking time and power range, **PMOS input device** always provides better noise performances than NMOS input (*except for the 130 nm process at  $t_p$  close to 10 ns*)
- Using the 90 nm process may yield quite significant improvement with respect to the 130 nm technology, especially when NMOS input charge preamplifiers are considered
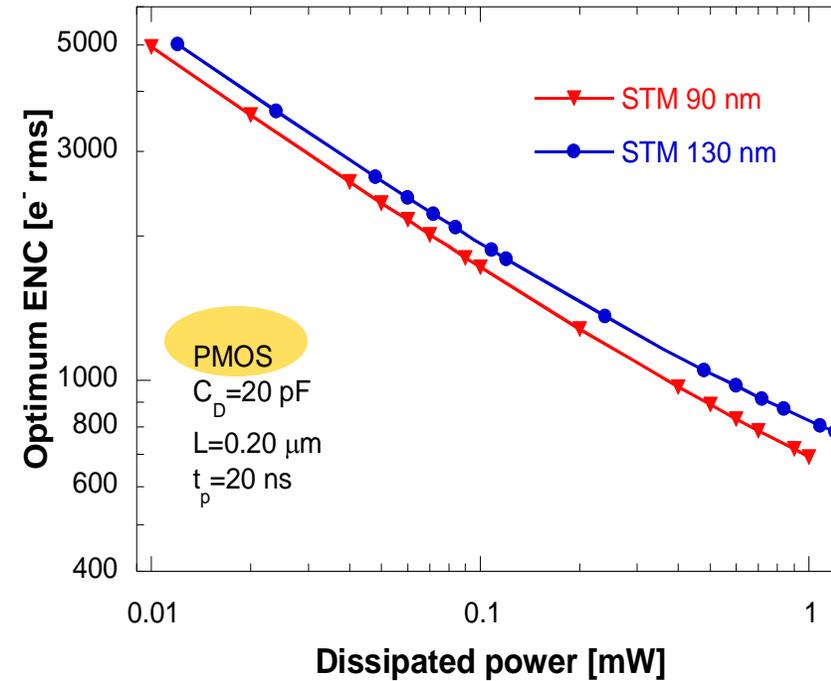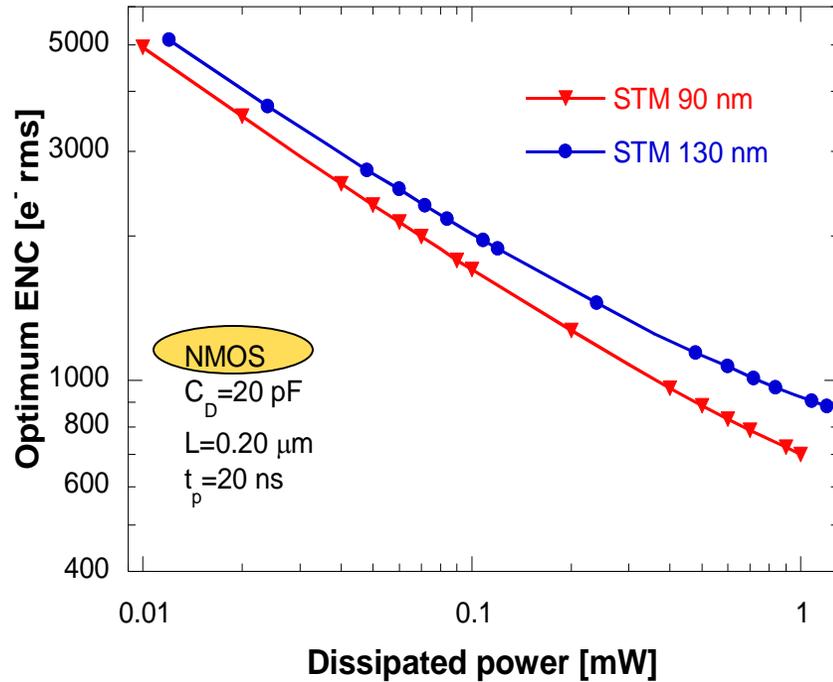
# ENC as function of power necessary ( $P$ et $N$ ) **for given $t_p$**

**L. Rattia NSS 2007** => The 90nm needs less power at a constant noise level




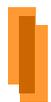At  $t_p=20$  ns, noise performances provided by NMOS and PMOS input devices in the 90 nm technology are comparable



Better noise-power trade-off can be achieved by using the 90 nm technology

# Figure of Merit for a MOS Process

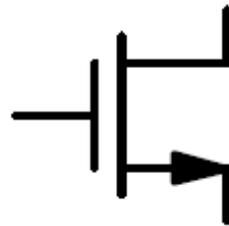

- Transit Frequency

$$\omega_T = \frac{g_m}{C_{gs}}$$

- Transconductor Efficiency

$$\frac{g_m}{I_D}$$

- Intrinsic Gain

$$g_m r_o$$


**DO NOT FORGET:** You may optimize the *bias point of input transistor* (moderate inversion, for a  $g_m/I_D$  efficiency)



# **HOW THE AMPLIFIER STAGE IS BUILT USING TRANSISTORS**

Exemple of single stage amplifier
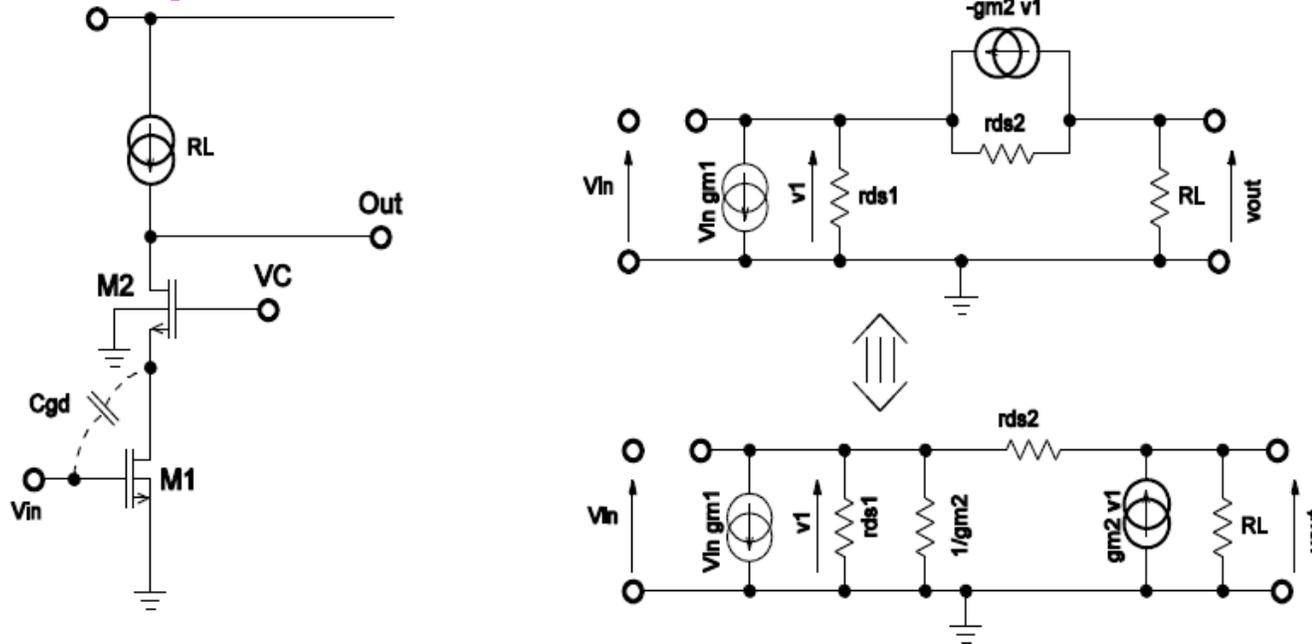
# Telescopic Cascode: Common source-common gain




$$K_U \cong \frac{-g_{m1}}{g_{DS1} \frac{g_{DS2}}{g_{m2}} + g_L}$$

$$GBW = \frac{g_{m1}}{2\pi C_{OUT}}$$

Courtesy Y. Kaplon, Cern

- ❑ single stage amplifier; one dominant pole
- ❑ no Miller effect (low gain of common source stage)

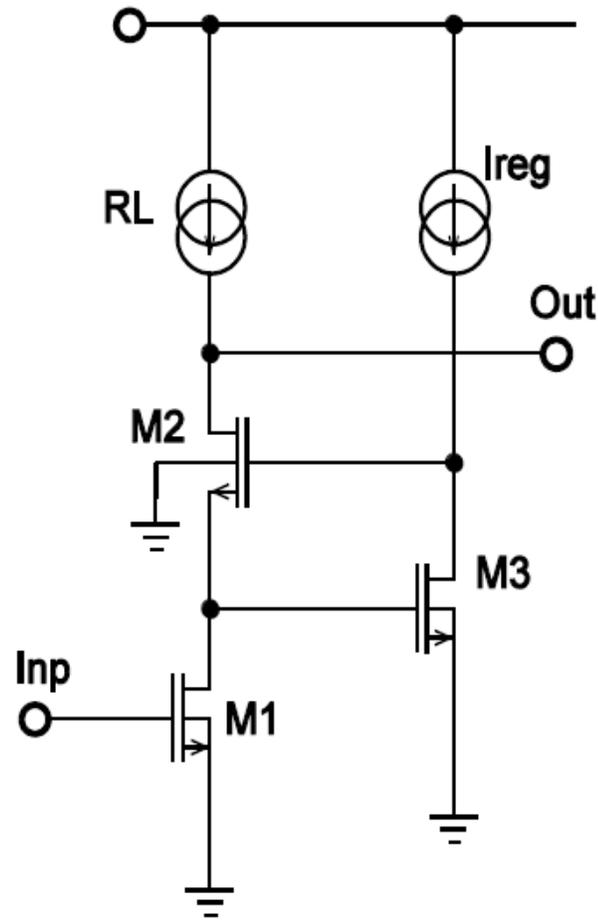
# Regulated Cascode: **A0** improvement by acting on the cascode



$$K_U \cong \frac{-g_{m1}}{\frac{g_{DS1} \cdot g_{DS2}}{g_{m2}} \cdot \frac{g_{DS3}}{g_{m3}} + g_L}$$

- Cascode transistor controlled with common source amplifier
- Higher output conductance of cascode; possible higher gain
- GBW the same as for simple cascode
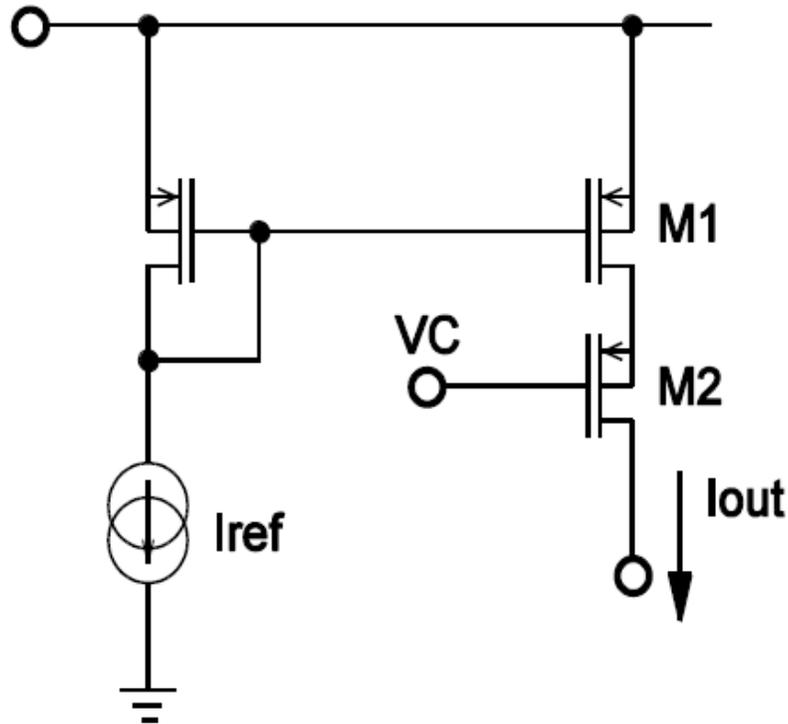
# Cascode current: gain boosting via the load




$$r_{OUT} \cong g_{m2} \cdot r_{DS2} \cdot r_{DS1}$$

But the dynamic range is reduced by  $2 \cdot V_{dssat}$

- ❑ Amplification of  $r_{DS1}$  by  $g_{m2}$
- ❑ For short SSD application; OK for 250nm, not sufficient for 130 & 90nm

# Boosting both Gain & bandwidth

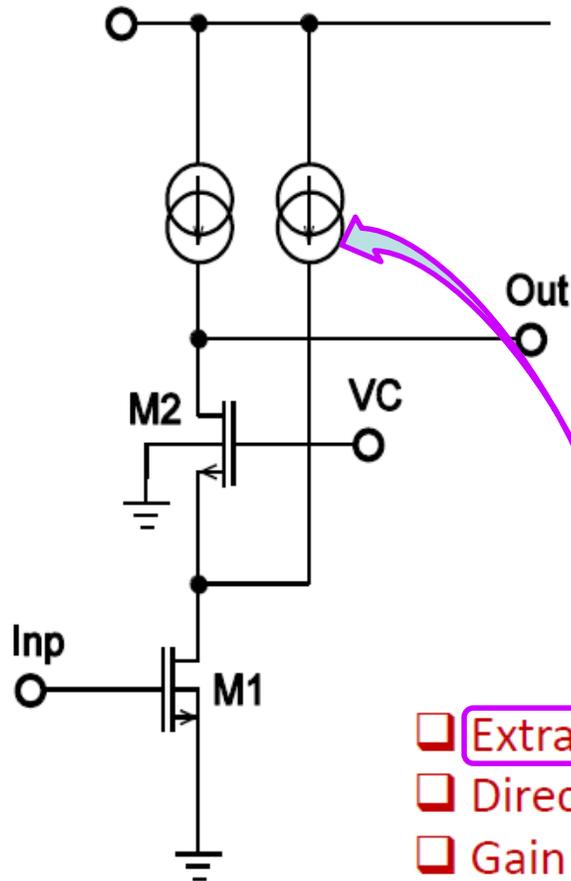

$$GBW = \frac{g_{m1}}{2\pi C_{OUT}}$$

$$K_U \cong \frac{-g_{m1}}{g_{DS1} \cdot g_{DS2} + g_L}$$

- ❑ Extra current source to drain of M1 → increase of  $g_{m1}$
- ❑ Direct impact on gain bandwidth
- ❑ Gain changed according to output conductance of cascode and active load


Courtesy Y. Kaplon, Cern

After the amplification schemes, let introduce how electronics noise looks like in the readout flow

## **NOISE EFFECT IN THE FLOW**

# Noise: Time domain characteristics

## Noise: Time Domain Characteristics

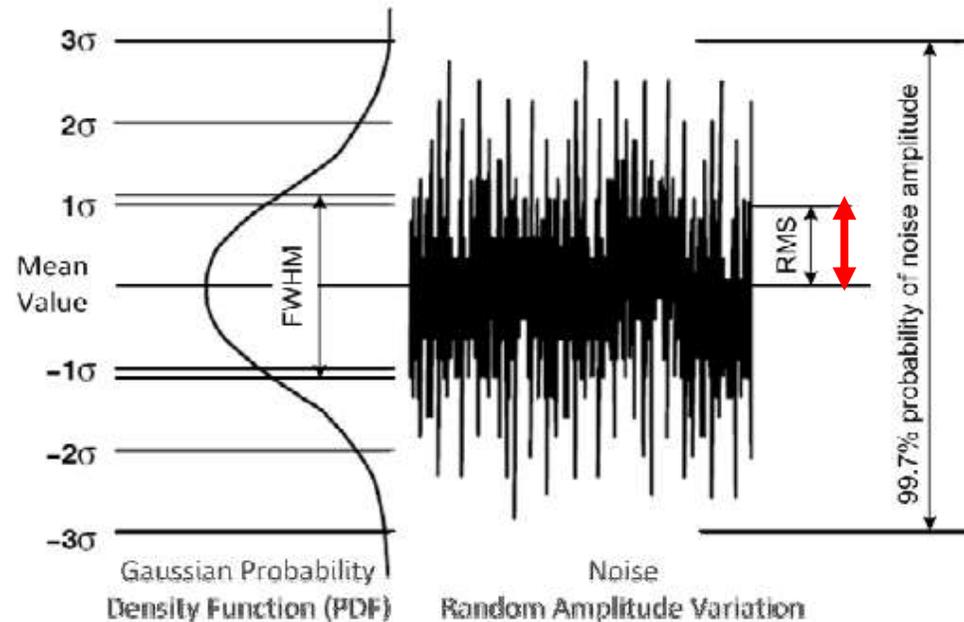


- Noise amplitudes vary randomly with time.
- Noise can only be specified by a Probability Density Function (PDF).
- Thermal noise and shot noise have Gaussian PDFs.
- Theoretically Gaussian noise amplitudes may have values approaching infinity.

Topics for later sessions

How can one characterize a comparator for counting accurately?

In counting flow: Frequency of noise hits (**fn**);  
Threshold **Vth**; input noise (**vn**) ...

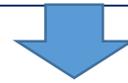**S. O. Rice** *Mathematical analysis of random noise* [1945] Bell System Technical journal, 24; 46-156



- How often are noisy events counted?
- Noise at your comparator input?
- Threshold value above the baseline?
- Counting rate and so your bandwidth or  $\tau$ ?


$$f_n = \frac{1}{2\pi\tau} e^{-(V_{th}^2/2V_n^2)}$$

Or Threshold over noise ratio

$$\frac{V_{th}}{V_n} = \sqrt{-2\ln(f_n * 2\pi\tau)}$$

**EXO: estimate  $f_n$  for  $V_{th}/V_n = 7$  for different  $\tau$**
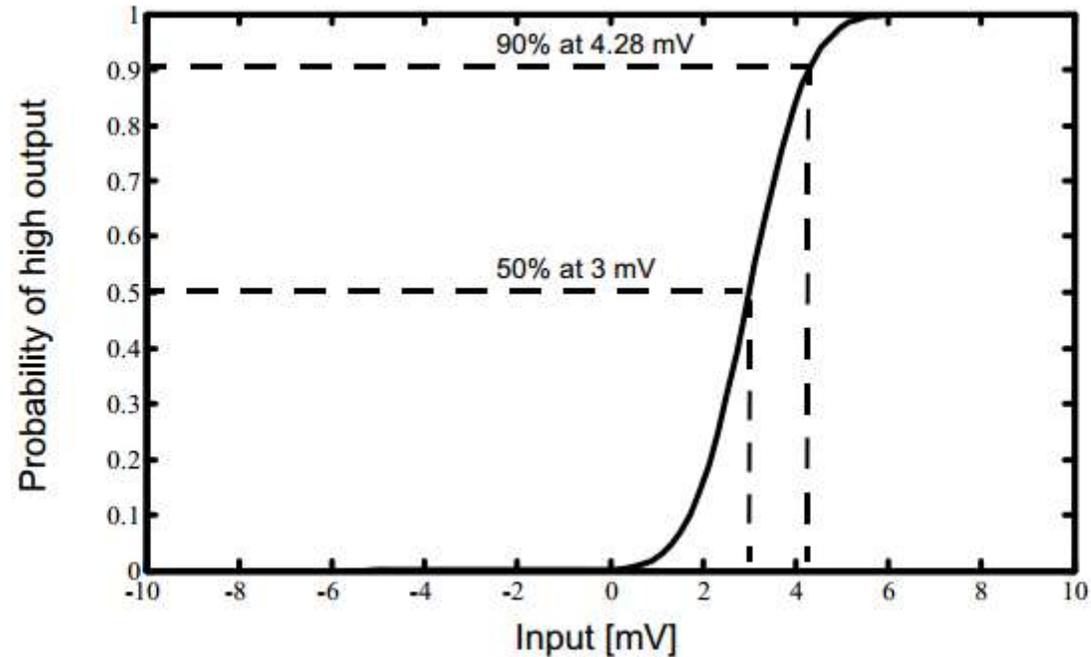
# Cumulative distribution function (CDF) The comparator issue using S-curve



Probability of a high output logic level with varying input level for a particular comparator

The 90% confidence interval for

A normal distribution is at **1.3** (or **1.2816**) times its standard deviation (rms)

In this example 90% correspond to 4.28mV; hence the rms input noise will be

$(4.28\text{mV} - 3\text{mV})/1.2816 = 1\text{mV rms}$

# Cumulative Distribution Function

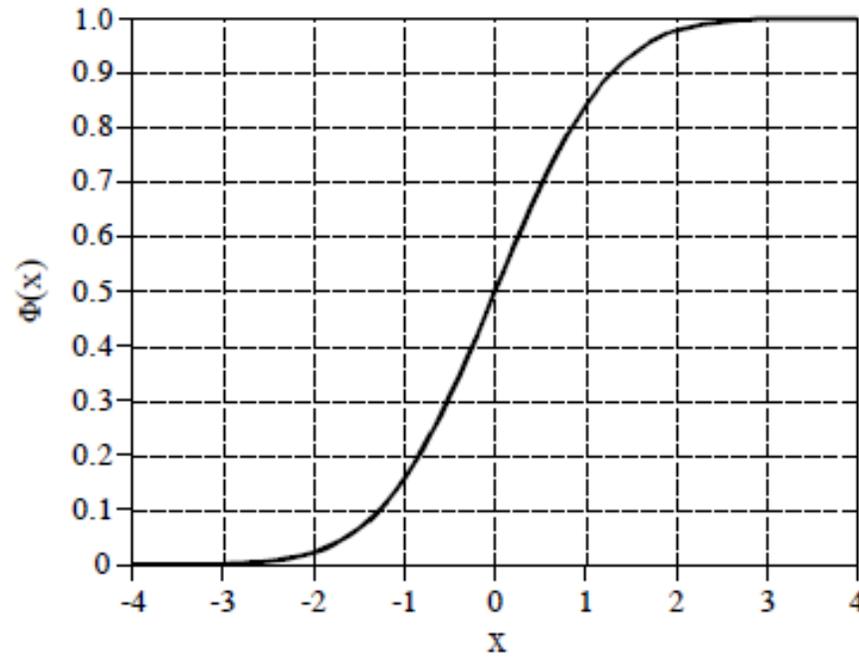



FIGURE 2-9 & TABLE 2-5  
 $\Phi(x)$ , the cumulative distribution function of the normal distribution (mean = 0, standard deviation = 1). These values are calculated by numerically integrating the normal distribution shown in Fig. 2-8b. In words,  $\Phi(x)$  is the probability that the value of a normally distributed signal, at some randomly chosen time, will be less than  $x$ . In this table, the value of  $x$  is expressed in units of standard deviations referenced to the mean.

x	$\Phi(x)$	x	$\Phi(x)$
-3.4	.0003	0.0	.5000
-3.3	.0005	0.1	.5398
-3.2	.0007	0.2	.5793
-3.1	.0010	0.3	.6179
-3.0	.0013	0.4	.6554
-2.9	.0019	0.5	.6915
-2.8	.0026	0.6	.7257
-2.7	.0035	0.7	.7580
-2.6	.0047	0.8	.7881
-2.5	.0062	0.9	.8159
-2.4	.0082	1.0	.8413
-2.3	.0107	1.1	.8643
-2.2	.0139	1.2	.8849
-2.1	.0179	1.3	.9032
-2.0	.0228	1.4	.9192
-1.9	.0287	1.5	.9332
-1.8	.0359	1.6	.9452
-1.7	.0446	1.7	.9554
-1.6	.0548	1.8	.9641
-1.5	.0668	1.9	.9713
-1.4	.0808	2.0	.9772
-1.3	.0968	2.1	.9821
-1.2	.1151	2.2	.9861
-1.1	.1357	2.3	.9893
-1.0	.1587	2.4	.9918
-0.9	.1841	2.5	.9938
-0.8	.2119	2.6	.9953
-0.7	.2420	2.7	.9965
-0.6	.2743	2.8	.9974
-0.5	.3085	2.9	.9981
-0.4	.3446	3.0	.9987
-0.3	.3821	3.1	.9990
-0.2	.4207	3.2	.9993
-0.1	.4602	3.3	.9995
0.0	.5000	3.4	.9997

# Cumulative Distribution Function (CDF)
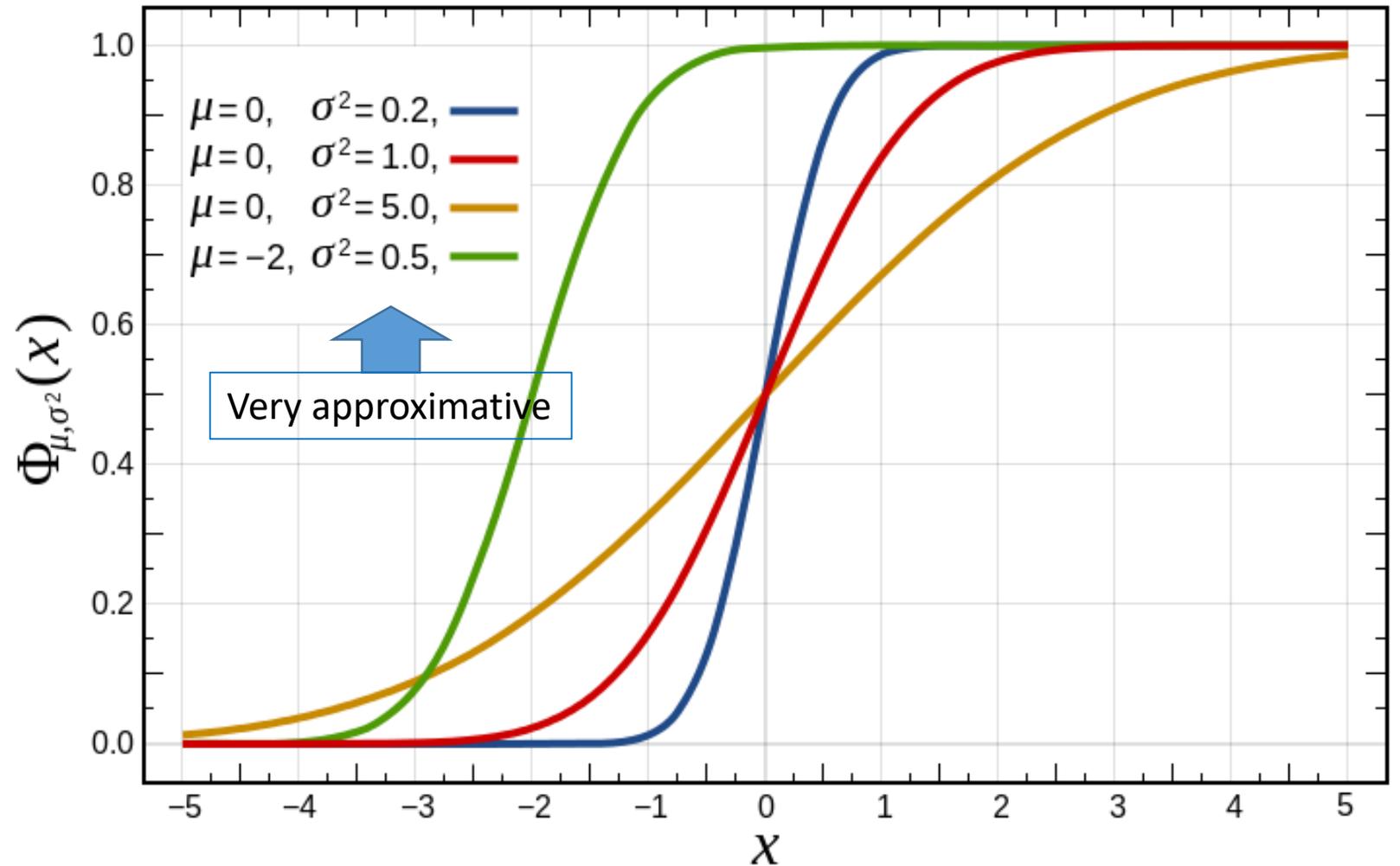
## The comparator issue using S-curve

The mean value  $\mu$   
could correspond to:  
The Vth  $\pm$  offset



*EXO: Can you calculate a more accurate value using 90% ->1.3*