

# RF Systems I



H. Damerau  
CERN



**Introduction to Accelerator Physics**

3 October 2023



## **Copyright statement and speaker's release for video publishing**

The author consents to the photographic, audio and video recording of this lecture at the CERN Accelerator School. The term “lecture” includes any material incorporated therein including but not limited to text, images and references.

The author hereby grants CERN a royalty-free license to use his image and name as well as the recordings mentioned above, in order to post them on the CAS website.

The material is used for the sole purpose of illustration for teaching or scientific research. The author hereby confirms that to his best knowledge the content of the lecture does not infringe the copyright, intellectual property or privacy rights of any third party. The author has cited and credited any third-party contribution in accordance with applicable professional standards and legislation in matters of attribution.

# Outline

- **Introduction**
- **Choice of parameters**
  - Frequency and voltage
- **RF cavity parameters**
  - Shunt impedance, beam loading, power coupling
- **Power amplifiers**
  - Tube or solid state
  - Local feedbacks
- **Longitudinal beam control system**
  - Building blocks: RF source and receiver
  - Phase, radial and synchronization loops
- **Summary**


# Introduction

# Introduction

- The **radiofrequency (RF)** system transforms a string of magnets into an **accelerator**
- Cavity most is the most visible part of an RF system
  - On top of the RF system **food chain**
  - Interacts directly with beam

→ What is below?

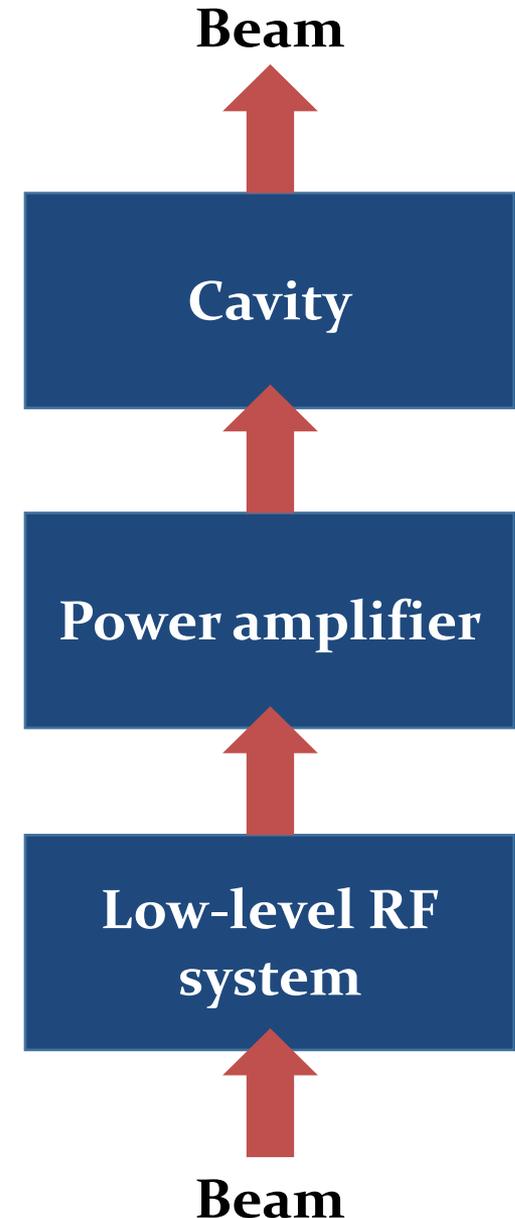→ How are RF signals generated which make the beam feel comfortable?




# Frequency and wavelength ranges




**PS longitudinal damper**



**PS main RF system**

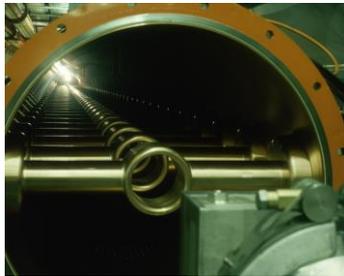

**SPS 200 MHz**

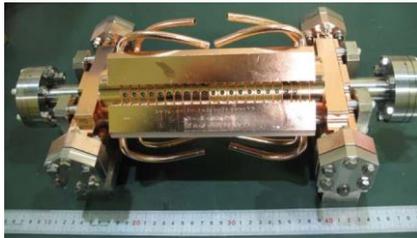

**CLIC 12 GHz**



**Long wave**

**Medium/  
short wave**




**VHF**



**Microwave  
links**



# Amplitude ranges

Signals from beam pick-ups

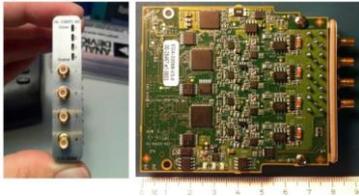

LLRF systems

Low/Medium energy hadron RF

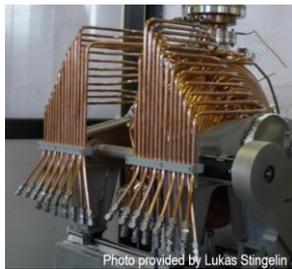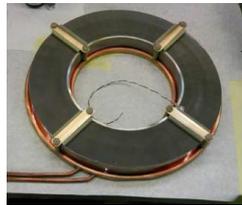

SLS



LHC: 16 MV



LEP: 3.6 GV total

1  $\mu$ V

1 mV



1 V

1 kV

1 MV



1 GV

Cooled hadron beams (ELENA)

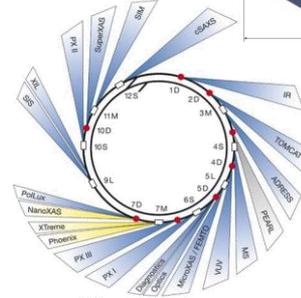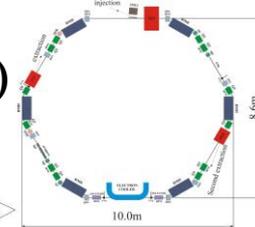

LHC



Electron light sources

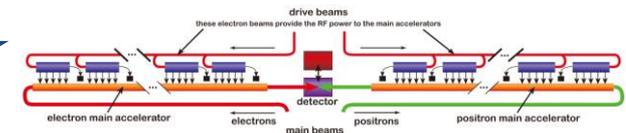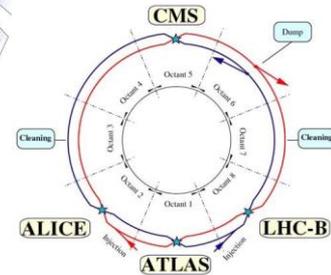

ILC and CLIC: several TV

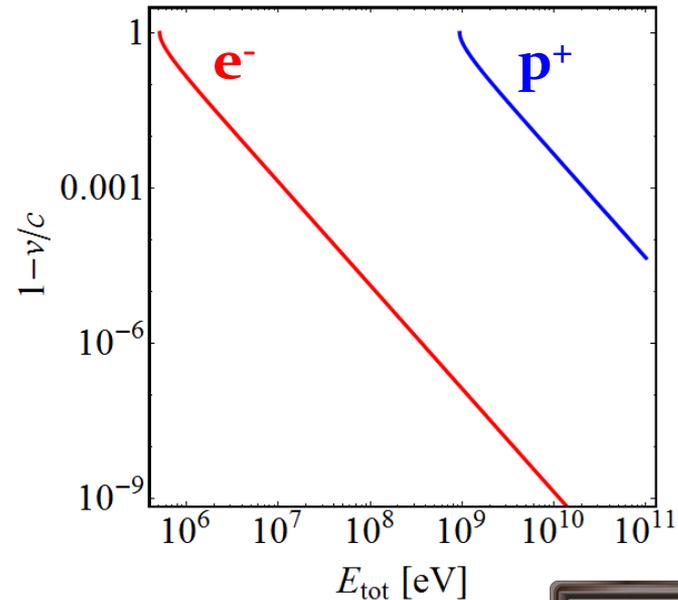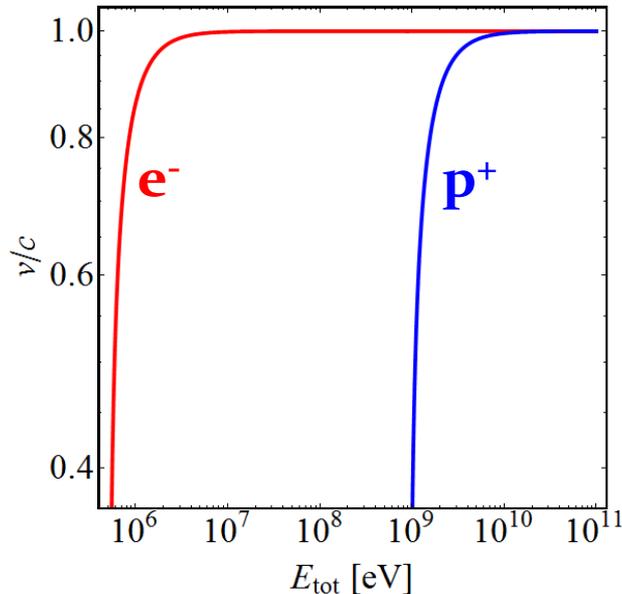
# Particle velocity

- Particle velocity depends on its type:  $\beta = v/c = \sqrt{1 - (E_0/E)^2}$




- Old television set (30 kV): **Electrons** at 30% of  $c_0$   
**Protons** just at 0.7%
- Small synchrotron (500 MeV): **Electrons** at 99.99995%  
**Protons** at 75.8%

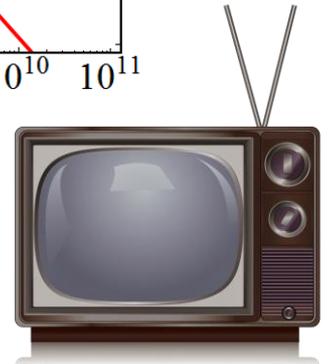→ Most electron accelerators at 'fixed' frequency



# Parameter choices

# RF system for high-energy accelerators

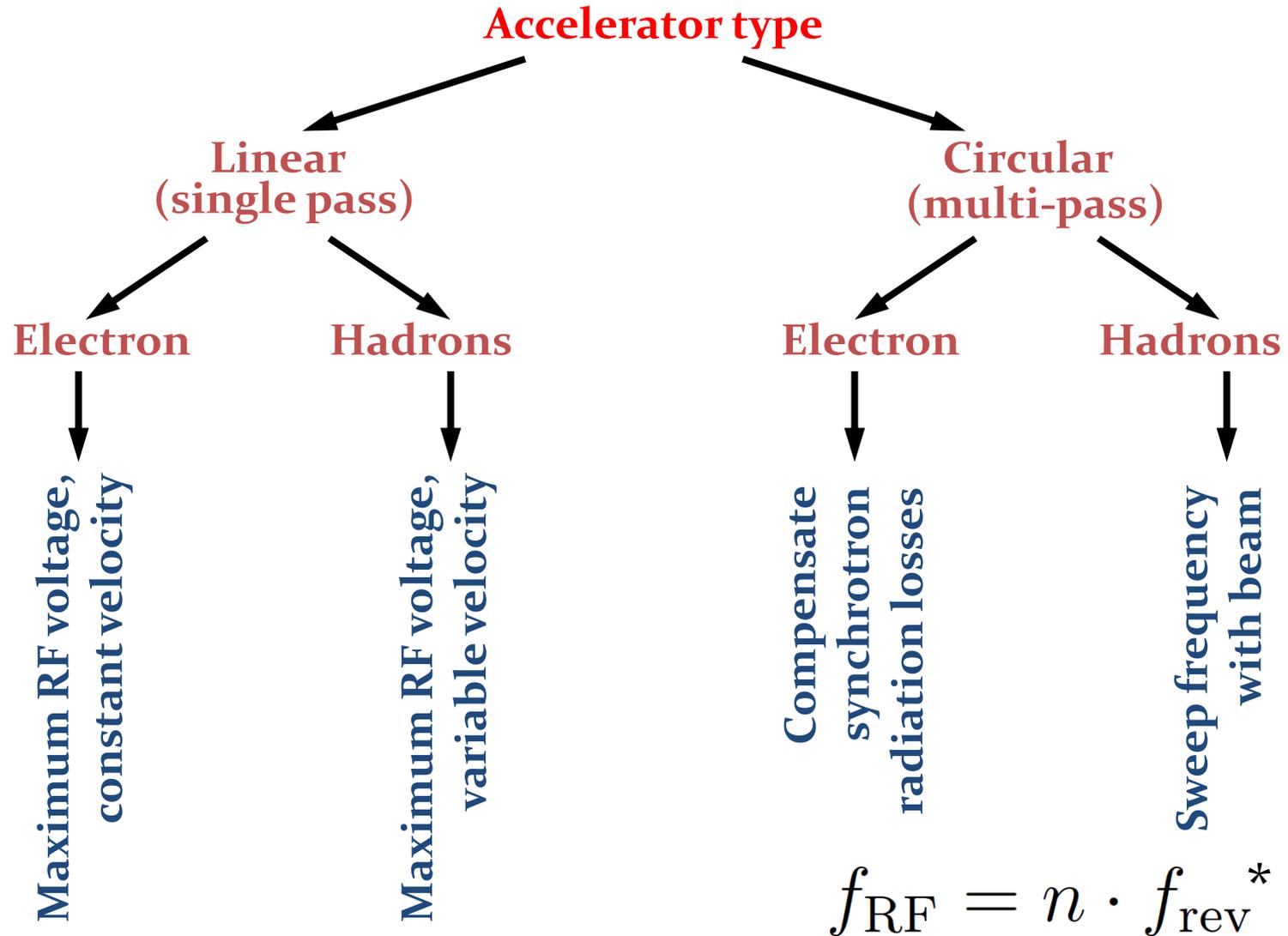

\*Exceptions (rare) exist

# Choice of frequency (range)

# Why choose a **low** RF frequency?

| Advantages   | Disadvantages  |
|--|--|
| <ul style="list-style-type: none"> <li>• Large beam aperture</li> <li>• Long RF buckets, large acceptance</li> <li>• <b>Wide-band or wide range tunable cavities</b> possible</li> <li>• Power amplification and transmission straightforward</li> </ul> | <ul style="list-style-type: none"> <li>• <b>Bulky cavities, size scales <math>\propto 1/f</math>, volume <math>\propto 1/f^3</math></b></li> <li>• Lossy material to downsize cavities</li> <li>• Moderate or low acceleration gradient</li> <li>• Short particle bunches difficult to generate</li> </ul> |

RF frequencies **below**  
~200 MHz for



- **Some hadron linear accelerators**
- **Cyclotrons**
- **Low- and medium energy hadron synchrotrons**

# Why choose a **high** RF frequency?

| Advantages   | Disadvantages   |
|--|---|
| <ul style="list-style-type: none"> <li>• Cavity size scales <math>\propto 1/f</math>, volume <math>\propto 1/f^3</math></li> <li>• Break down voltage increases</li> <li>• High gradient per length</li> <li>• Particle bunches are short</li> </ul> | <ul style="list-style-type: none"> <li>• Maximum beam available aperture scales <math>\propto 1/f</math></li> <li>• <b>No technology for wide-band or tunable</b> cavities</li> <li>• Power amplifiers more difficult</li> <li>• Power transmission losses</li> </ul> |


RF frequencies **above**  
~**200 MHz** used for



- **Linear accelerators**
- **Electron storage rings**
- **High energy hadron storage rings**

# Limits to maximum gradient

- Surface electric field in vacuum

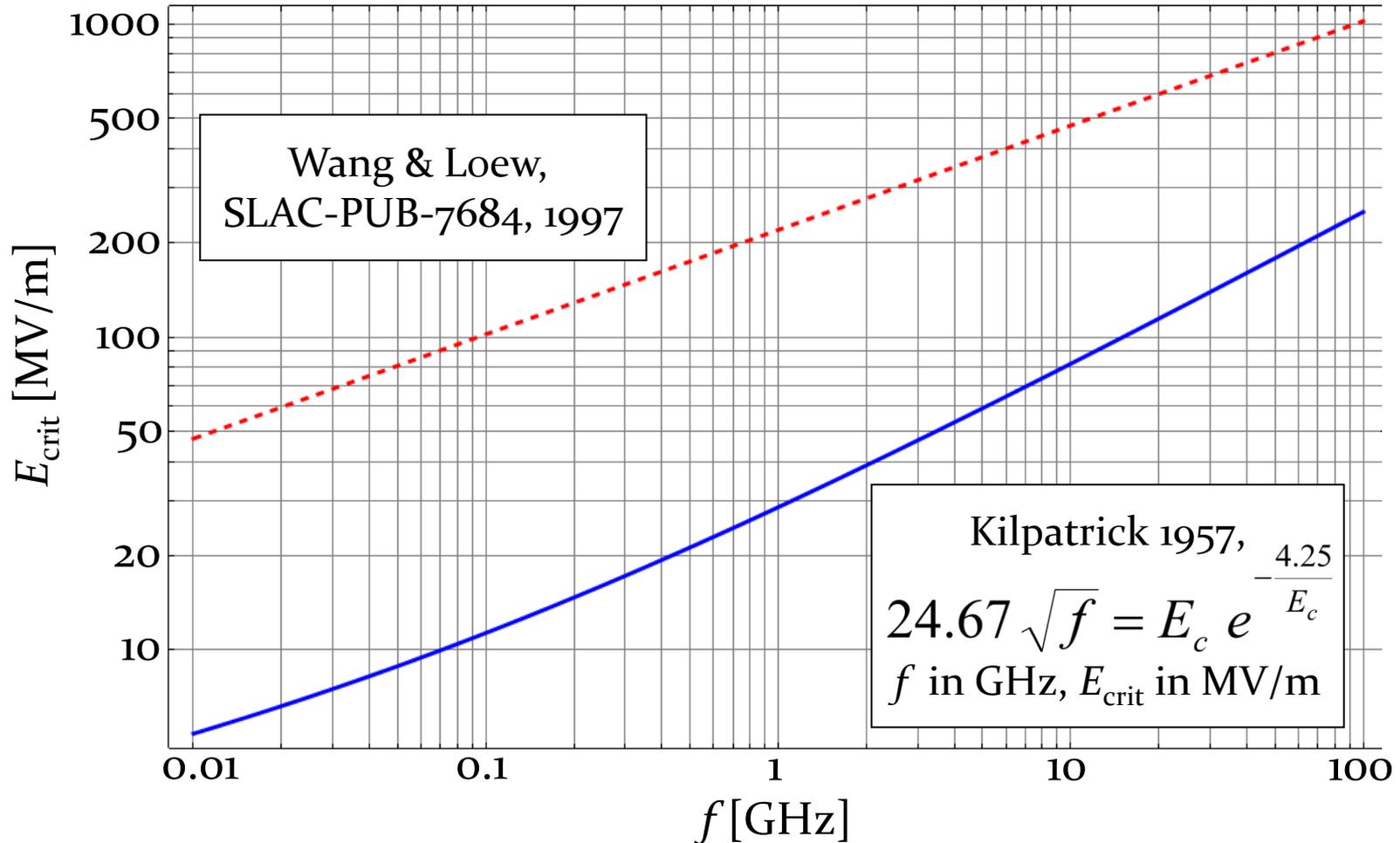

→ High frequencies preferred for large gradient

# Some standard frequencies

If exact RF frequency not critical, choose standard value

| Accelerator   | Frequency         |
|---|-------------------|
| Hadron synchrotrons (PSB, PS, JPARC RCS, MR)          | <10 MHz           |
| Hadron accelerators and storage rings (RHIC, SPS)     | ~200 MHz          |
| Electron storage rings (LEP, ESRF, Soleil)            | 352 MHz           |
| Electron storage rings (DORIS, BESSY, SLS,...)        | 499.6...499.8 MHz |
| Superconducting electron linacs and FELs (X-FEL, ILC) | 1300 MHz          |
| Normal conducting electron linacs (SLAC)              | 2856 MHz          |
| High-gradient electron linac (CLIC)                   | 11.99 GHz         |

- **Off-the-shelf RF components easily available in frequency ranges used by industry**
- **Exchange of developments and equipment amongst research laboratories**


# RF voltage

# Minimum voltage requirement

- RF system expected to provide given energy gain

$$qV = \Delta E$$

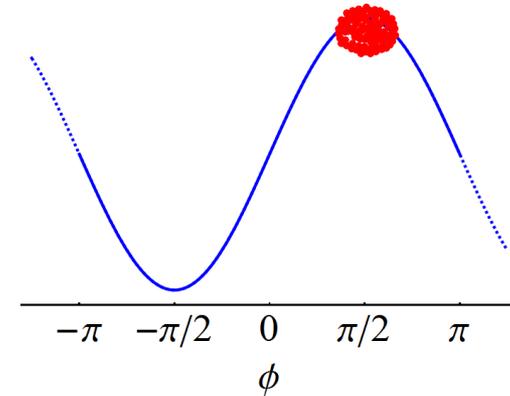
- On-crest acceleration
- Used in some linear accelerators
- **Insufficient in a circular accelerator**



- More voltage provided to avoid on-crest acceleration



$$qV > \Delta E \rightarrow qV \sin(\phi_S) = \Delta E$$

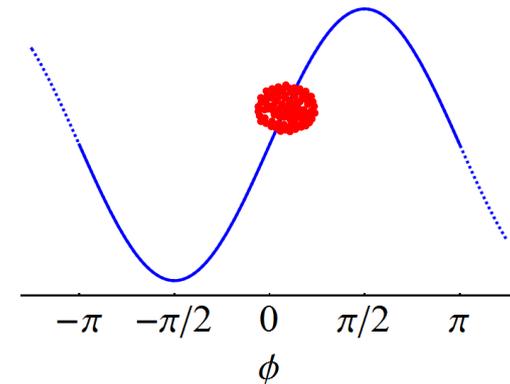- Off-crest acceleration
- Needed for circular accelerator
- **Higher voltage for given energy gain**


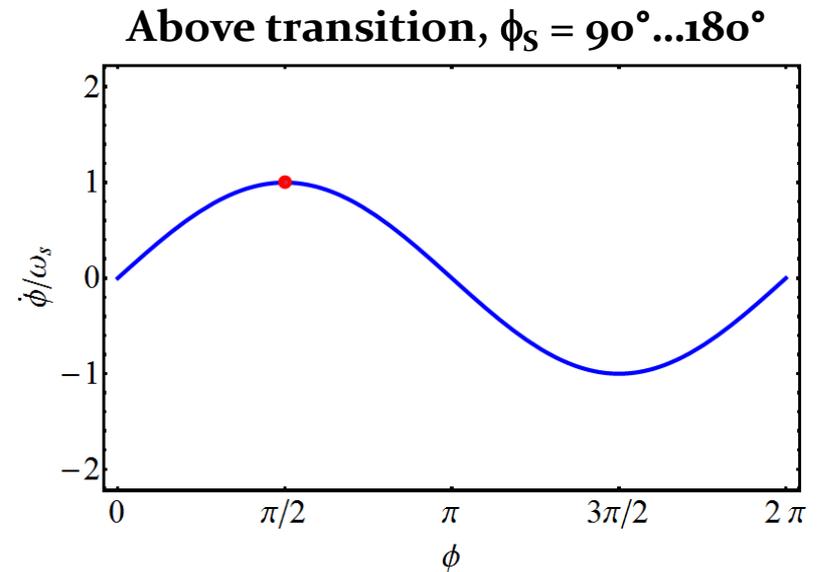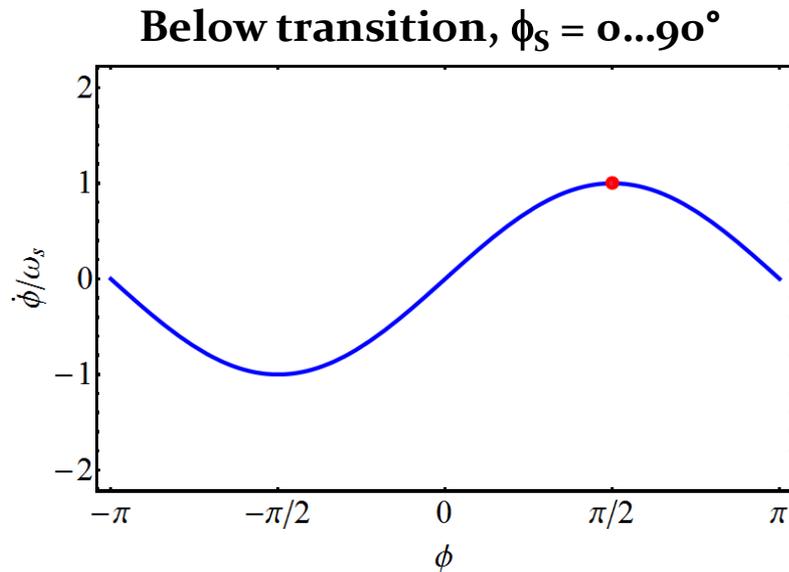
# Bucket area dependence on stable phase

- In a circular accelerator the area in energy-time phase space (bucket area) depends on the stable phase



- Typical synchronous phase with respect to  $0^\circ$  or  $180^\circ$ 
  - Hadron accelerators:  $< 40^\circ$
  - Electron storage rings:  $\sim 20^\circ$

# Minimum voltage requirement (circular)

The RF system must compensate

1. Energy gain per turn due to changing magnetic field

$$F_Z = F_L \quad \rightarrow \quad \frac{p}{q} = \rho B \quad \rightarrow \quad \dot{p} = q\rho\dot{B}$$

$$\dot{p} = \frac{\Delta p}{\Delta t} = \frac{m_0 c^2 \beta}{2\pi R} (\beta \Delta \gamma + \gamma \Delta \beta) = \frac{\Delta E_{\text{turn}}}{2\pi R}$$

$$\Delta E_{\text{turn}} = 2\pi q \rho R \dot{B}$$


2. Energy loss, e.g., due to synchrotron radiation (electrons)

$$\Delta E_{\text{turn}} = \frac{e^2}{3\epsilon_0 (m_0 c^2)^4} \frac{E^4}{\rho}$$


$$\Delta E_{\text{turn}}[\text{keV}] = 88.5 \cdot \frac{E^4[\text{GeV}]^4}{\rho[\text{m}]} \quad \Delta P_{\text{loss}}[\text{kW}] = 88.5 \cdot \frac{E^4[\text{GeV}]^4}{\rho[\text{m}]} \cdot I_B[\text{A}]$$

$\rightarrow (m_p/m_e)^4 = 1836^4 \sim 1.1 \cdot 10^{13}$  times less for protons

# RF system overview

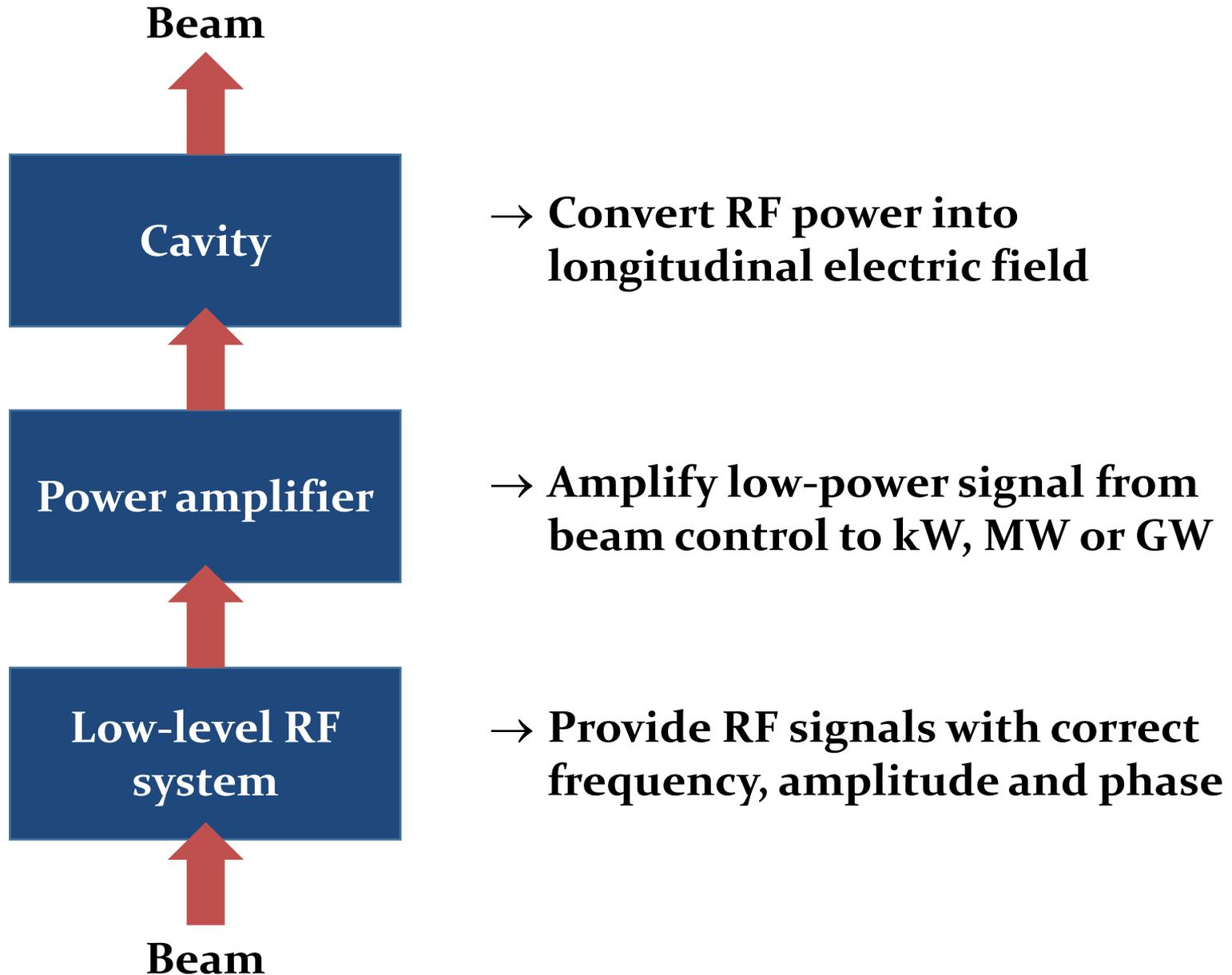


# RF system overview

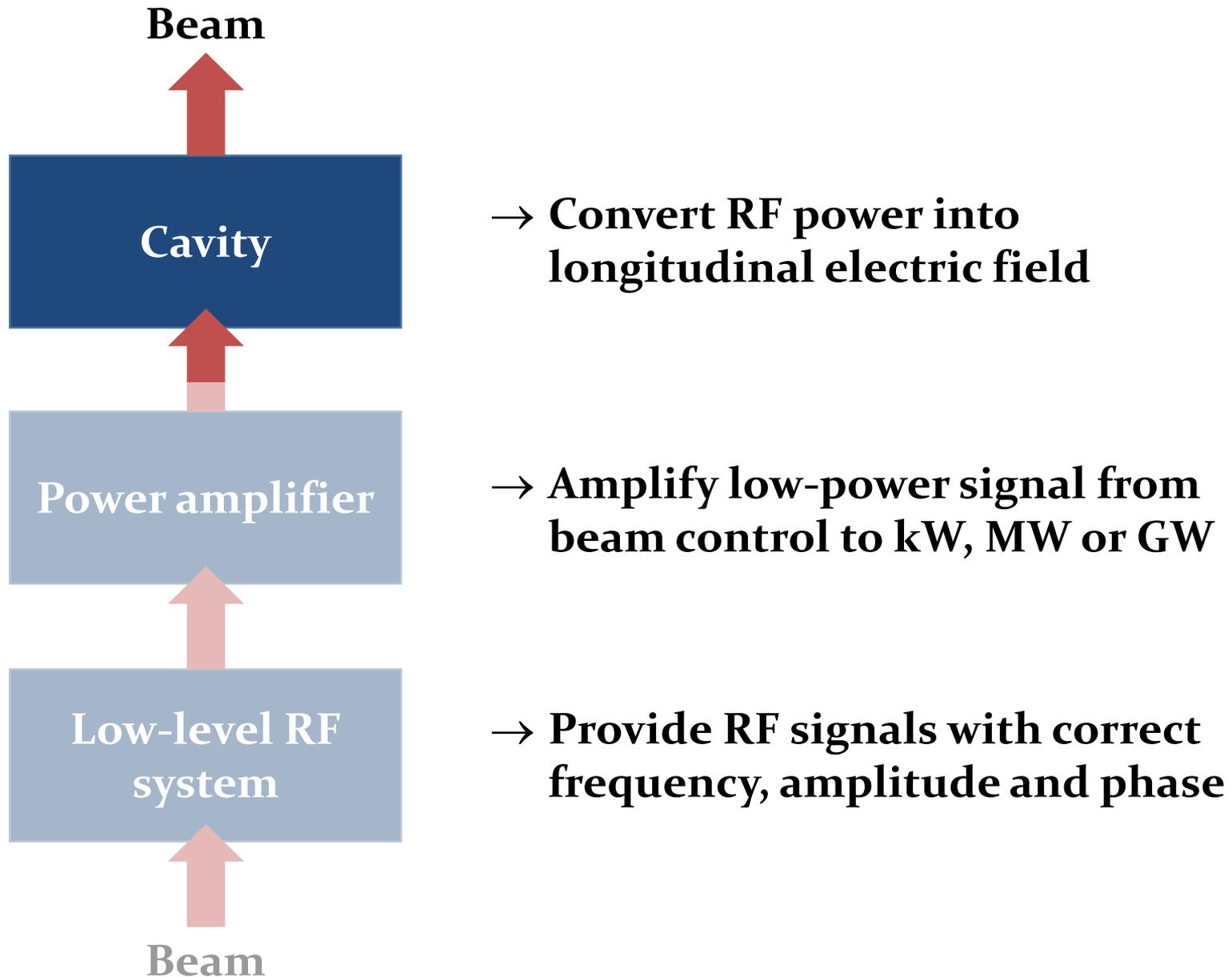

# RF cavity
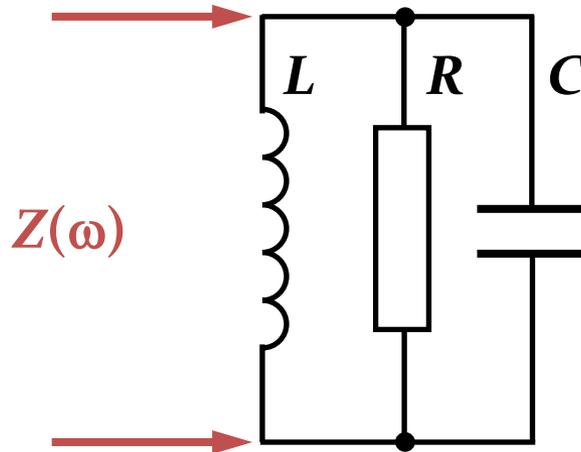
# Cavity parameters

- The resonance of a cavity can be understood as simple parallel resonant circuit described by  $R, L, C$



$$\frac{1}{Z(\omega)} = \frac{1}{R} + \frac{1}{i\omega L} + i\omega C$$

with  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$Q = \omega_0 \frac{\text{Stored energy}}{\text{Average power loss}} = \frac{\omega_0 E}{P}$$


$$E = \frac{1}{2} CV^2 = \frac{1}{2} LI^2$$

$$P = \frac{1}{2} \frac{U^2}{R} = \frac{1}{2} I^2 R$$

$$Q = \omega_0 RC = \frac{R}{\omega_0 L}$$
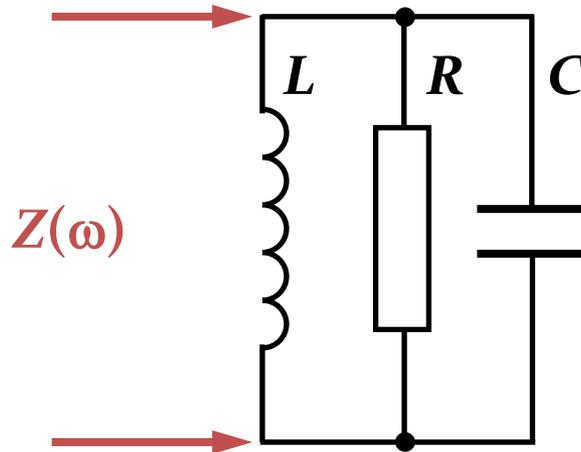
# Cavity parameters

- The resonance of a cavity can be understood as simple parallel resonant circuit described by  $R, L, C$



$$\frac{1}{Z(\omega)} = \frac{1}{R} + \frac{1}{i\omega L} + i\omega C$$



with  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$Q = \omega_0 RC = \frac{R}{\omega_0 L} \quad Z(\omega) = \frac{R}{1 + iQ \left( \frac{\omega^2 - \omega_0^2}{\omega\omega_0} \right)} \approx \frac{R}{1 + 2iQ \frac{\Delta\omega}{\omega_0}}$$

- Resonant circuit can also be described by  $R, R/Q, \omega_0$  or any other set of three parameters
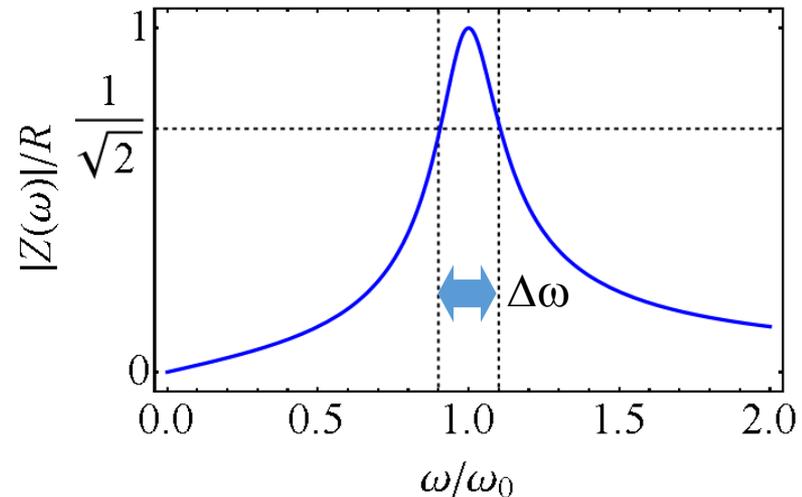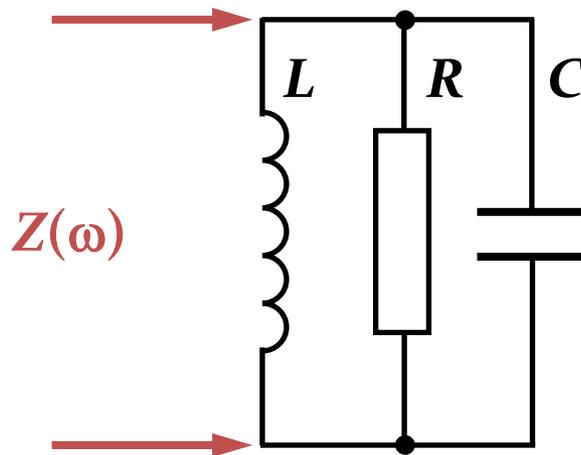
# Cavity parameters

- The resonance of a cavity can be understood as simple parallel resonant circuit described by  $R$ ,  $L$ ,  $C$



$$Q = \omega_0 RC = \frac{R}{\omega_0 L} \quad Z(\omega) = \frac{R}{1 + iQ \left( \frac{\omega^2 - \omega_0^2}{\omega \omega_0} \right)} \approx \frac{R}{1 + 2iQ \frac{\Delta\omega}{\omega_0}}$$



- Resonant circuit can also be described by  $R$ ,  $R/Q$ ,  $\omega_0$  or any other set of three parameters

# Cavity parameters

- Most common choice by cavity designers  $\omega_o$ ,  $R$ ,  $R/Q$  – why?
- **Resonance frequency,  $\omega_o$** 
  - Exactly defined for given application, e.g.  $hf_{\text{rev}}$
- **Shunt impedance,  $R$** 
  - Power required to produce a given voltage **without beam**
- **“R-upon-Q”,  $R/Q$** 
  - Defined only by the cavity geometry
  - Criterion to optimize a geometry
  - Detuning with beam proportional to  $R/Q$
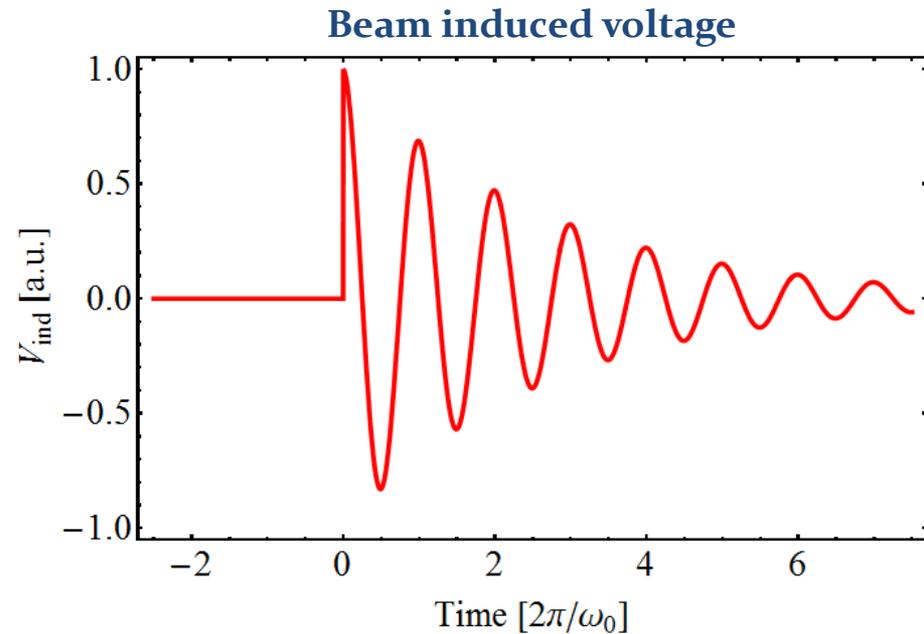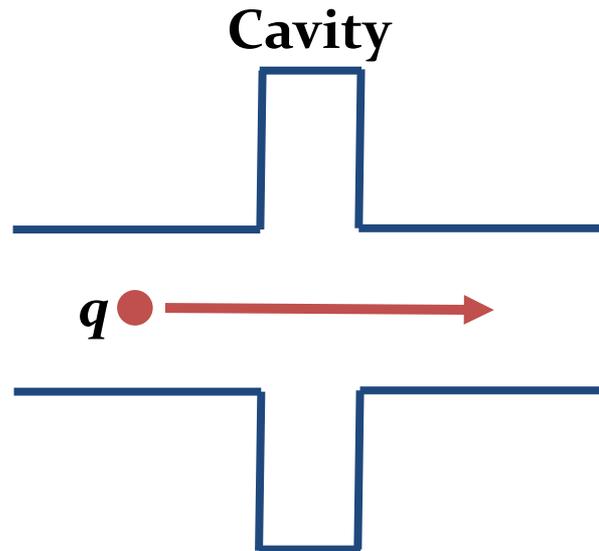
# Why R/Q?

→ Charged particle experiences cavity gap as capacitor



$$q = V_{\text{ind}} C$$


$$Q = \omega_0 RC \quad \rightarrow \quad \frac{1}{C} = \left( \frac{R}{Q} \right) \omega_0$$

$$V_{\text{ind}} = \frac{q}{C} \propto \frac{R}{Q}$$

→ Cavity geometry with small  $R/Q$  to reduce beam loading
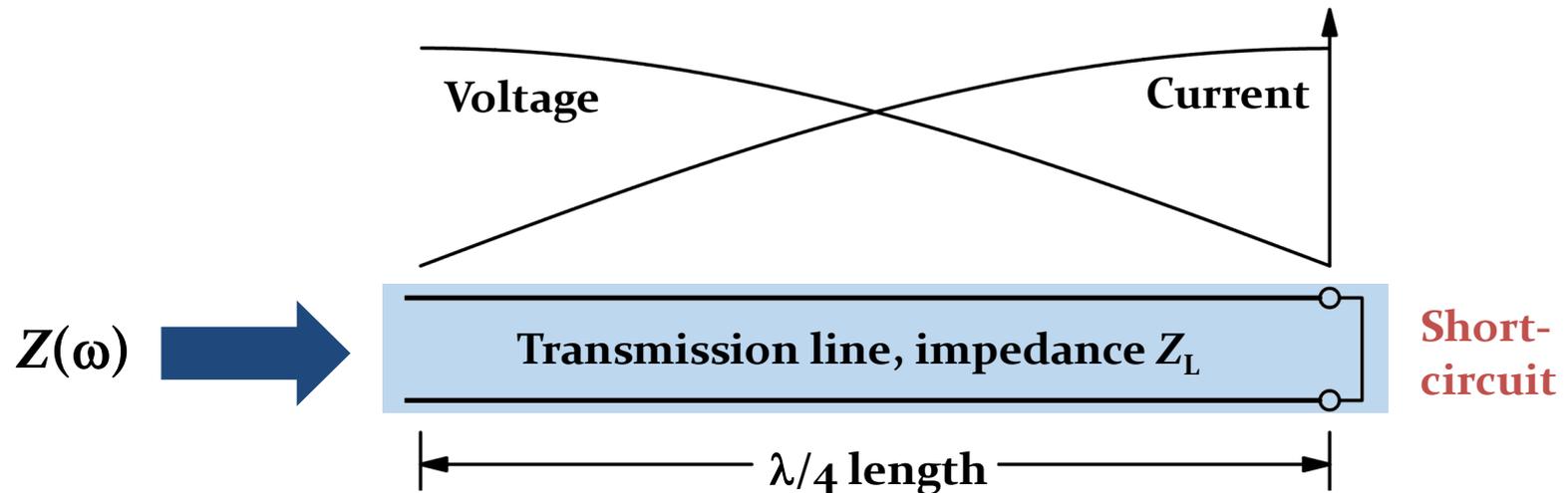
# RF cavities in low frequency range

- **RF wavelength large below ~10 MHz: >30 m**
- Would need huge cavities → too large for accelerators
- Line resonators:  **$\lambda/4$  resonator**




- Short circuit on one side
- Open end on other

- Voltage is zero
- No current but voltage

Why is this resonator so common in particle accelerators?


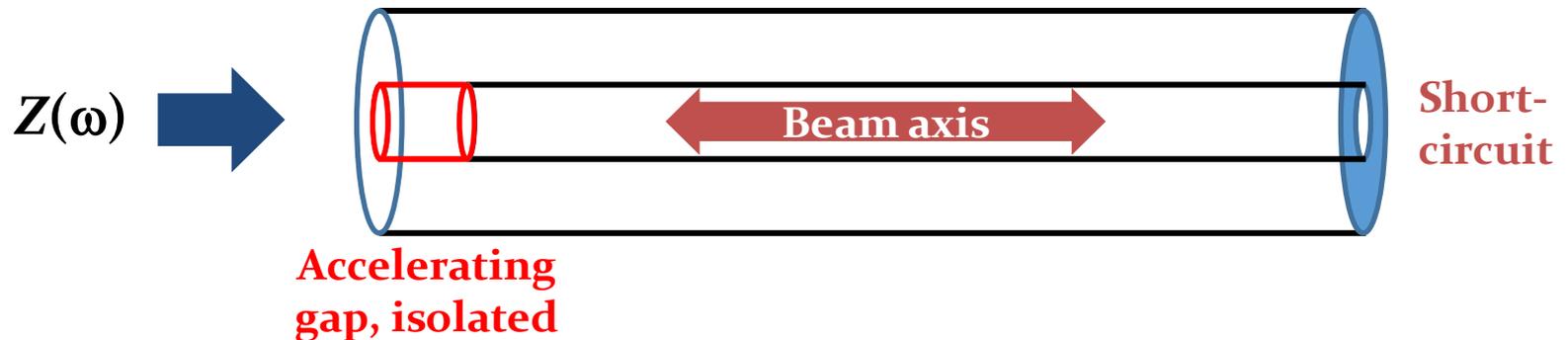
# RF cavities in low frequency range

- Coaxial structure with inner conductor as beam pipe



→ Still rather long geometry, 7.5 m at 10 MHz


→ Add capacitive or inductive shortening

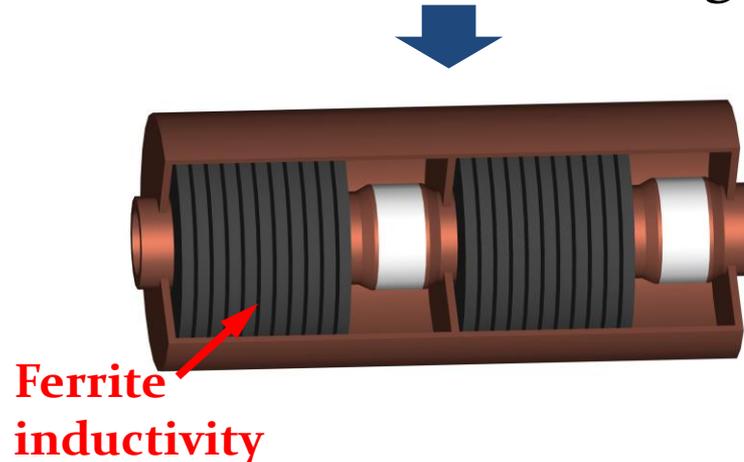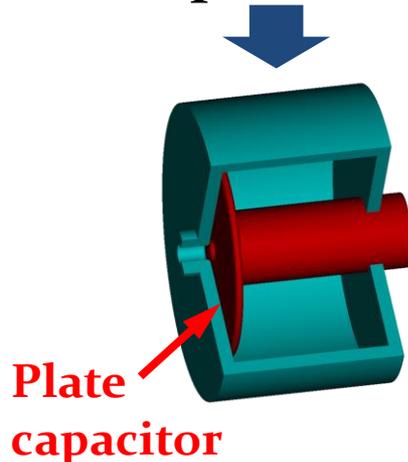


# Capacitive loading

→ Add capacitor at gap of cavity to shorten the resonator


NSLS, 52.88 MHz

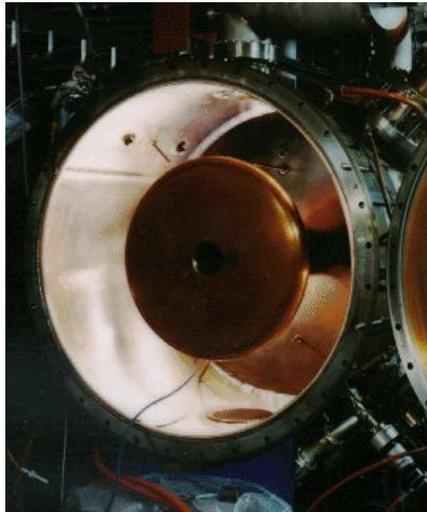


DESY PIA, 10.4 MHz, inner cond.

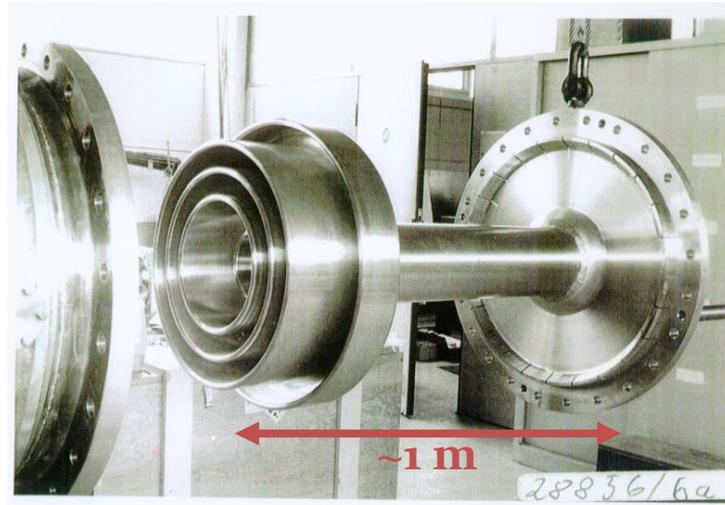

Outer cond.

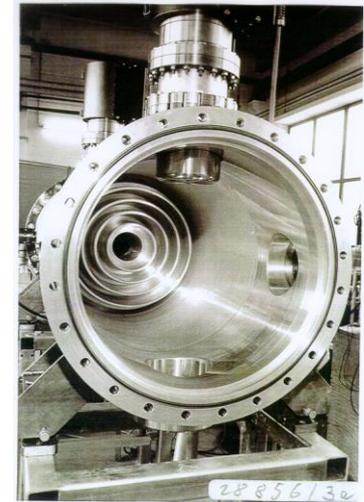

ACOL, 9.53 MHz

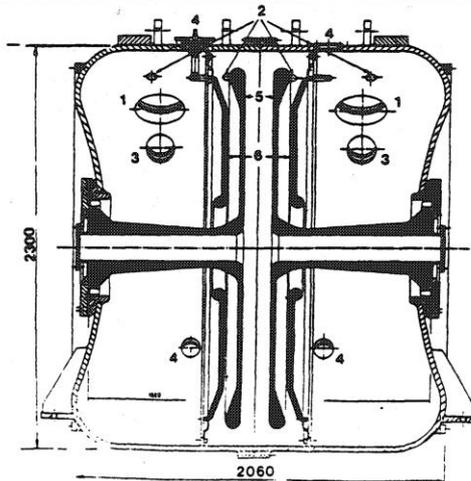


- Significantly reduces cavity size
- Fixed frequency only
- Small losses due to capacitor
- Cavity in vacuum

# Inductive loading

- Inductive loading with magnetic material shortens resonator from tens of meters to a device, **lossy though**

CERN PSB Finemet cav., 0.6-18 MHz

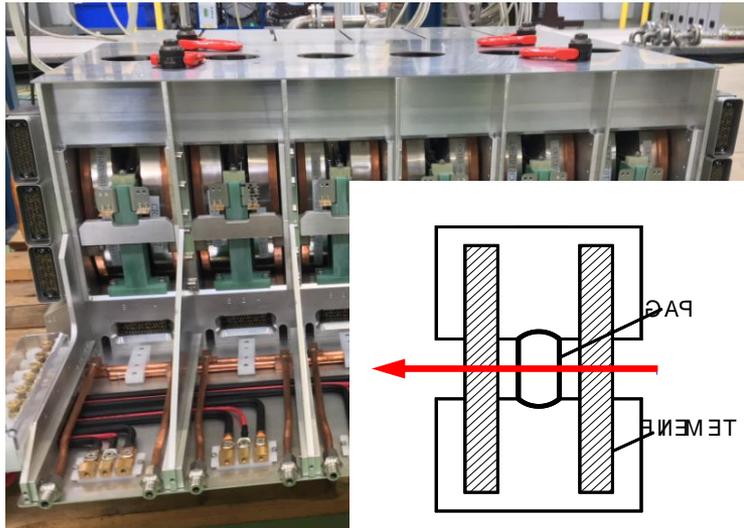

M. Paoluzzi

CERN PS, double gap, 2.8-10 MHz




- Additional advantage: permeability of ferrite can be controlled by DC bias current → **variable inductivity**
  - Cavity with programmable resonance frequency
  - Essential for hadron acceleration in low-energy accelerators
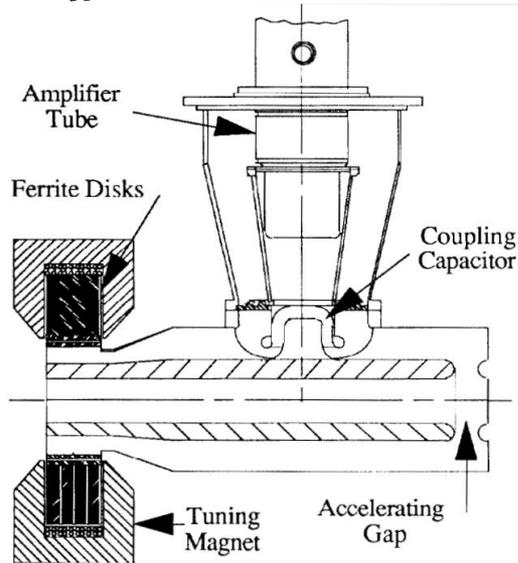
# Tunable cavities at higher frequencies


→ Remove inductive or capacitive loading

SSC Low Energy Booster,  
~47 MHz to 60 MHz



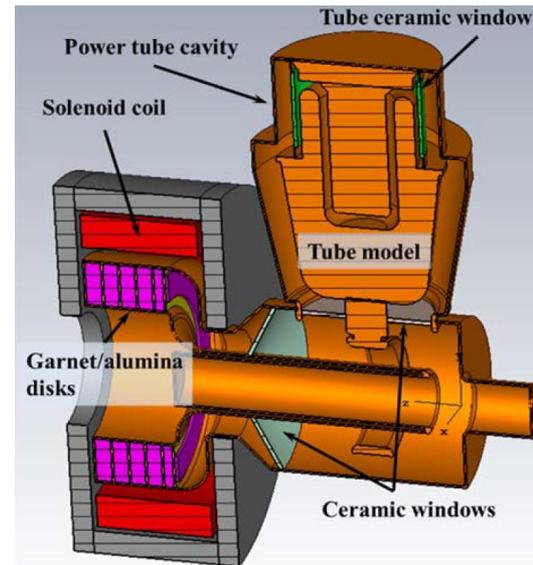C. C. Friedrichs et al., PAC91, p. 1020

FNAL Booster 2<sup>nd</sup> harmonic,  
76 MHz – 106 MHz, 100 kV



R. L. Madrak, IPAC16, p. 130


→ Upper frequency limit for cavities with large tuning range
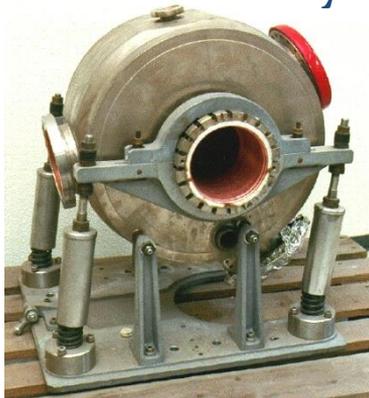
# Further increase frequency


→ Remove inner conductor from coaxial set-up




→ The resonator becomes a pill-box cavity  
DORIS cavity



Electric field,  
 $TM_{010}$ -mode

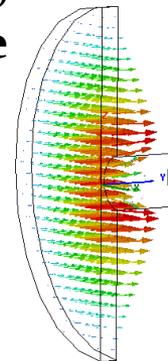

Magnetic field,  
 $TM_{010}$ -mode

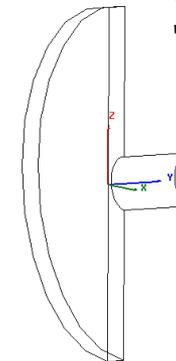


E. Jensen



→ The basis for cavity resonators
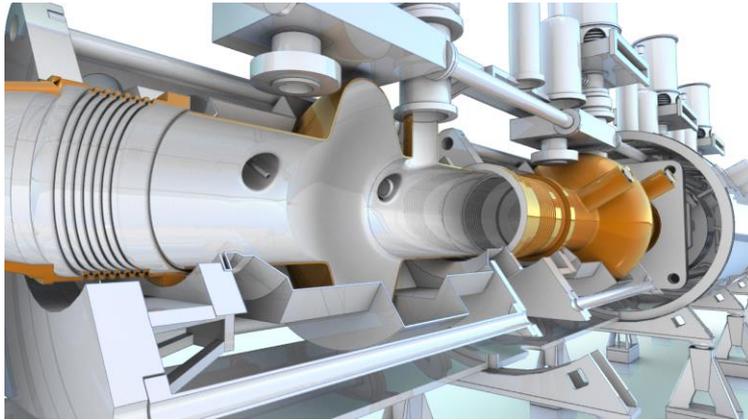
# Example: 400 MHz cavities in LHC

- Reduce beam loading in RF cavities
- Shunt impedance,  $R$ , low for small  $R/Q$  with normal conducting cavities → superconducting cavities in LHC



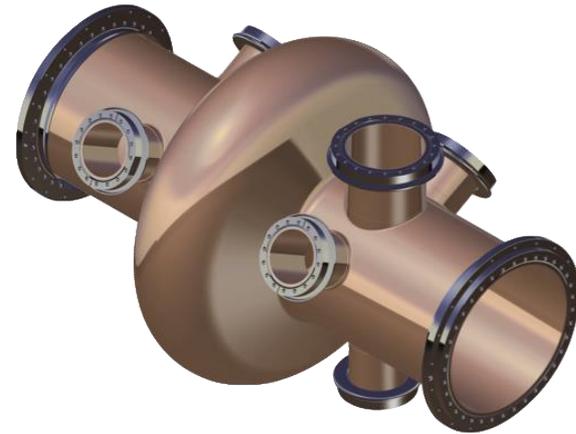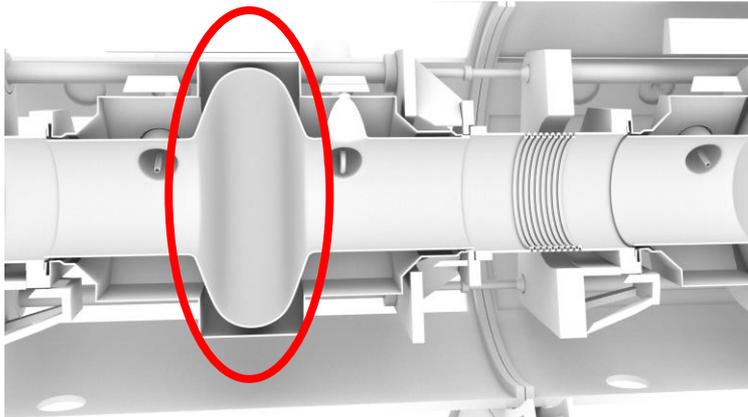Bell shape:  $R/Q \sim 44 \Omega$ , 400 MHz



→ 2×8 cavities, 5.3 MV/m

$$\frac{1}{Q} = \frac{1}{Q_{\text{cav}}} + \frac{1}{Q_{\text{ext}}}$$

$\nearrow \sim 0$


# RF cavities in linear accelerators

- Beam only passes once → **Maximize gradient**
- Many accelerating cells to best reuse RF voltage

SuperHILAC, ~70 MHz, Berkley



CLIC, 12 GHz, ~100 MV/m

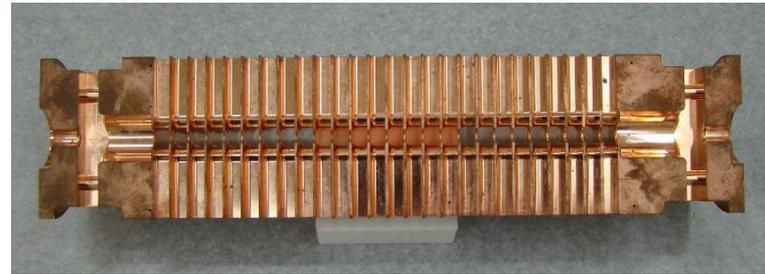


- Cavity is the **contrary to 'one size fits all'**
- **Many, many more variants**

# Coupling power into a cavity
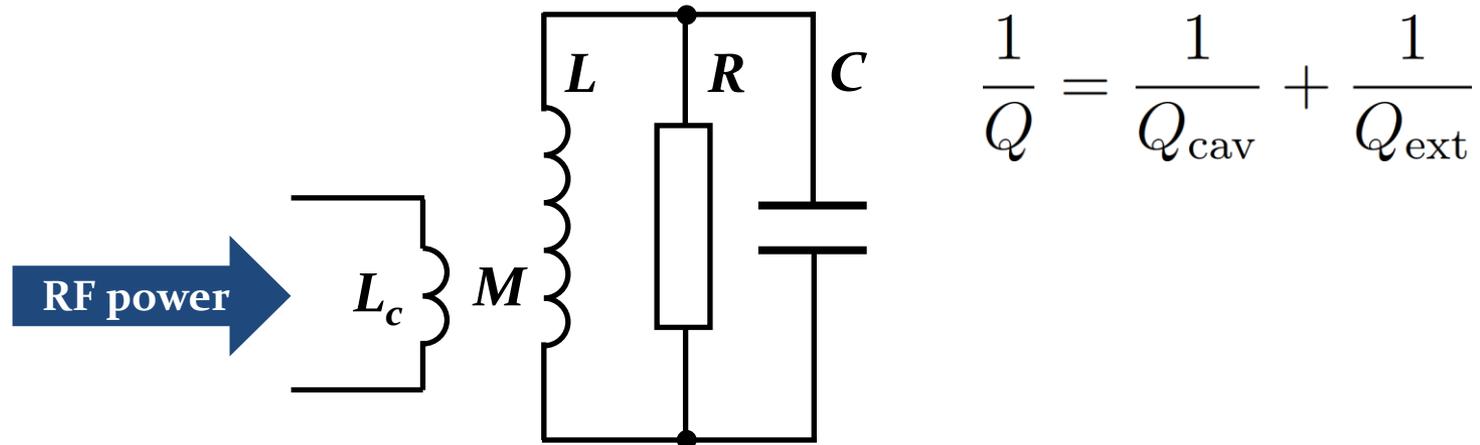
# Coupling power into a cavity

- **Attack inductivity or capacitance of resonator, or combined**



→ **Coupling loop forms transformer with resonator inductivity**



L. Stigelin


- **Main coupler  
PSI cyclotron**
- **~1 MW at 50 MHz**



A. Rodchenko
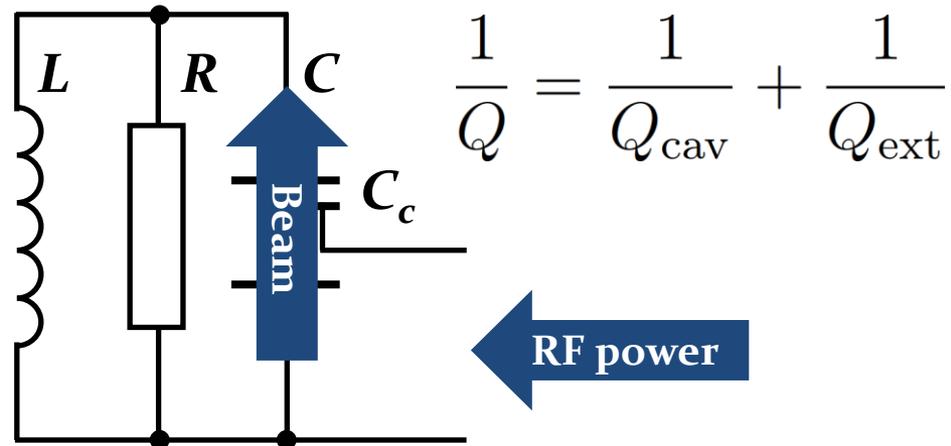
# Coupling power into a cavity

- Attack inductivity or **capacitance** of resonator, or combined



- **Capacitive divider** to gap to transform generator impedance to cavity shunt impedance
- Beam also **couple**s capacitively via the gap

Coupler of CERN PS 40 MHz



- Coupler forms one **half of** capacitor with the gap

# Capacitive (electric) coupling

- Coupling through an electric antenna


Electrical coupler to space



[https://en.wikipedia.org/wiki/Transmitter\\_Solt](https://en.wikipedia.org/wiki/Transmitter_Solt)

→ 2 MW at 540 kHz


Power coupler of LHC cavities

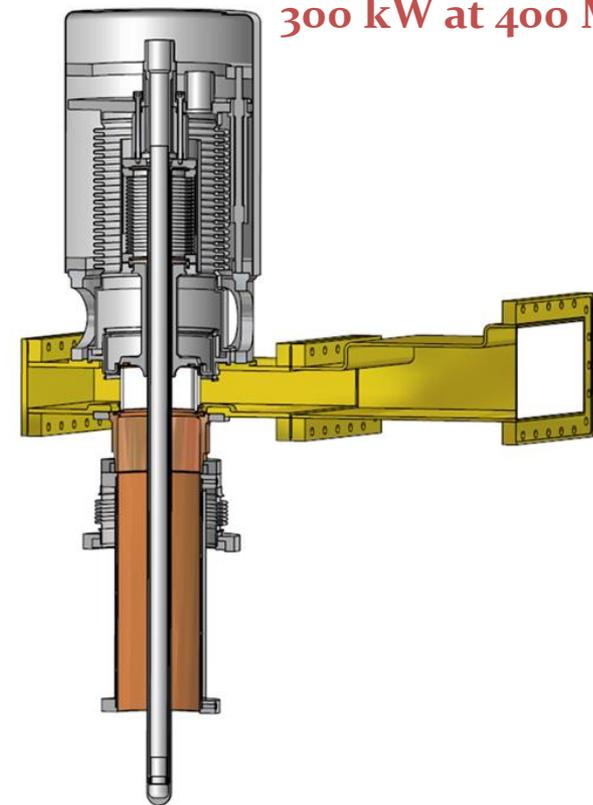

300 kW at 400 MHz

→ Coupler antenna transmits directly into the cavity


# RF system overview

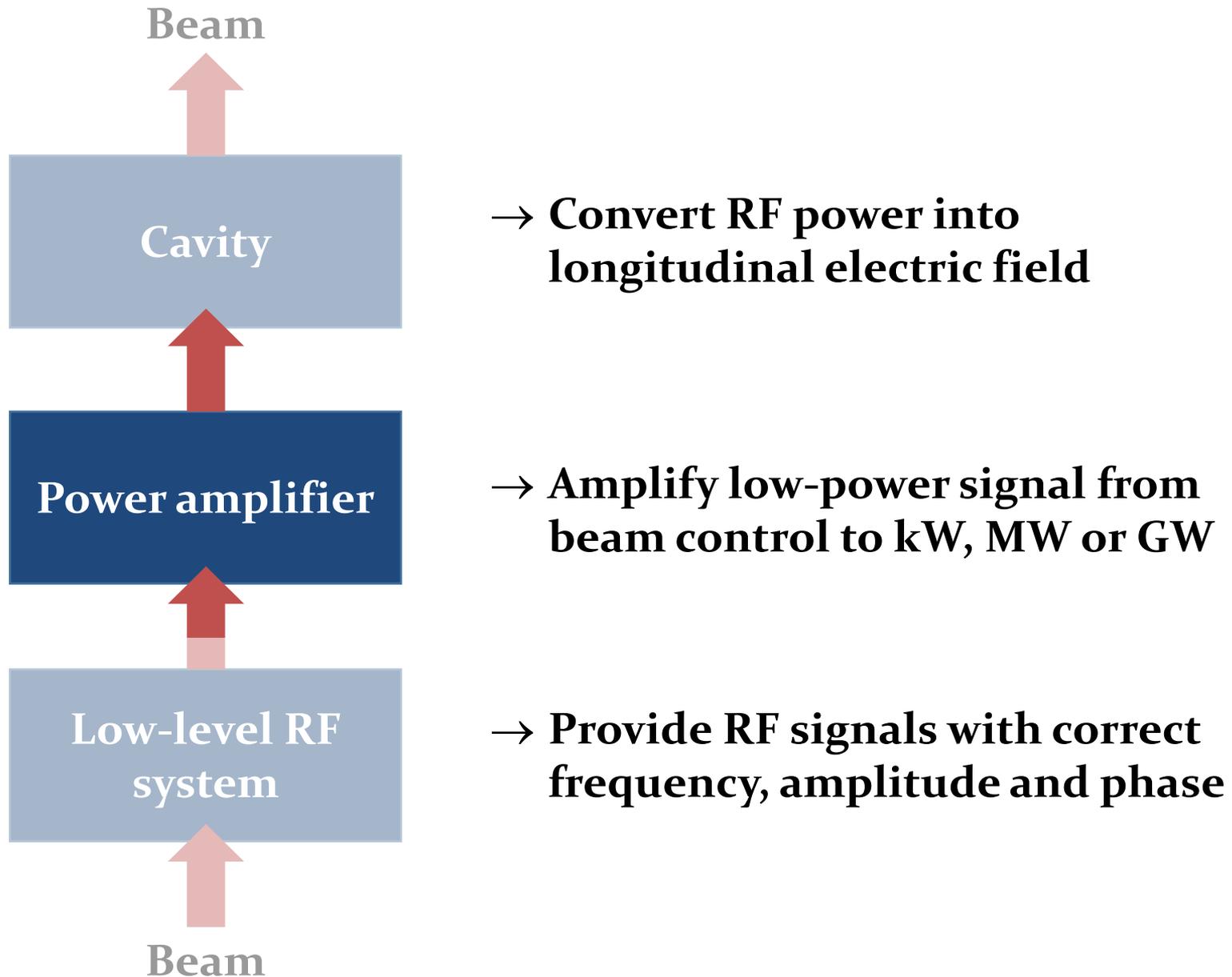

# Power amplifiers

# How much power is required?

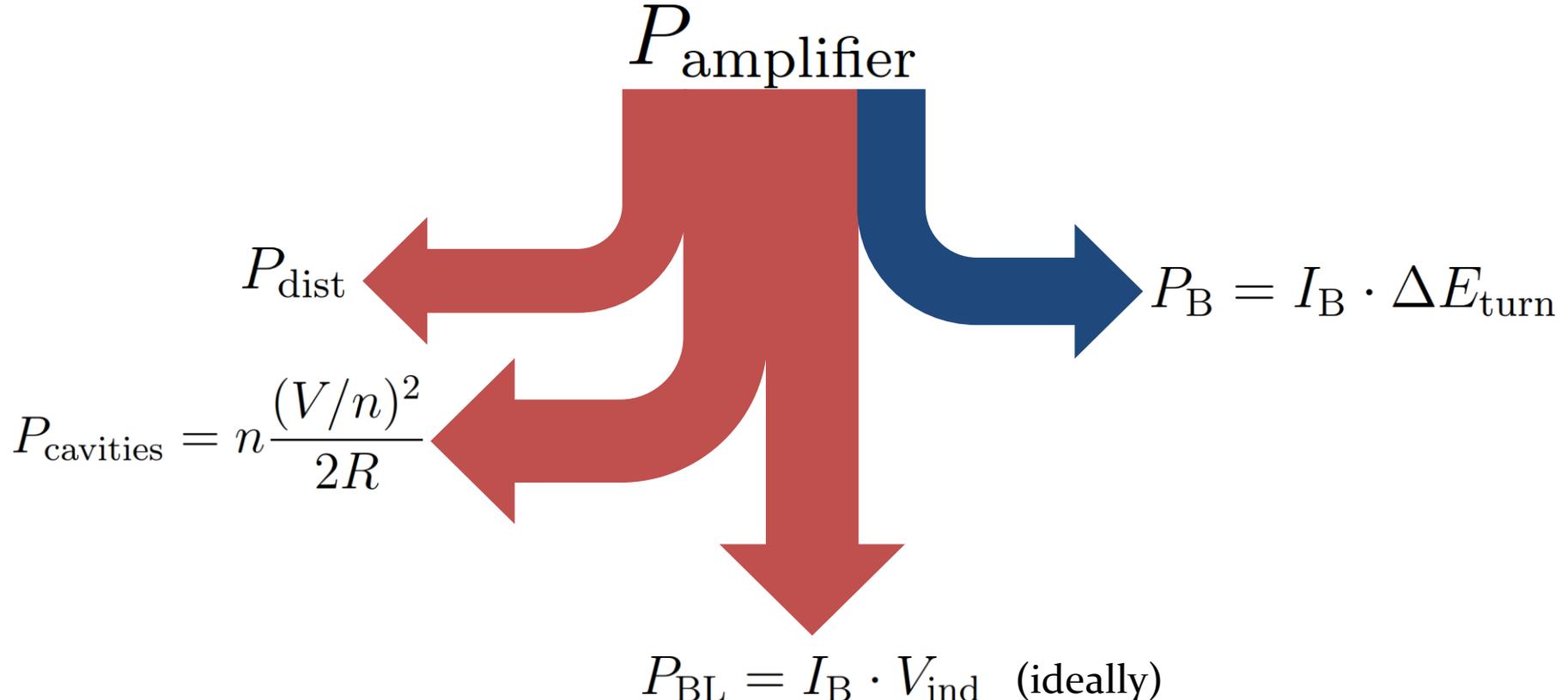1. Power to accelerate beam → Wanted
2. Compensate beam-induced voltage → Refl.  $P$
3. Compensate electrical losses in cavity → Heat
4. Compensate electrical losses in distribution → Heat



# Power amplifiers

- Basically


$$P_{\text{out}} = g \cdot P_{\text{in}} \quad \text{or} \quad V_{\text{out}} = \sqrt{g} \cdot V_{\text{in}}$$

- The ideal power amplifier

- Large bandwidth: amplifies all frequencies equally
  - No saturation, infinite power
  - Zero delay
  - No added noise
  - Unconditionally stable and resistant to reverse power
  - Radiation-hard
- 
- Unfortunately such a device has not been invented yet
  - Let us have a look at some real amplifiers

# Basics of grid tube

- From diode to tetrode amplifier

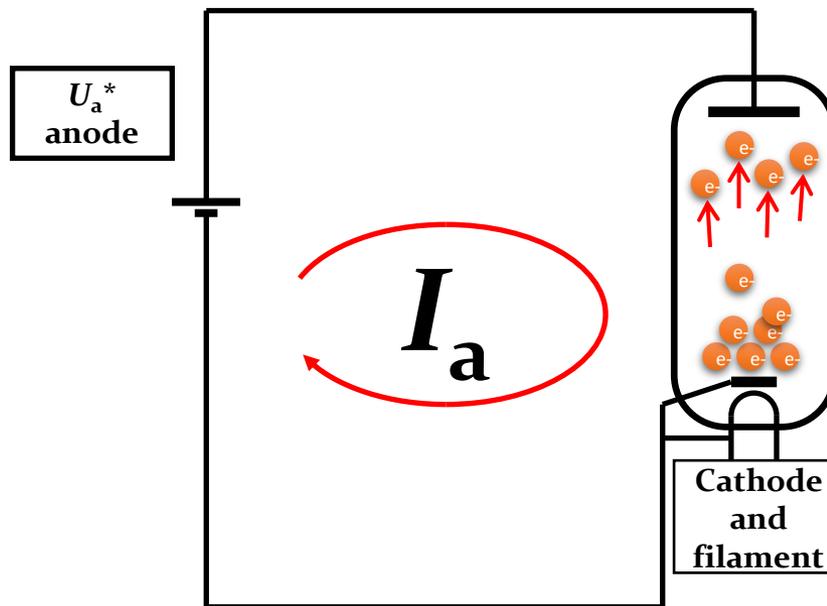


- Vacuum tube
  - Heater + Cathode
    - Heated cathode
      - Coated metal, carbides, borides,...
    - thermionic emission
    - Electron cloud
  - Anode
- Diode

\*For tube amplifier designs  
voltages are named  $U$  instead of  $V$

# Basics of grid tube


- From diode to tetrode amplifier

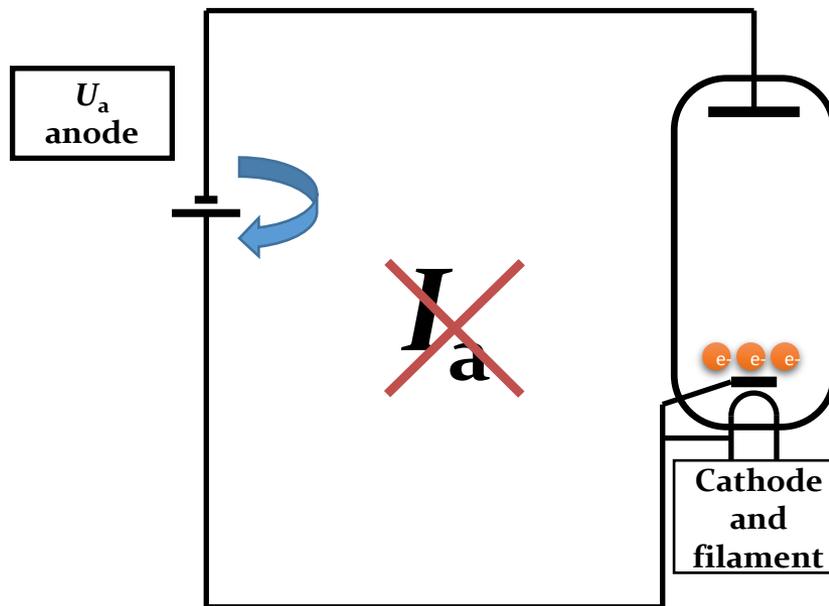

- Vacuum tube
  - Heater + Cathode
    - Heated cathode
      - Coated metal, carbides, borides,...
    - thermionic emission
    - Electron cloud
  - Anode
- Diode

# Basics of grid tube

- From diode to tetrode amplifier

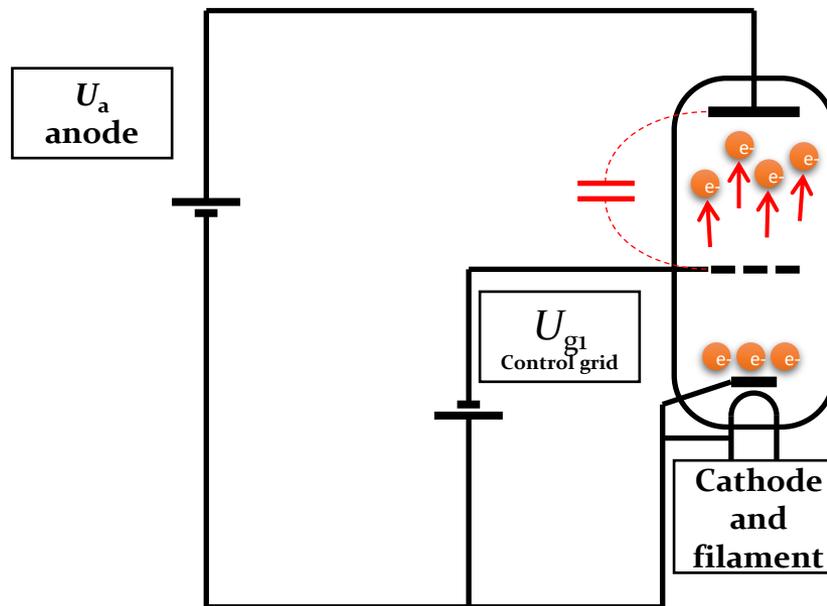


## →Triode

- Modulating the grid voltage proportionally modulates the anode current
- Transconductance
  - Voltage at grid
  - Current at anode
- **Limitations**
  - Parasitic capacitor from anode to control grid ( $g_1$ )
  - Tendency to oscillate

# Basics of grid tube

- From diode to tetrode amplifier

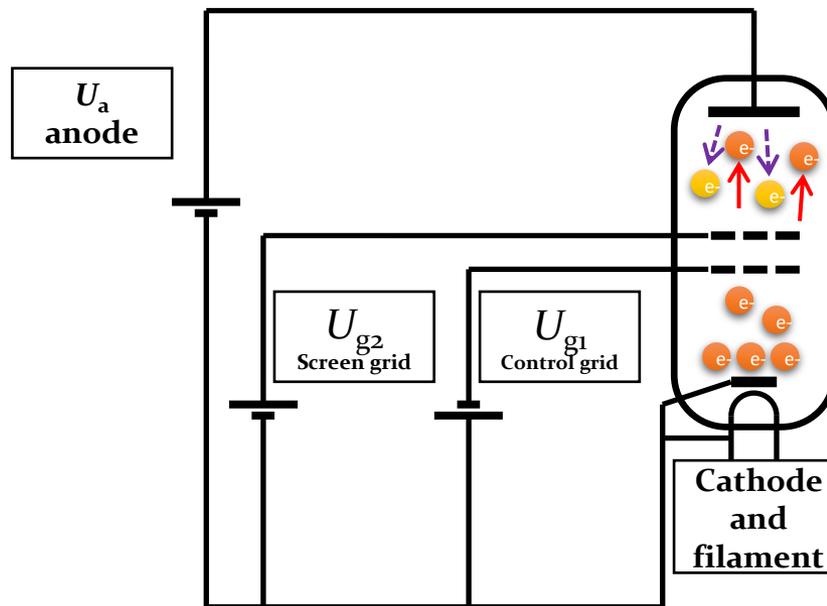


## →Tetrode

- **Screen grid**
  - Positive (lower anode)
  - Decouple anode and  $g_1$
  - Higher gain
- **Limitations**
  - Secondary electrons
  - Anode treated to reduce secondary emission

# Tetrode based power amplifier

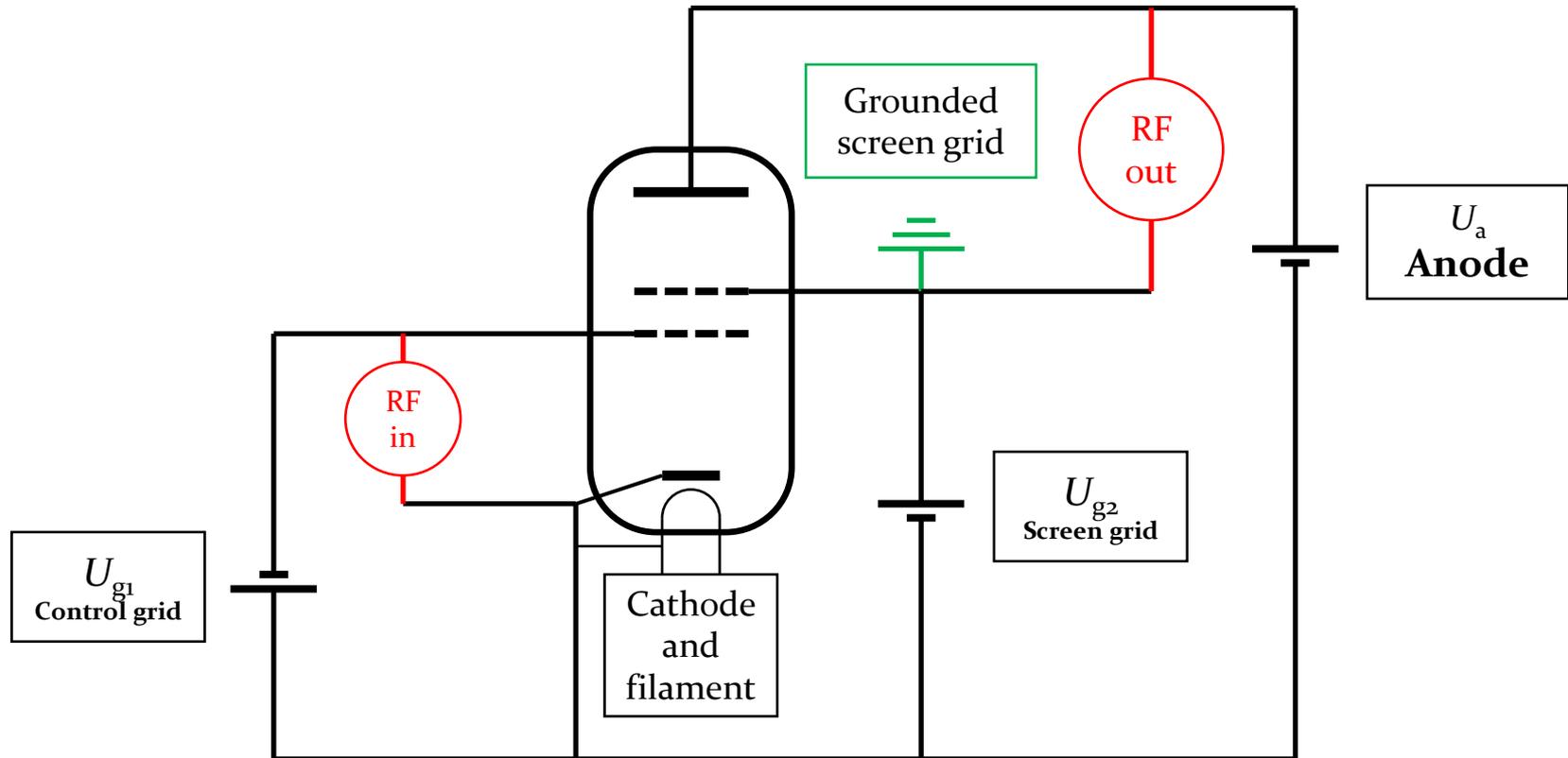- Example of SPS 200 MHz amplifier, tetrode RS2004



→ Very simplified block diagram

# Example: Tetrode amplifier driving SPS RF

- Two transmitters,  $2 \times 1$  MW at 200 MHz (almost continuous)
- Eight tetrodes per amplifier

RS2004 tetrode



Amplifier trolley




Complete transmitter



→ In operation since 1976
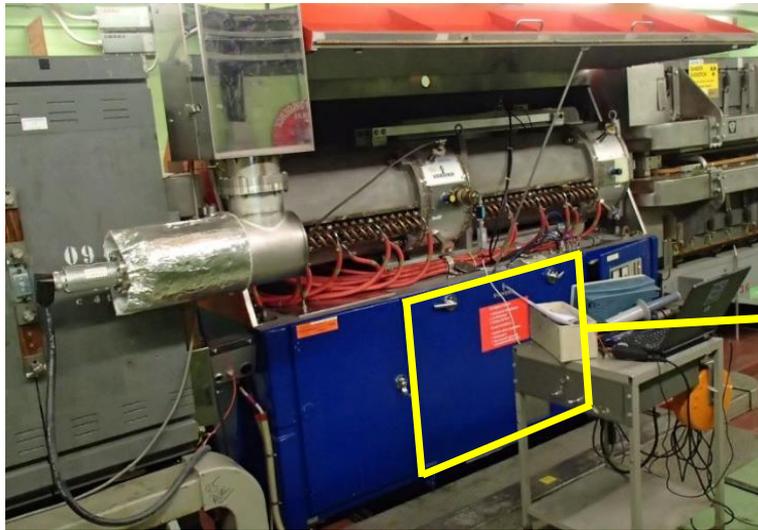
# Tetrode amplifier driving PS RF

- Frequency range 2.8...10 MHz, ~60 kW per cavity, 11 units
- **Space constraints to have amplifier installed below cavity**




Amplifier trolley



- **Tetrode is obvious choice**
  - High power in small volume
  - Operates in radioactive environment
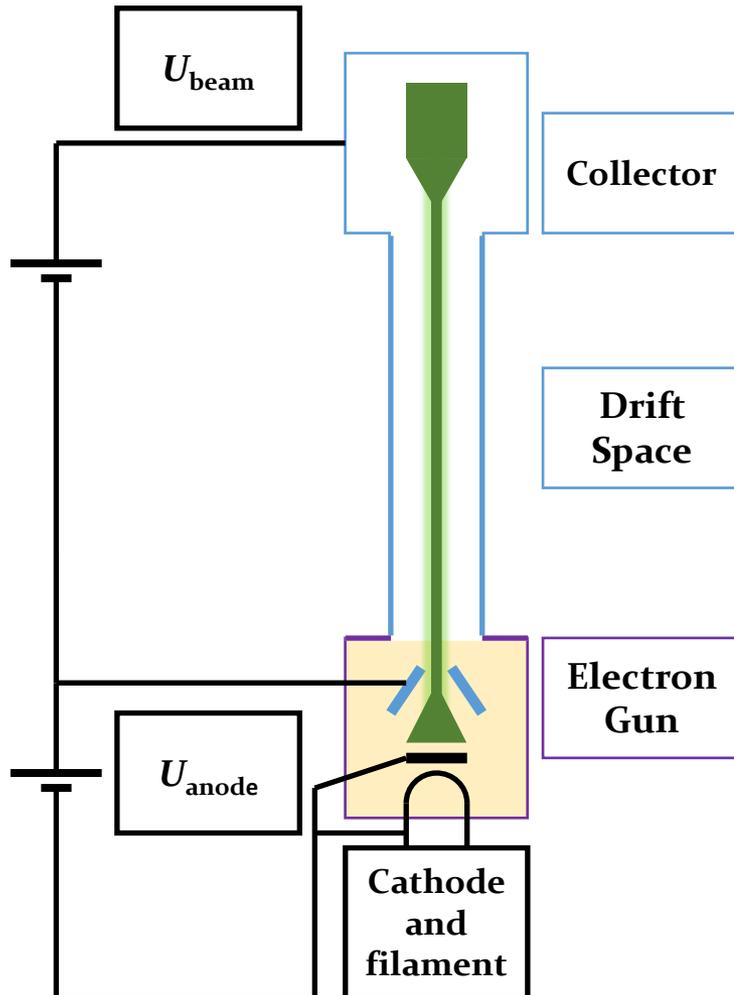
# Basics of linear beam tube


- **Klystron: a complete mini-accelerator**



- **Klystrons velocity modulation**
  - Converts the kinetic energy into RF power
- **Vacuum tube**
- **Electron gun**
  - Thermionic cathode
  - Anode
- **Electron beam**
- **Drift space**
- **Collector**
- **e- constant speed until the collector**
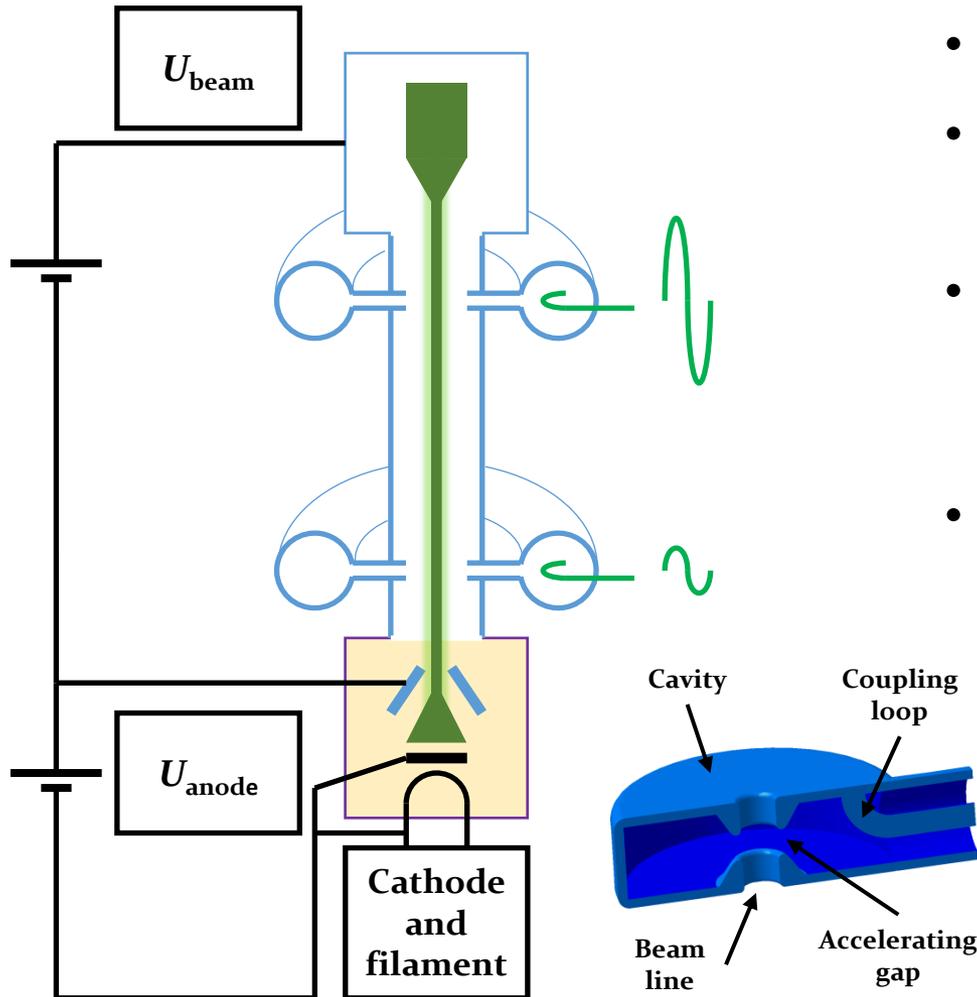
# Basics of linear beam tube


- **Klystron: a complete mini-accelerator**



- **Cavity resonators and drift**
- **RF input cavity (Buncher)**  
→ Modulates electron velocity
- **Drift space**  
→ Faster electrons catch up  
→ Slower electrons fall behind
- **RF output cavity (Catcher)**
  - Resonating at same frequency as input cavity
  - At place where electrons are **maximally bunched**
  - Kinetic energy converted into voltage and extracted
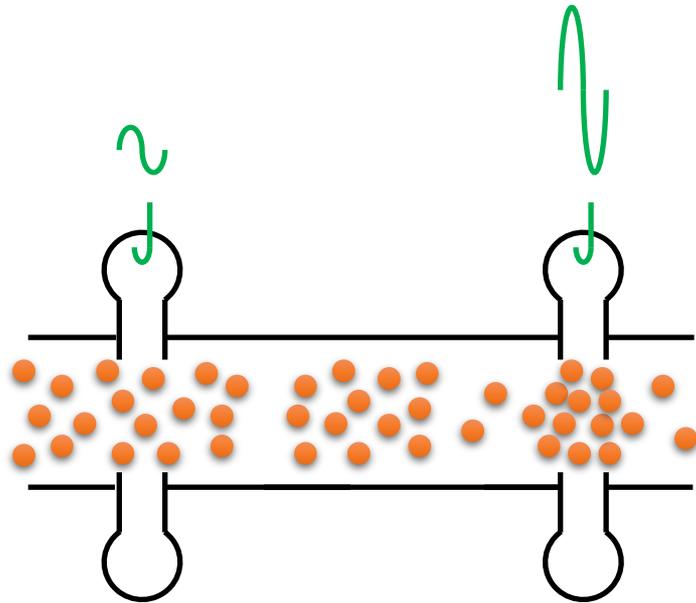
# Basics of linear beam tube

- **Klystron: a complete mini-accelerator**



- **Cavity resonators and drift**
- **RF input cavity (Buncher)**
  - Modulates electron velocity
- **Drift space**
  - Faster electrons catch up
  - Slower electrons fall behind
- **RF output cavity (Catcher)**
  - Resonating at same frequency as input cavity
  - At place where electrons are **maximally bunched**
  - Kinetic energy converted into voltage and extracted

# Example: Klystrons driving accelerators

- **2 × 8 cavities**, each driven by separate 400 MHz klystron, **330 kW**  
→ First klystron amplifiers powering a hadron collider



E. Montesinos

- 12 GHz pulsed klystron for CLIC  
→ **50 MW in 1.5 μs**




G. McMonagle

- Significantly more power was required to feed LEP (until 2000)  
→ About **50 MW CW** was installed at **352 MHz**



# Basics of RF solid state amplifiers


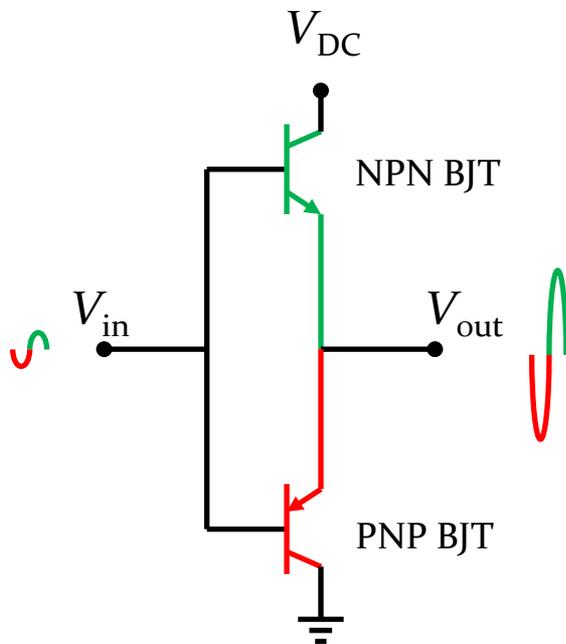


BJT: Bipolar Junction Transistor

- In a **push-pull** circuit the RF signal is applied to **two devices**
  - One of the devices is active on the positive voltage swing and off during the negative voltage swing
  - The other device works in the opposite manner so that the two devices conduct half the time
- The full RF signal is then amplified

→ Needs two different type of devices

# Basics of RF solid state amplifiers

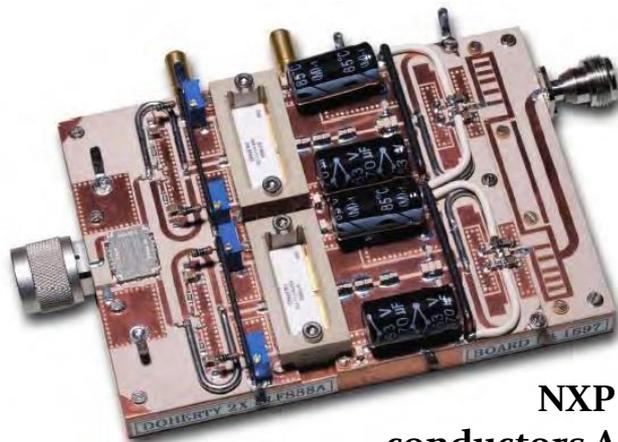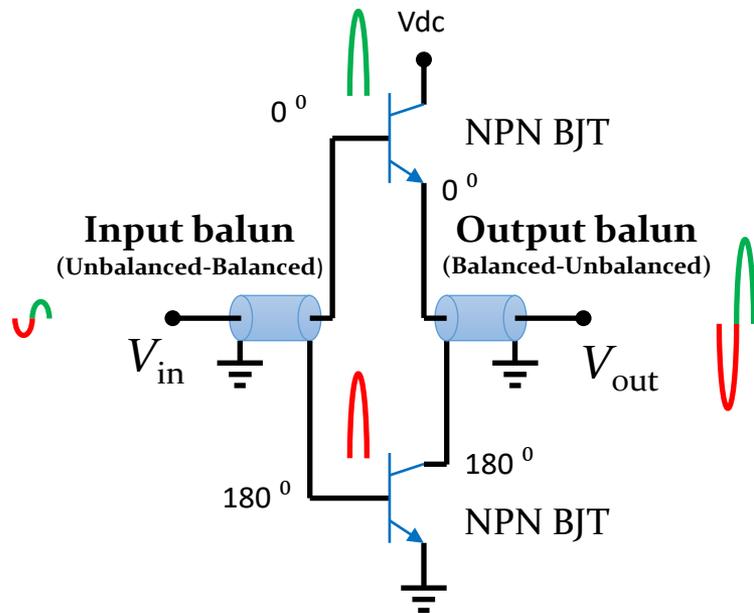


NXP Semi-  
conductors AN11325  
2-way Doherty amplifier with BLF888A


- Another **push-pull configuration** is to use a balun (balanced-unbalanced)
    - Power splitter, equally dividing the input power between the two transistors
    - Balun keeps one port in phase and inverts the second port in phase
  - Since the signals are out of phase only one device is On at a time
- This configuration is easier to manufacture since only one type of device is required

# Example: Soleil 45 kW, 352 MHz


Electron storage ring running at 352 MHz

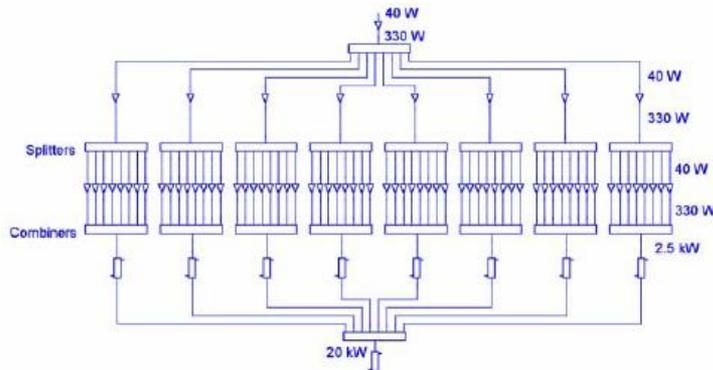

330 W amplifier module

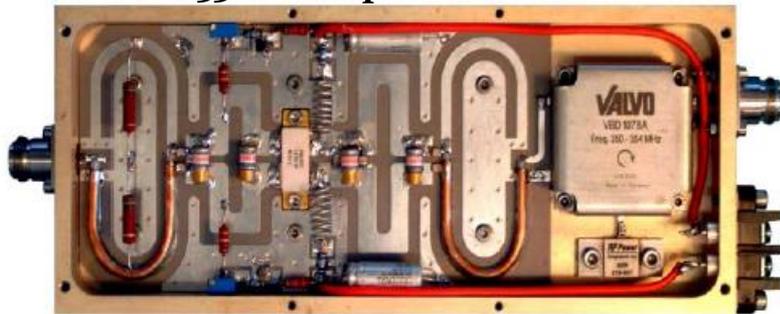

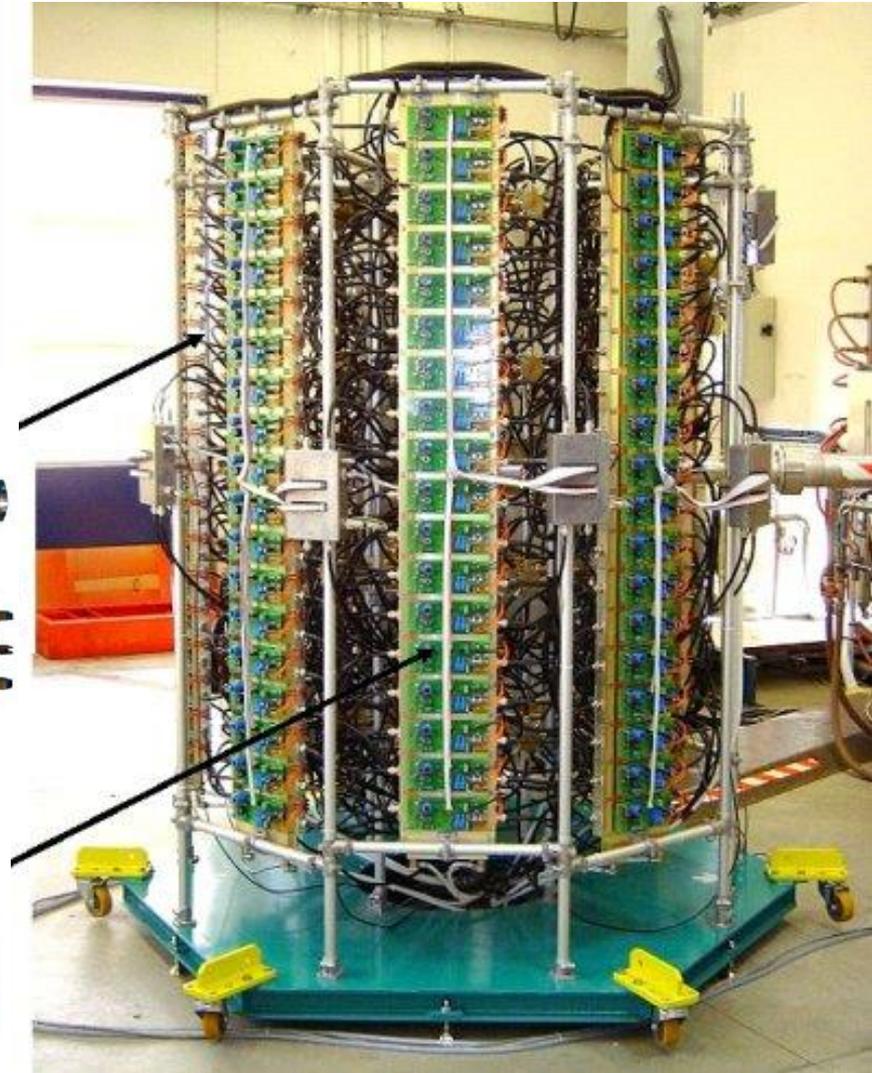600 W, 300 V<sub>DC</sub> / 30 V<sub>DC</sub> converter




# Example: Soleil 45 kW, 352 MHz

## Large scale solid state amplifier installations

45 kW per tower (2004 and 2007)




150 kW per tower (2012)

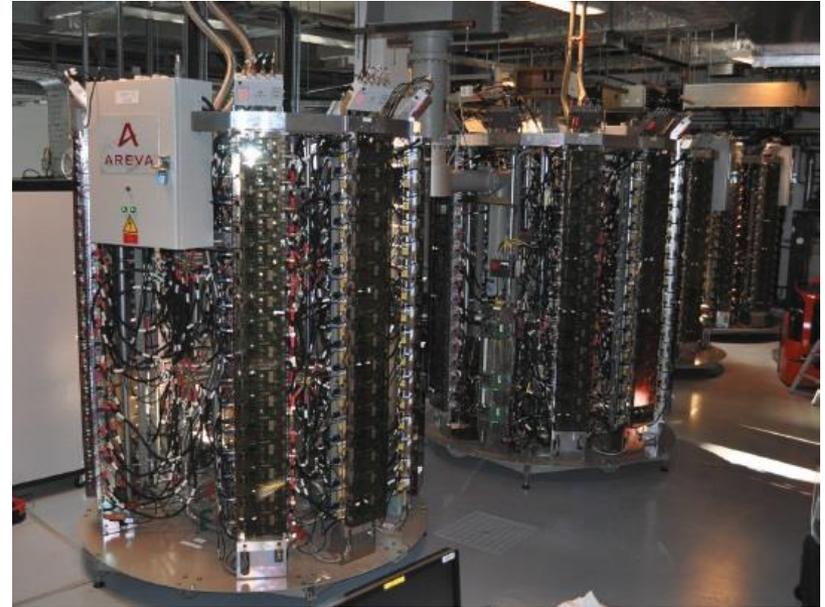

→ Requires a series of power combiners to moderate power per amplifier module to several tens of kilowatts
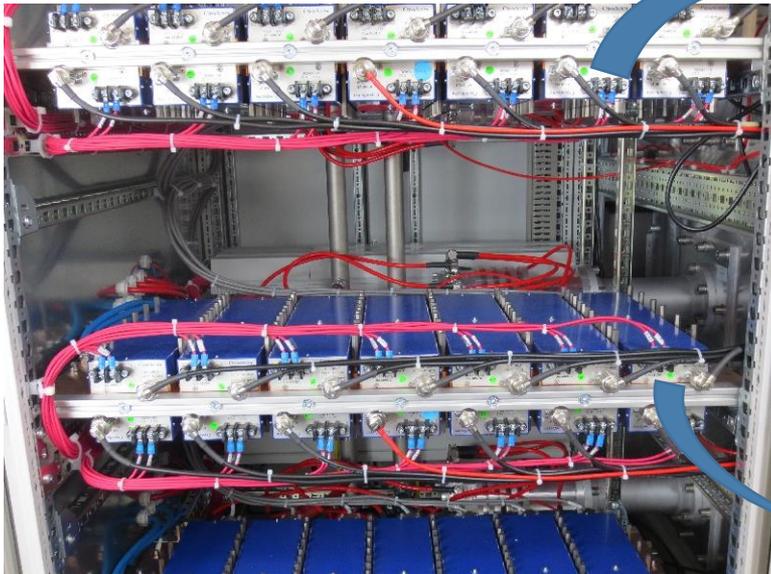
# Example: BESSY II


500 MHz solid state amplifiers:  $4 \times 80$  kW for storage ring,  
 $40$  kW for booster synchrotron



Amplifier modules



80 kW unit

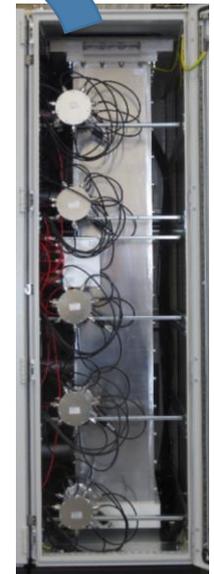


Combiner

- Power per module limited by RF transistors
- Increasing with modern semiconductor devices
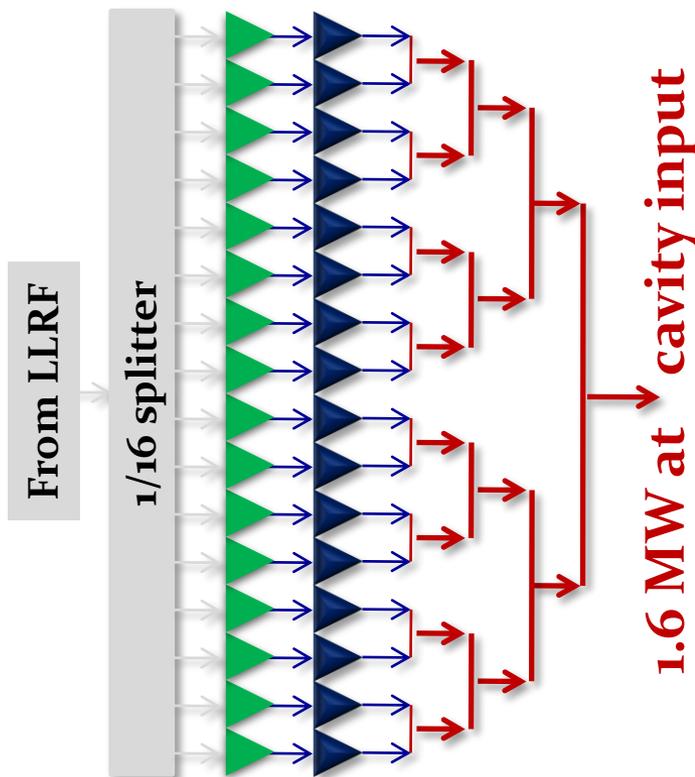
# Example: SPS


200 MHz solid state amplifiers:  $2 \times 1.6$  MW peak power,  
 $2 \times 16$  towers per amplifier



- 80 modules per tower, 1280 modules with **5120 transistors per amplifier**
- Presently the **largest RF installation** in a particle accelerator

# RF power amplifier
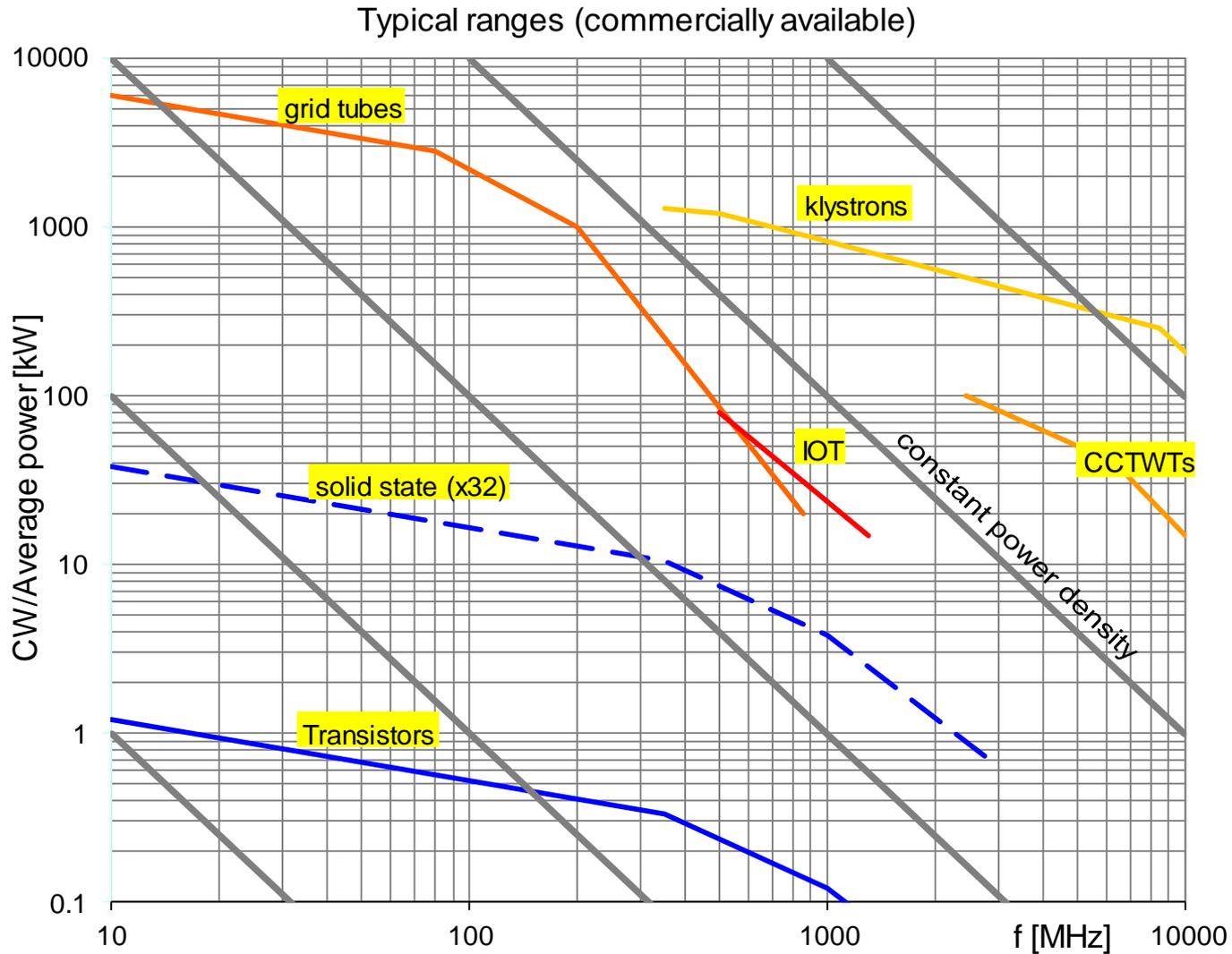
## Power capability of commercially available amplifier types



# How to choose the right RF amplifier?

| Prefer tube amplifier, when   | Prefer solid-state amplifier, when   |
|---|--|
| <ul style="list-style-type: none"> <li>• Amplifier must <b>be installed in the accelerator tunnel</b></li> <li>• Expecting important <b>spikes from beam induced voltage</b></li> <li>• <b>Large output power of a single device</b> is required, without combiners</li> <li>• Not much space is available</li> <li>• <b>High peak power</b> in pulsed mode</li> <li>• Amplifier must be <b>compact and/or close to cavity</b></li> </ul> | <ul style="list-style-type: none"> <li>• Amplifier can be located in <b>non-radioactive environment</b></li> <li>• <b>Circulator</b> can be installed to protect the amplifier</li> <li>• <b>Delay</b> due to unavoidable combiner stages is <b>little issue</b></li> <li>• Sufficient space can be made available</li> <li>• <b>Continuous operation</b></li> <li>• Amplifier can be <b>separate from the cavity</b></li> </ul> |

→ Mostly no hard criteria → decide on case by case basis

# Summary

- **RF system parameters**
  - **Choose frequency and voltage wisely**
- **Parameters of RF cavities**
  - **$R$ ,  $R/Q$**
  - **No 'one-size fits' all**
- **Power amplifier**
  - **Ideal amplifier does not (yet) exist**
  - **Tube or solid-state based**
- **Feedbacks and longitudinal beam control**
  - **Make the beam feel comfortable in bucket**
  - **Beam phase, radial and synchronization loops**

# RF Systems II



H. Damerou  
CERN



**Introduction to Accelerator Physics**

3 October 2023



## **Copyright statement and speaker's release for video publishing**

The author consents to the photographic, audio and video recording of this lecture at the CERN Accelerator School. The term “lecture” includes any material incorporated therein including but not limited to text, images and references.


The author hereby grants CERN a royalty-free license to use his image and name as well as the recordings mentioned above, in order to post them on the CAS website.

The material is used for the sole purpose of illustration for teaching or scientific research. The author hereby confirms that to his best knowledge the content of the lecture does not infringe the copyright, intellectual property or privacy rights of any third party. The author has cited and credited any third-party contribution in accordance with applicable professional standards and legislation in matters of attribution.

# Outline

- Introduction
- Choice of parameters
  - Frequency and voltage
- RF cavity parameters
  - Shunt impedance, beam loading, power coupling
- **Power amplifiers**
  - Tube or solid state
  - Local feedbacks
- **Longitudinal beam control system**
  - Building blocks: RF source and receiver
  - Phase, radial and synchronization loops
- **Summary**

# RF system overview

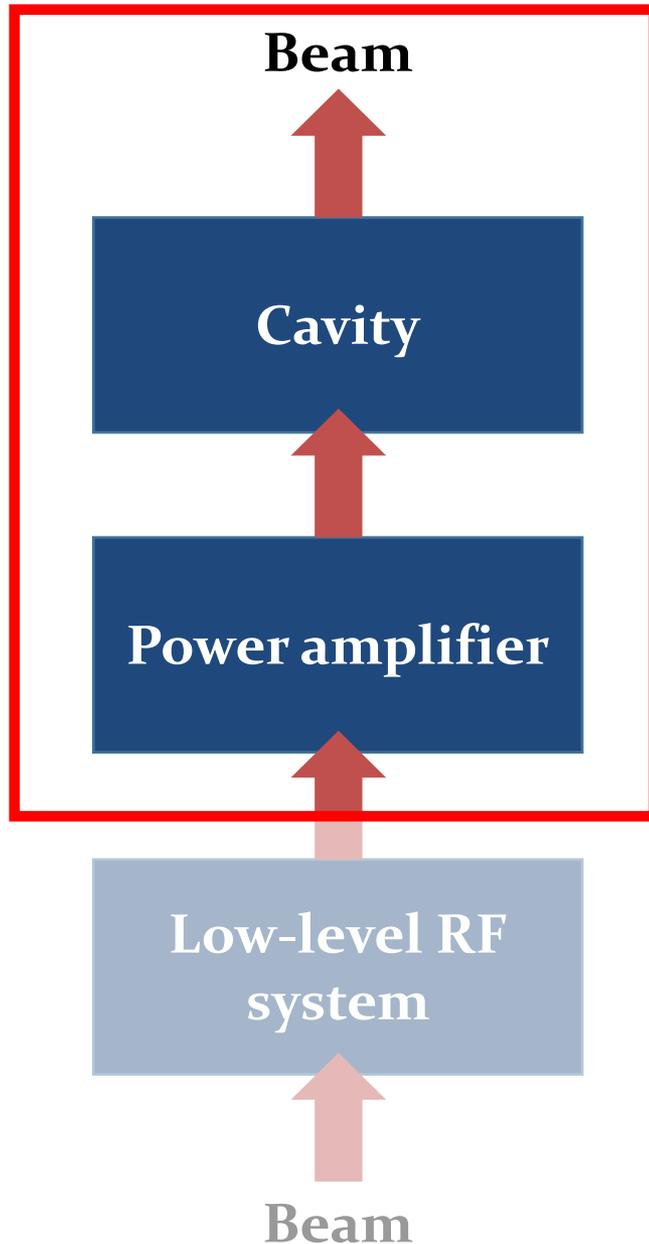

→ Convert RF power into longitudinal electric field


→ Amplify low-power signal from beam control to kW, MW or GW

→ Provide RF signals with correct frequency, amplitude and phase

# Local feedbacks
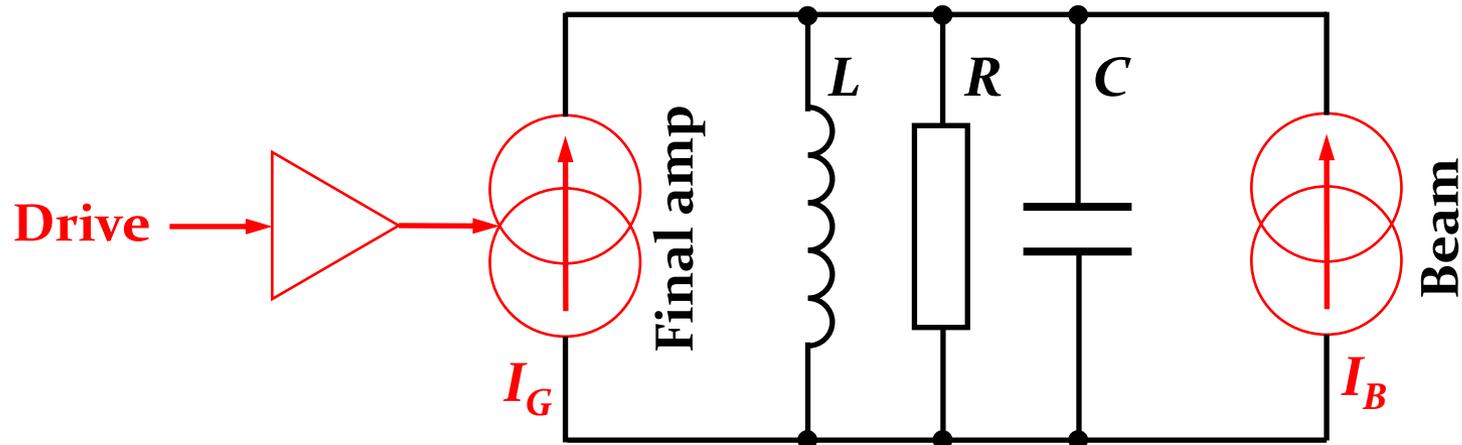
# Reduction of cavity impedance


- Energy transfer from cavity to beam, but **from beam to cavity**
- Both, RF generator and **beam can induced voltage** in cavity



1. Reduce beam induced voltage by reducing  $R$ , **but not efficient**  
→ Obviously needs more power → \$\$\$
2. Feedback to decrease the apparent impedance for the beam  
→ Use amplifier to counteract beam induced voltage
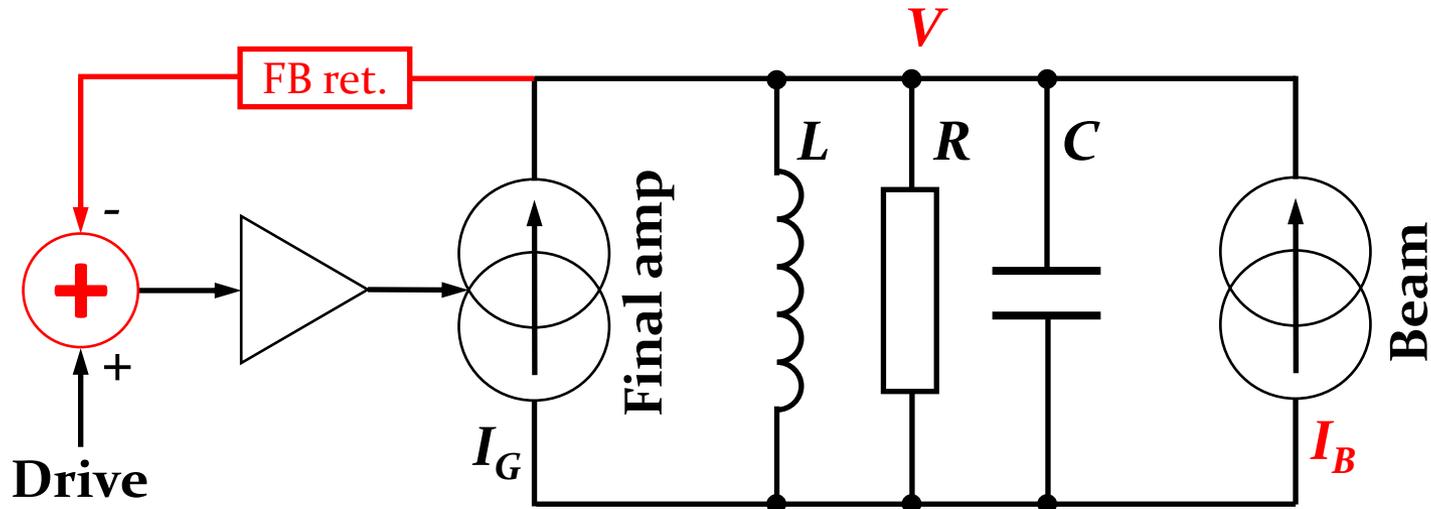
# Reduction of cavity impedance

- Energy transfer from cavity to beam, but **from beam to cavity**
- Both, RF generator and **beam can induced voltage** in cavity




1. **Compare** drive signal (no beam) with gap (beam and generator)
2. **Amplify** inverted difference

$$Z_{\text{eq}}(\omega) = \frac{dV}{dI_B} = \frac{Z(\omega)}{1 + g_{\text{OL}}}$$
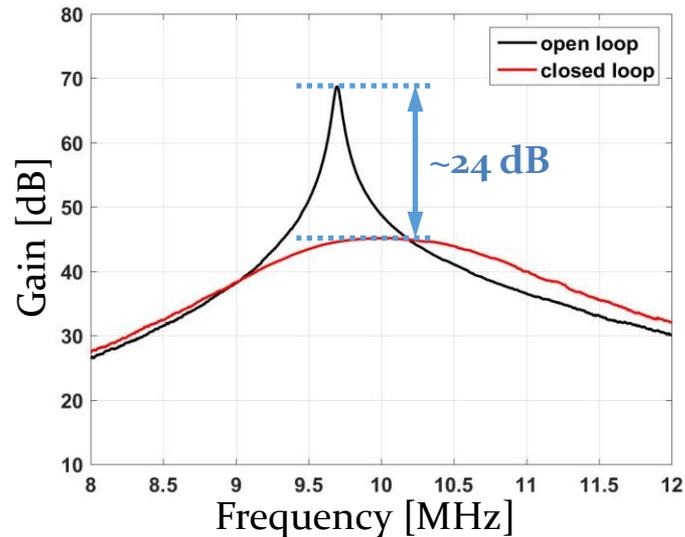
# Example: 10 MHz RF system in CERN PS

Transfer function with and without feedback



- Feedback gain of 24 dB
- Equivalent impedance,  $Z_{eq}(\omega)$  reduced
- Impedance for amplifier remains unchanged,  $Z(\omega)$




## Why not further reduction with more gain?

- Subtraction of gap voltage and drive signal imperfect due to
  1. Delay of cables and amplifier
  2. Parasitic resonances of amplifier and cavity system

Bandwidth  $\uparrow$   $\Leftrightarrow$  Achievable gain  $\downarrow$
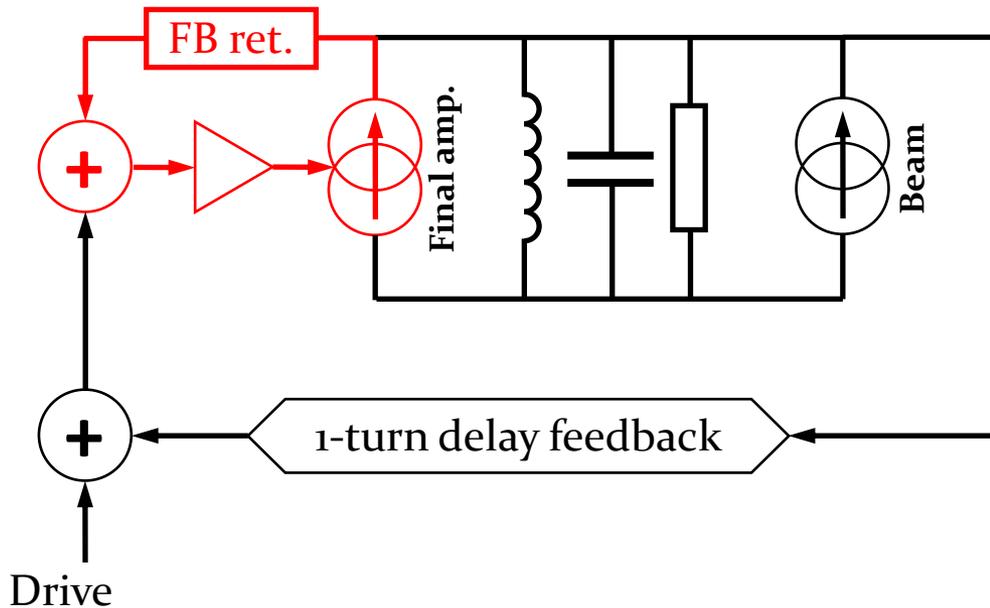
# Example: 10 MHz RF system in CERN PS


- 10 + 1 ferrite loaded cavities, tunable from 2.8...10 MHz



- Fast wide-band feedback  
around amplifier (internal)  
→ Gain limited by delay
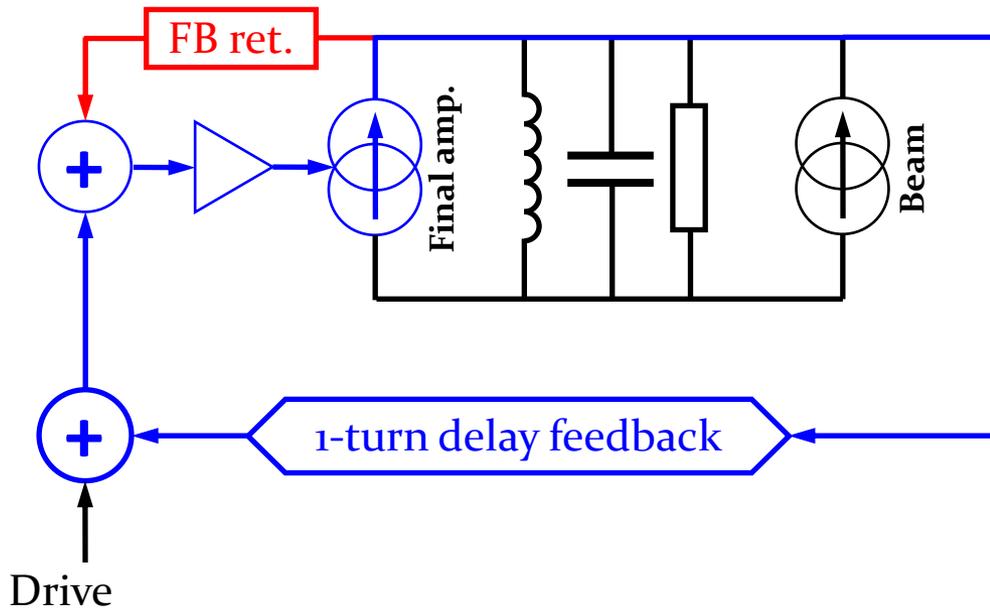
# Example: RF feedback with 1-turn delay

- 10 + 1 ferrite loaded cavities, tunable from 2.8...10 MHz




- Fast wide-band feedback around amplifier (internal)  
 → Gain limited by delay

- 1-turn delay feedback  
 → High gain at  $n \times f_{rev}$

# Example: RF feedback with 1-turn delay

→ Reduce cavity impedance beyond stability limit of wide-band FB



Open/closed loop transfer functions

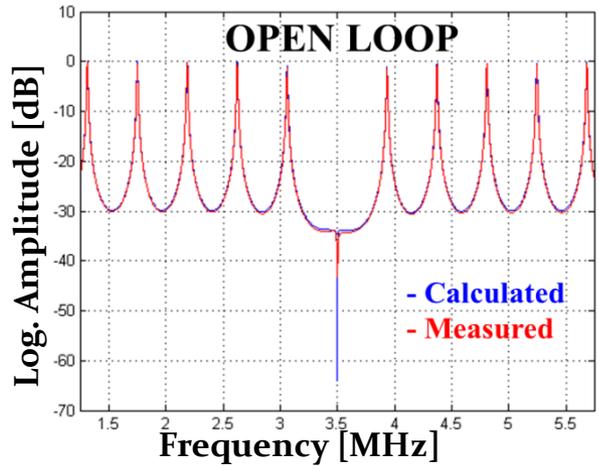


Spectrum at cavity gap return

Feedback **off**

Feedback **on**

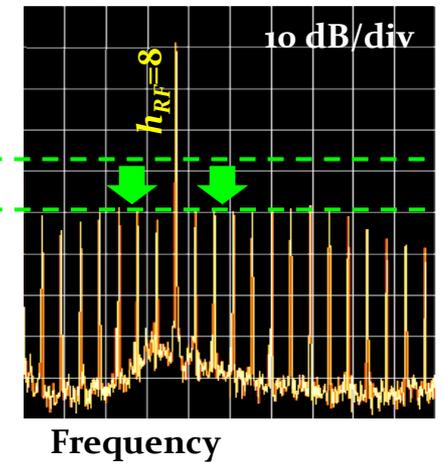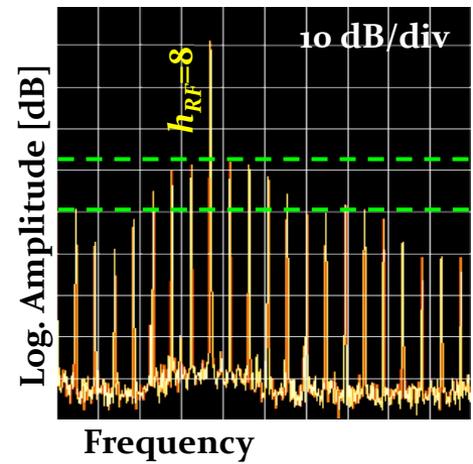


D. Perrelet

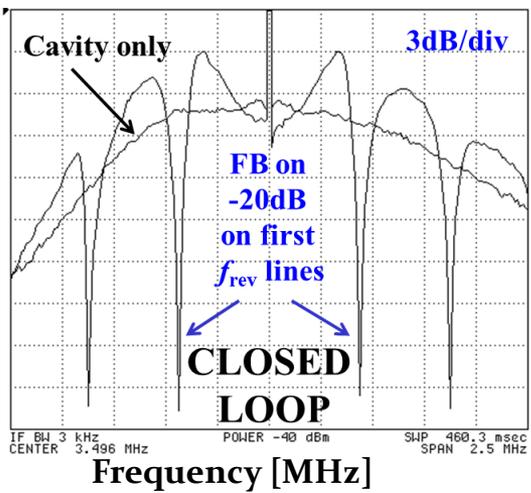

→ Important additional impedance reduction

→ Clever usage of beam periodicity in circular accelerator

# RF system overview

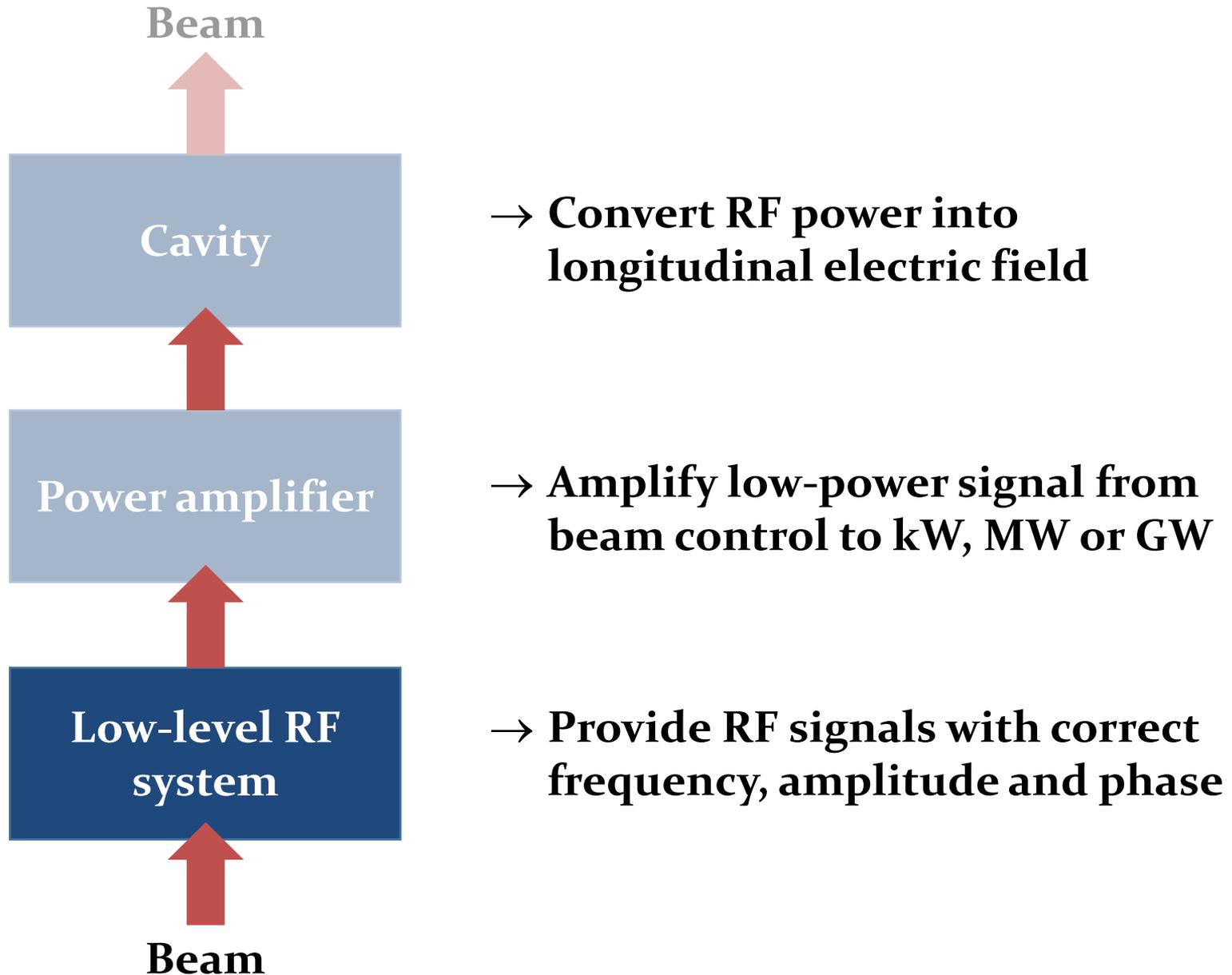


# **Global feedbacks**

## **Low-level RF beam control**
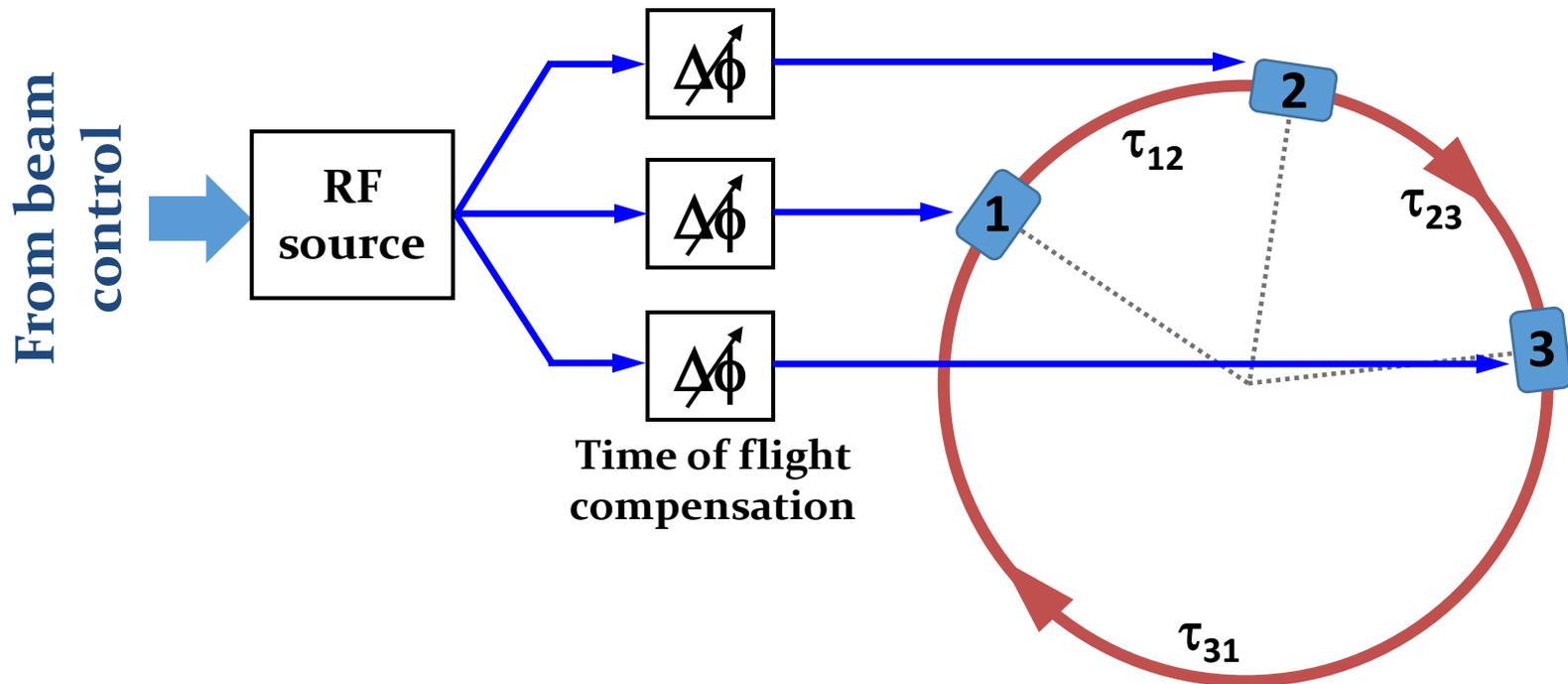
# Longitudinal beam control

- **Local** feedbacks → Act on individual RF stations
- **Global** feedbacks → Act on all RF stations simultaneously




- RF distribution to compensate time of flight between stations
- Beam control drives all stations **like a single one**

# Basic building blocks
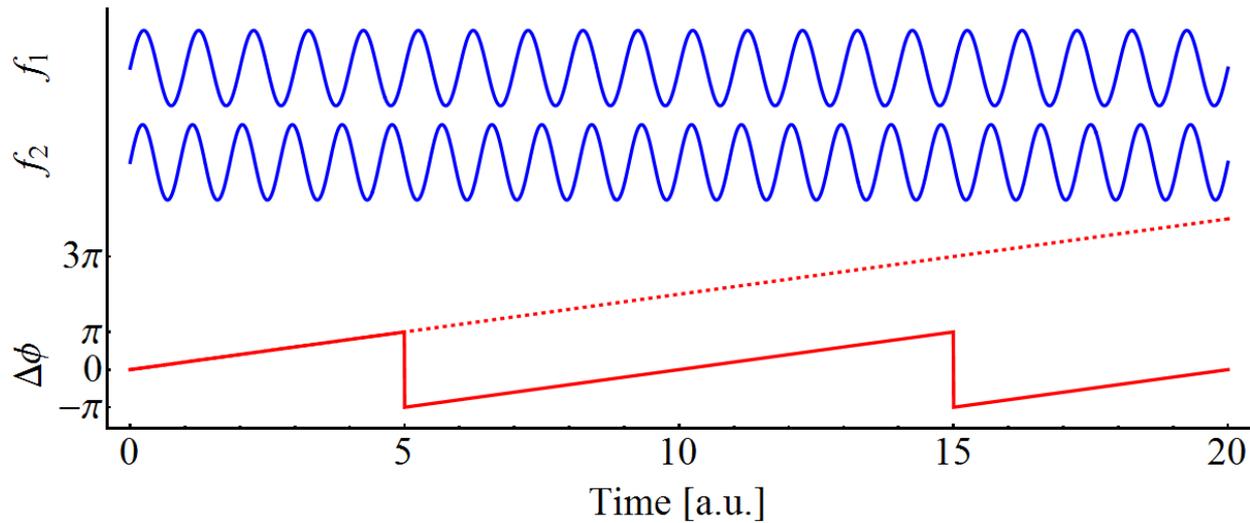
# Measure phase differences

- Two signals at different frequencies  $\omega_1$  and  $\omega_2$




- Phase difference,  $\Delta\phi$ , between both signals changes linearly
- Ambiguity to distinguish between  $\Delta\phi = -\pi, \pi, -3\pi, 3\pi, \dots$
- Saw-tooth in phase means constant frequency difference

→ Equivalence of frequency and phase


$$\omega = \frac{d\phi}{dt} \quad \Leftrightarrow \quad \phi = \int \omega dt$$

# Mixer or multiplier

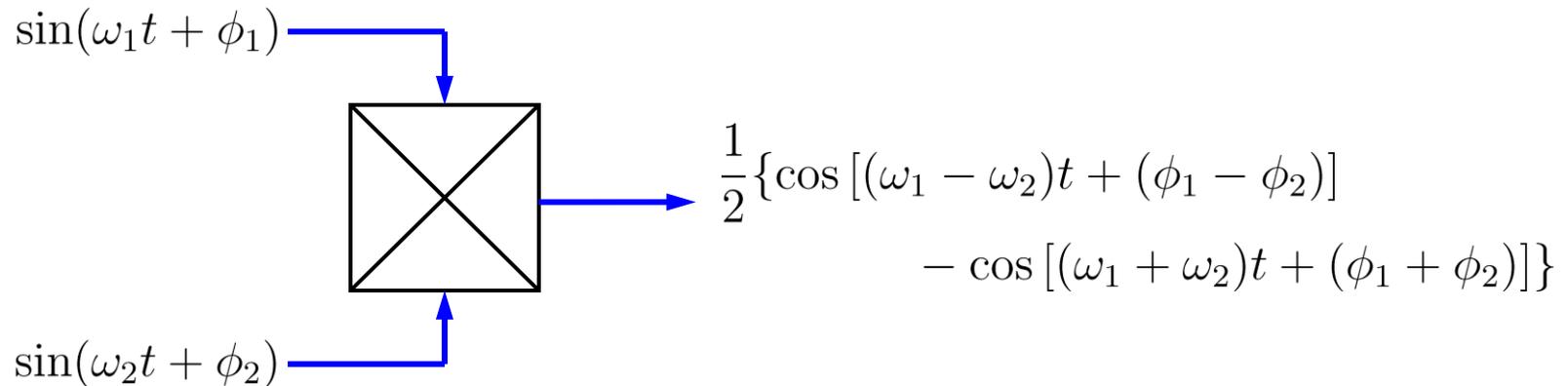- **Example: analogue 4 quadrant multiplier and low pass filter**




- **Signals:**

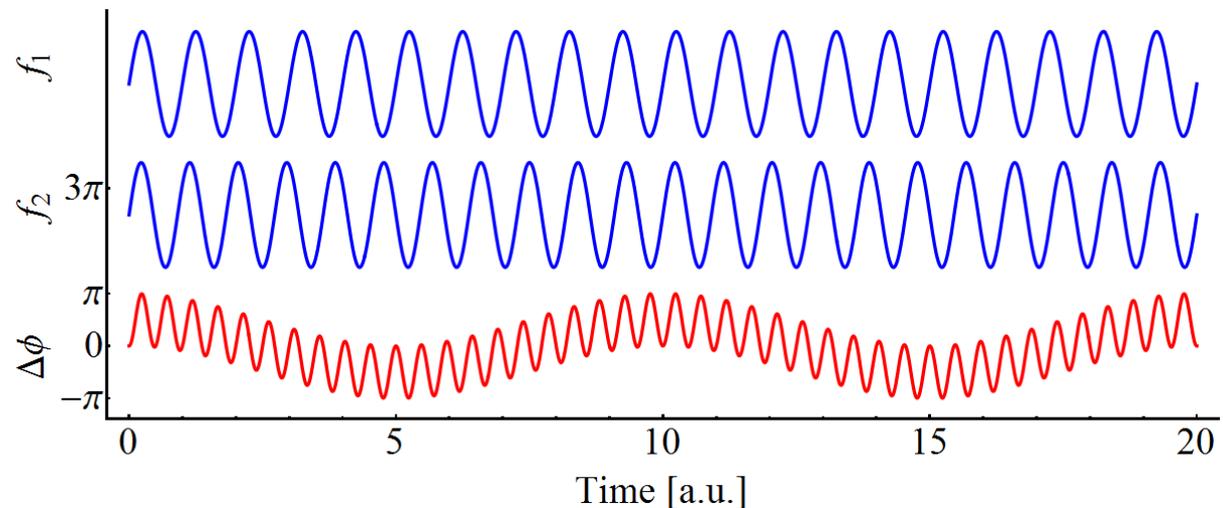


# Mixer or multiplier

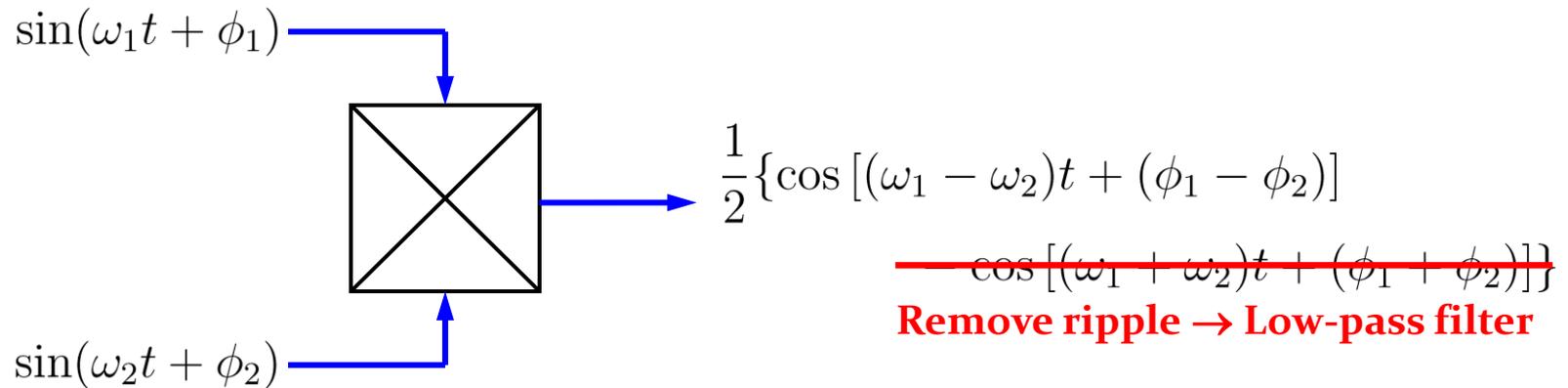- **Example: analogue 4 quadrant multiplier and low pass filter**




- **Signals:**

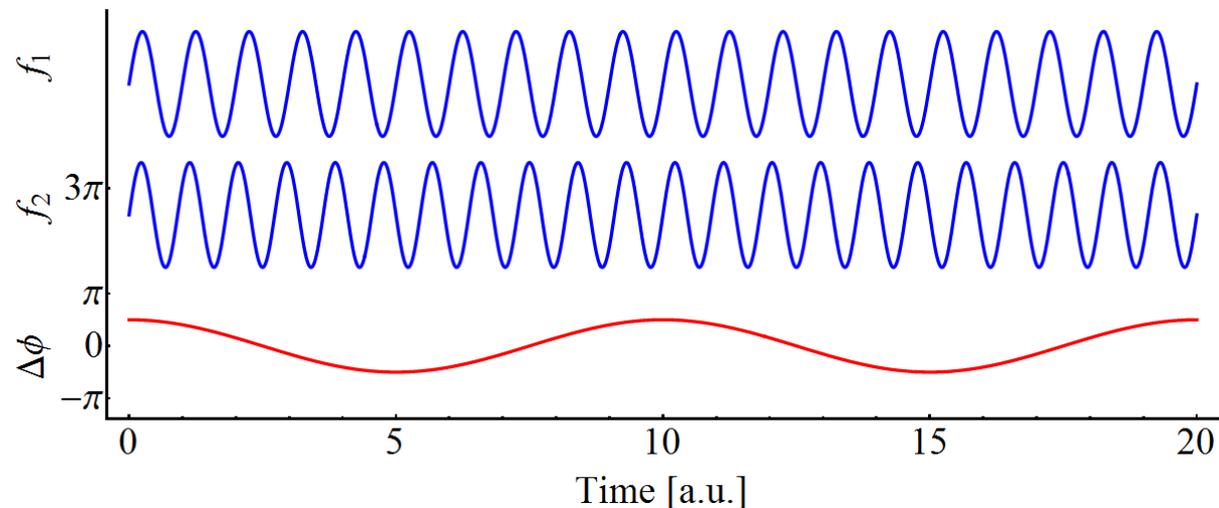


# How to detect phase differences?

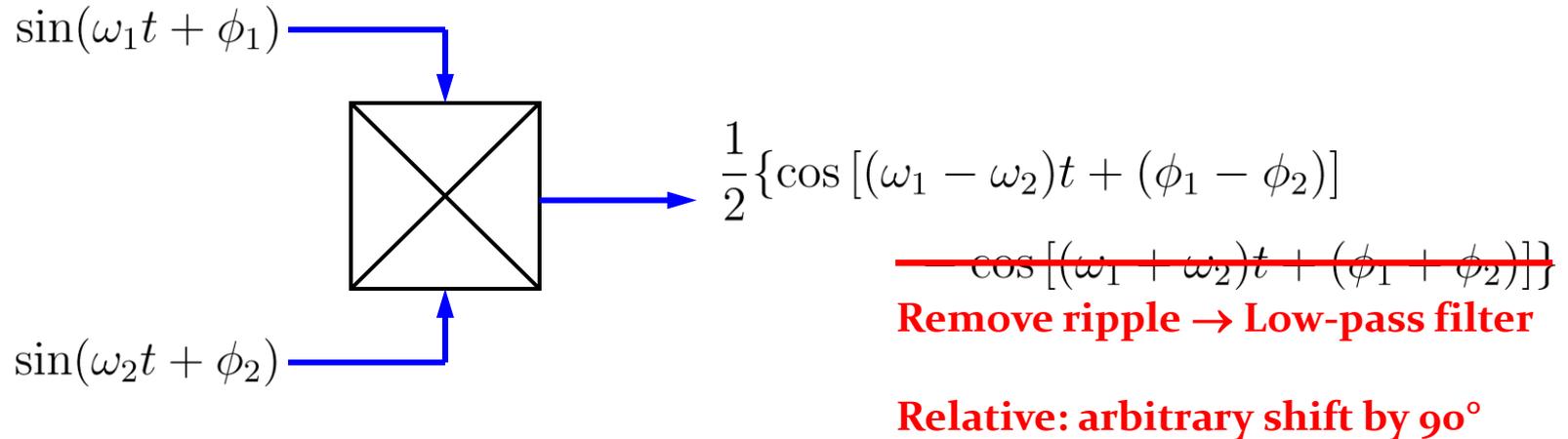- **Example: analogue 4 quadrant multiplier and low pass filter**



- **Signals:**

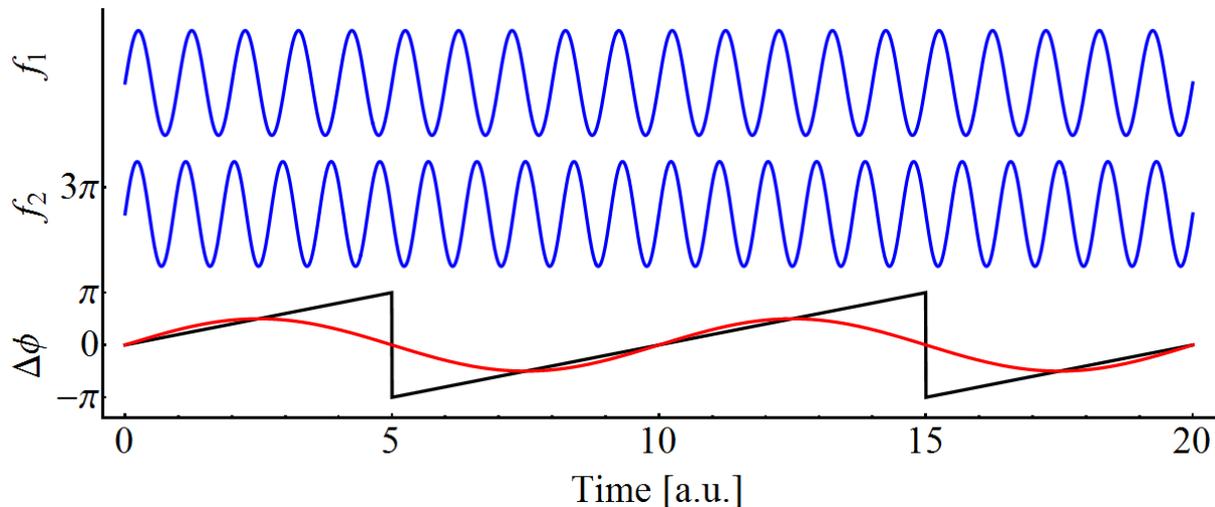

- **Phase discriminator in approximately  $\pm 90^\circ$  range**

# RF sources

# RF sources

What finally generates the RF signal to power amplifier and cavity?

→ Need an RF source!



- **Electron accelerators**



- Off-the-shelf high-performance laboratory generators as reference: **BESSY SR, CERN CTF<sub>3</sub>**
- Dedicated commercial fixed-frequency sources with low phase noise: **free electron lasers, CERN AWAKE**

- **Proton accelerators**

- Special sweeping RF sources, controlled by beam-based loops: **mostly in-house developments**
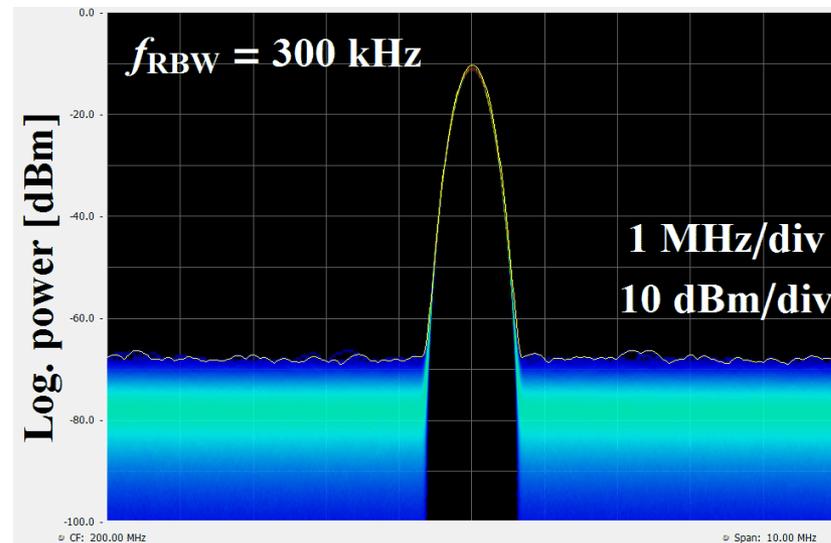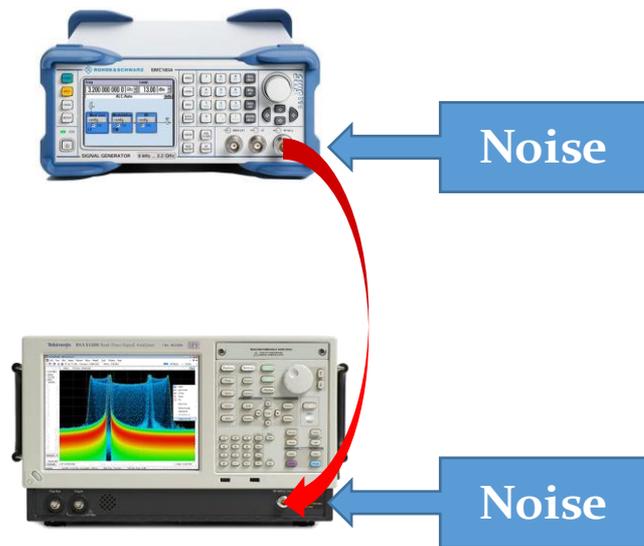
# Noisy RF signals


- Degradation of signal quality due to noise
  - Amplitude and/or phase jitter
- What is the difference between a coherent signal and noise?



- Amplitude of **coherent**, quasi **monochromatic** signal (at 200 MHz) is **independent of observation bandwidth**
- Incoherent **noise power** (dominated by spectrum analyzer front-end amplifier/mixer) is **proportional to bandwidth**
- Thermal noise power  $\frac{P}{\Delta f} = k_B T = 1.38 \cdot 10^{-23} \text{ J/K} \cdot 296 \text{ K} \simeq -174 \text{ dBm/Hz}$
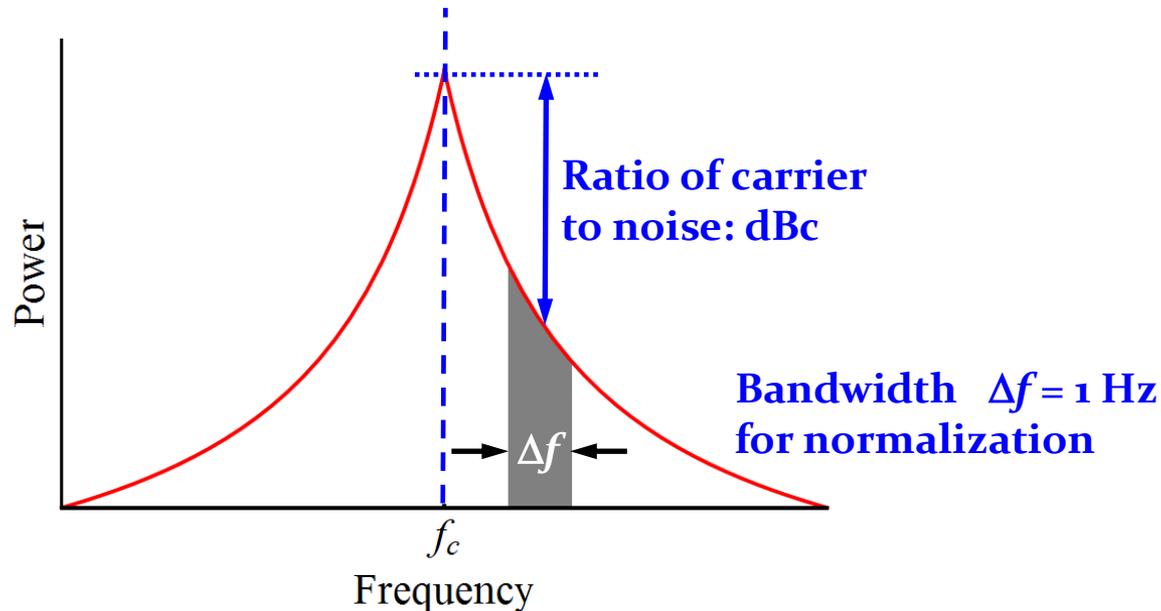
# Analysis of phase noise

- Compare noise power with carrier power as reference



- **Noise power density**  $\mathcal{L}(f) = \frac{\text{Power density}}{\text{Carrier power}} \left[ \frac{\text{dBc}}{\text{Hz}} \right] = \frac{1}{2} S_\phi(f)$



→ Its integral is the phase jitter and using  $\Delta t = \frac{\Delta\phi}{2\pi f_c}$

the jitter in time becomes

$$\Delta t_{\text{rms}} = \frac{1}{2\pi f_c} \sqrt{\int_{f_1}^{f_2} S_\phi(f) df}$$
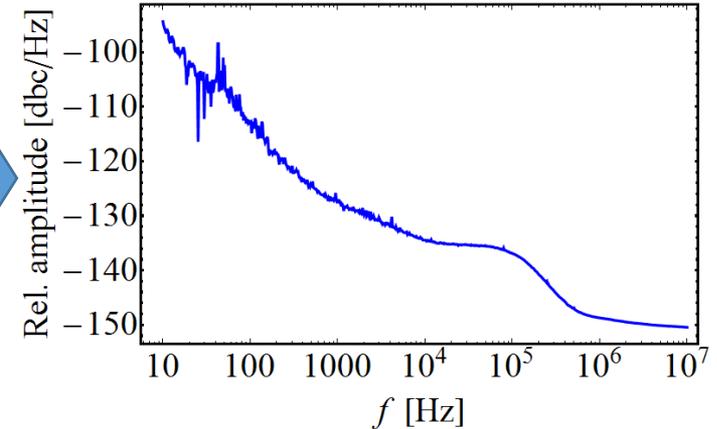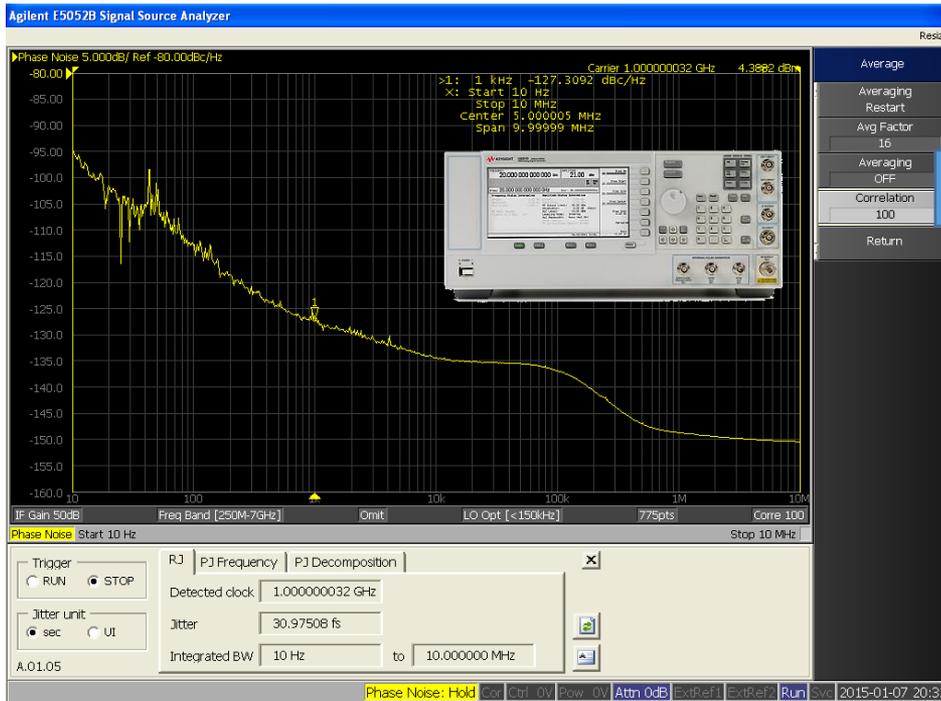
# Typical phase noise plots

- Measure phase noise of a synthesized lab generator



→ Note: jitter values can be added as square root of quadratic sum


$$\Delta t_{\text{rms}} = \sqrt{\Delta t_{\text{rms},1}^2 + \Delta t_{\text{rms},2}^2 + \dots}$$

→ Convenient split to relevant ranges

| Frequency range | $\Delta t_{\text{rms}}$ [fs] |
|-----------------|------------------------------|
| 10...100 Hz     | 12.4                         |
| 100 Hz ...1 kHz | 5.4                          |
| 1...10 kHz      | 5.4                          |
| 10...100 kHz    | 11.1                         |
| 100 kHz...1 MHz | 13.0                         |
| Total           | 31.0                         |
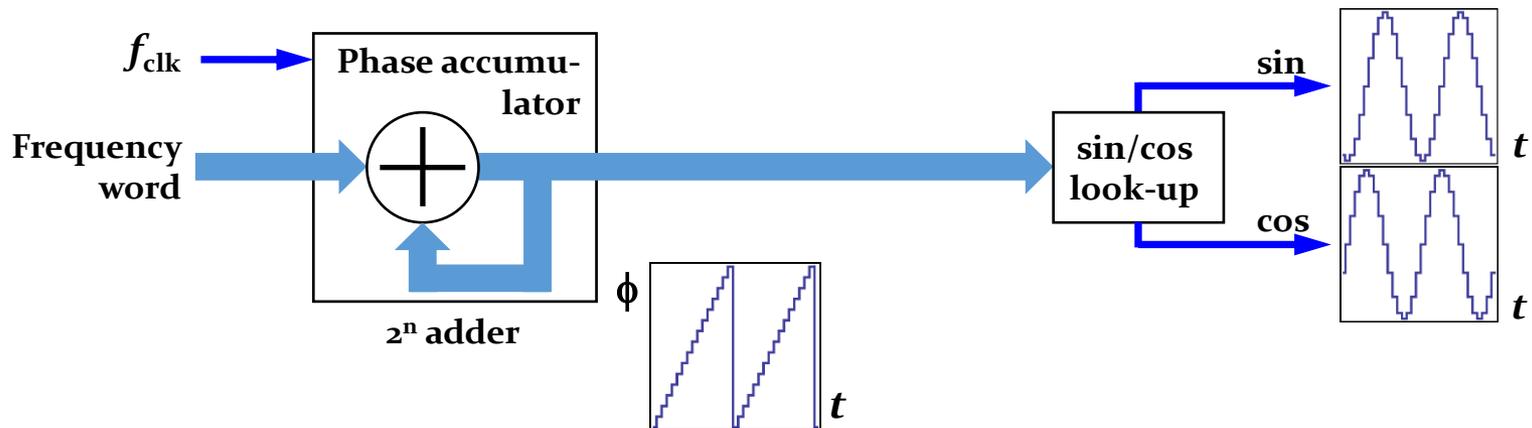
# Variable frequency: direct digital synthesis



- Generate (almost) any frequency starting from a given clock frequency,  $f_{\text{clk}}$
- Digitally programmable **in frequency**



$$f_{\text{out}} = \frac{\text{Frequency word}}{2^n} \cdot f_{\text{clk}}$$
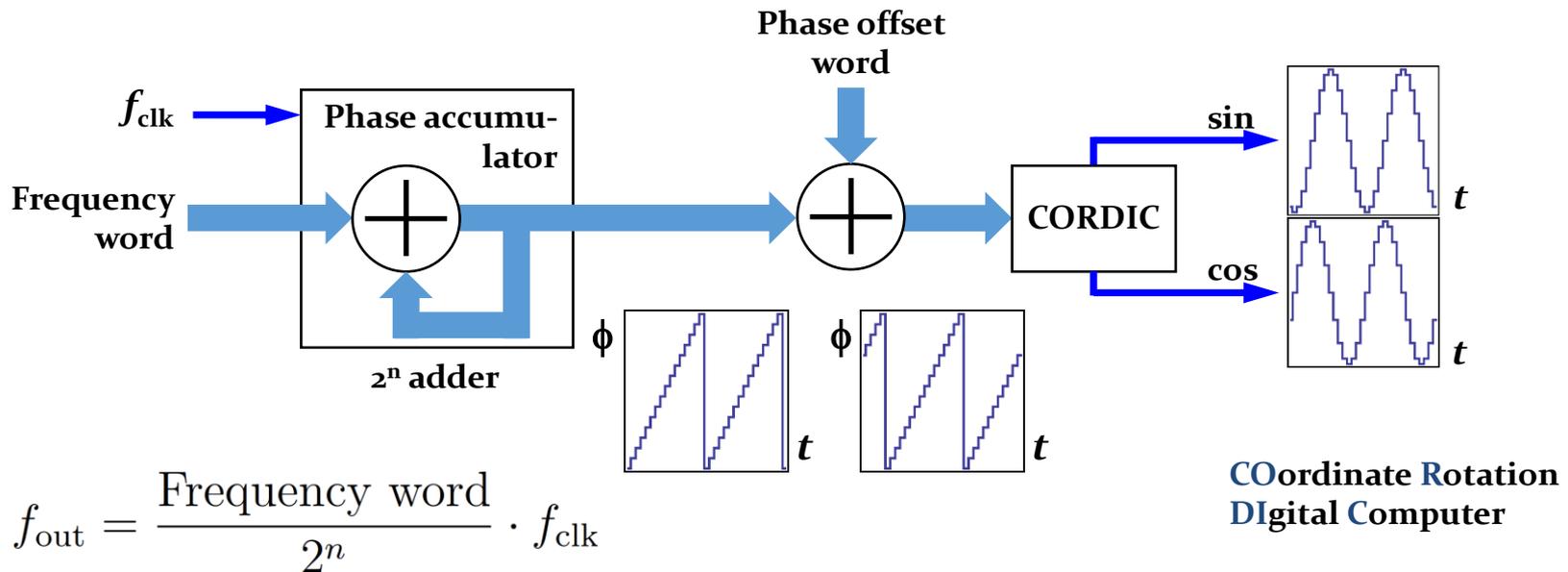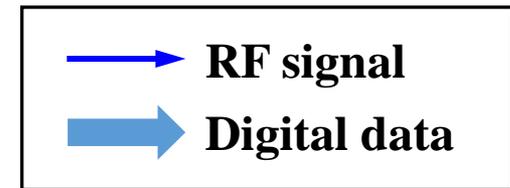
# Variable frequency: direct digital synthesis

- Generate (almost) any frequency starting from a given clock frequency,  $f_{\text{clk}}$
- Digitally programmable **in frequency and phase**




- Two output signals with ideal  $90^\circ$  phase shift
- Output signals are digital data streams

# Receivers
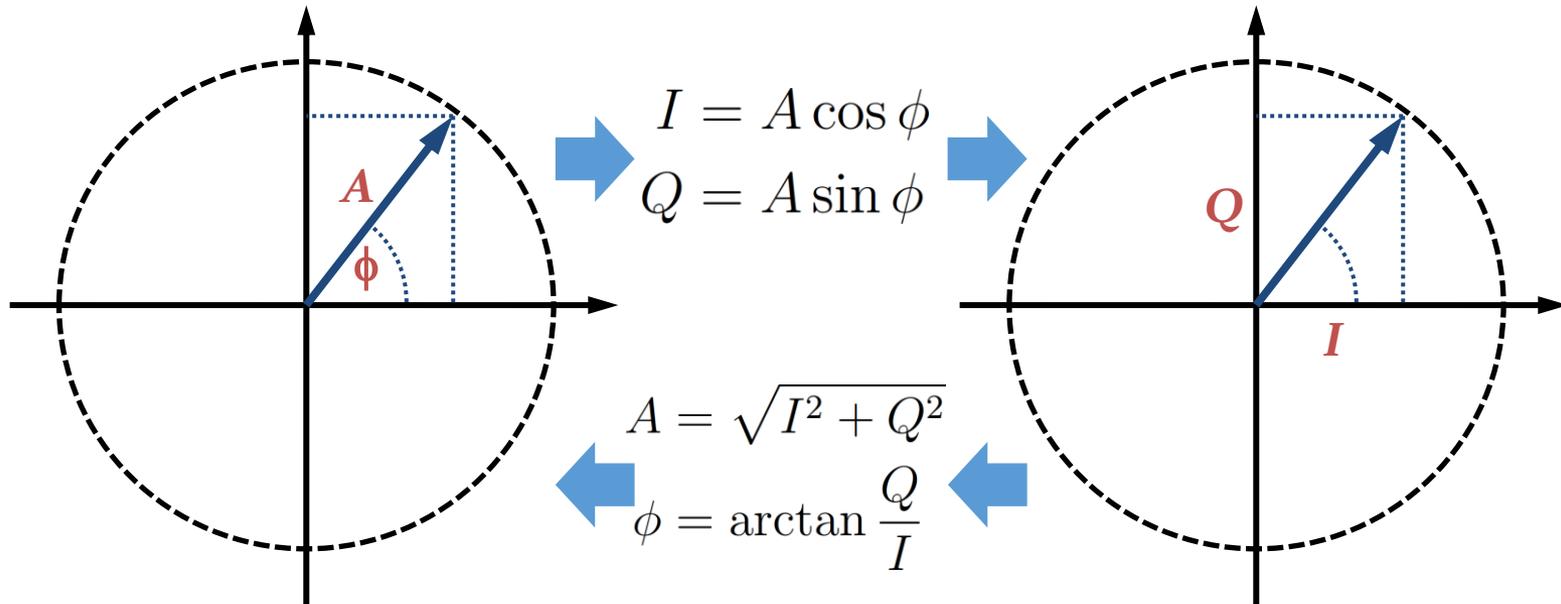
# I/Q representation of signals


- Any signal can be represented by amplitude  $A$  and phase  $\phi$



- **In phase,  $I$**  and **quadrature,  $Q$**  describe the same signal
- **Avoids phase discontinuities** at  $0, 2\pi, \dots$
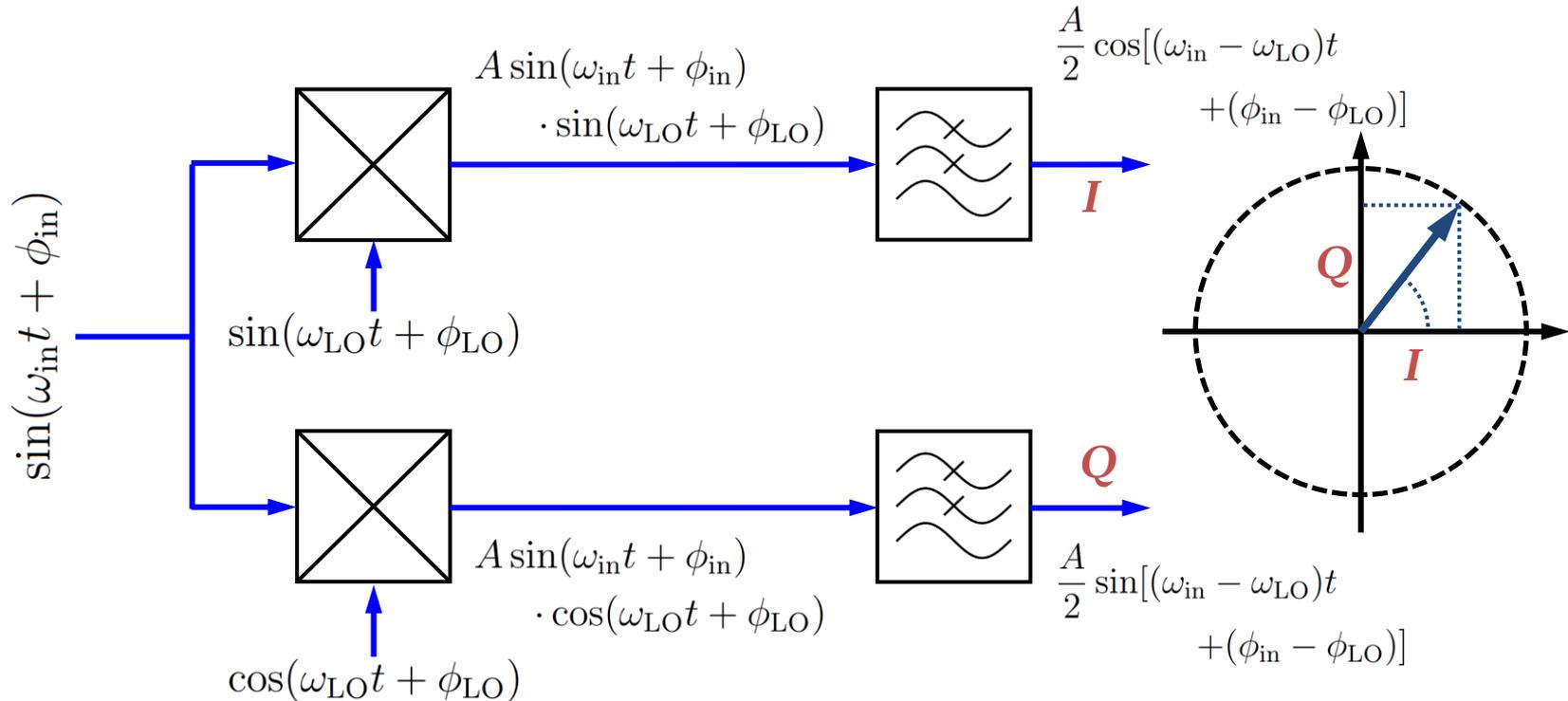
# Signal receivers

- Radio with listens to beam or cavity signals
- Listens to amplitude **and phase**




→ With  $\omega_{in} \approx \omega_{LO}$  input signal is down-converted to base-band

→ Resulting I/Q vector rotates slowly with  $\omega_{in} - \omega_{LO}$
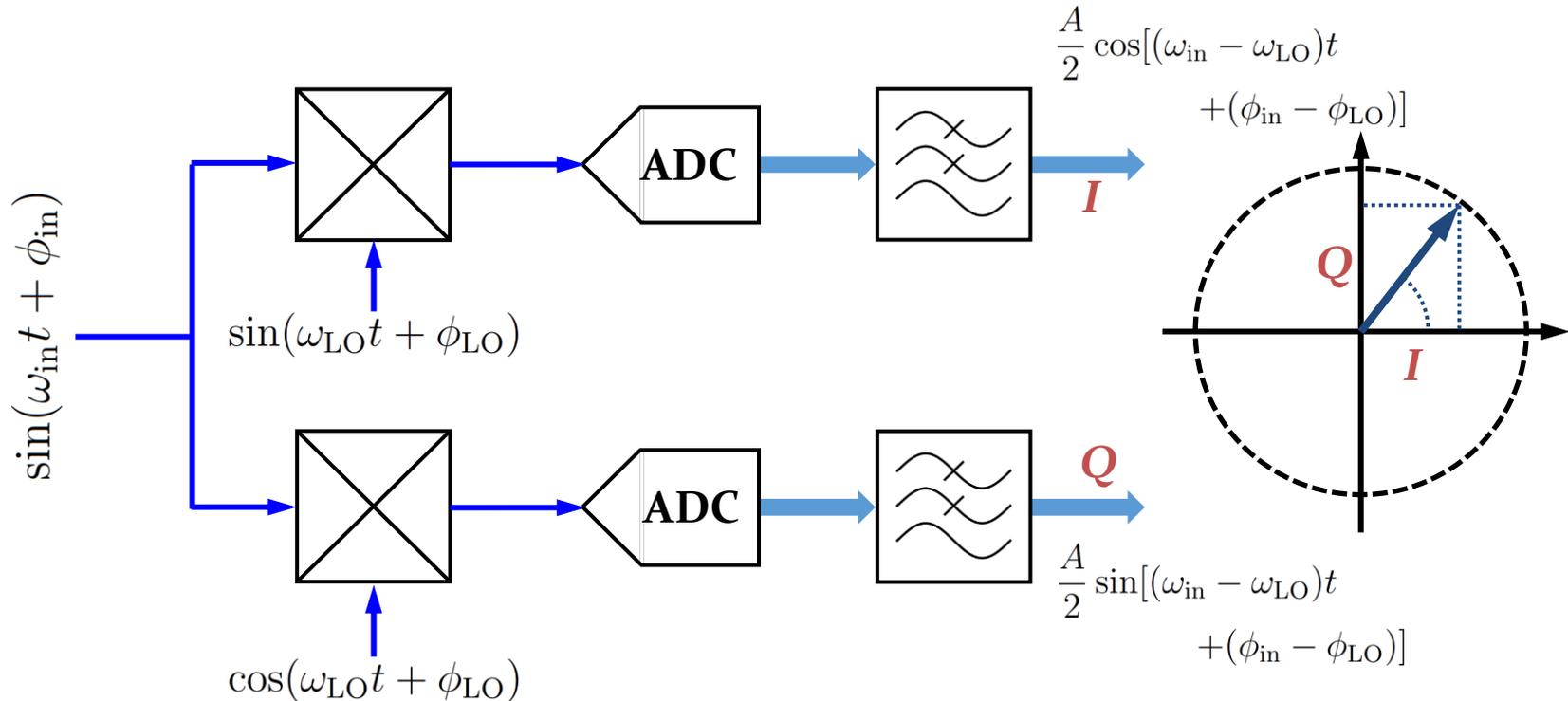
# Digital receivers


- No conceptual difference between analogue and digital
- Digitization can be performed at any level



- **Analog down-conversion** of I and Q, then **digital processing**
- **High input frequencies** beyond ADC sampling rates
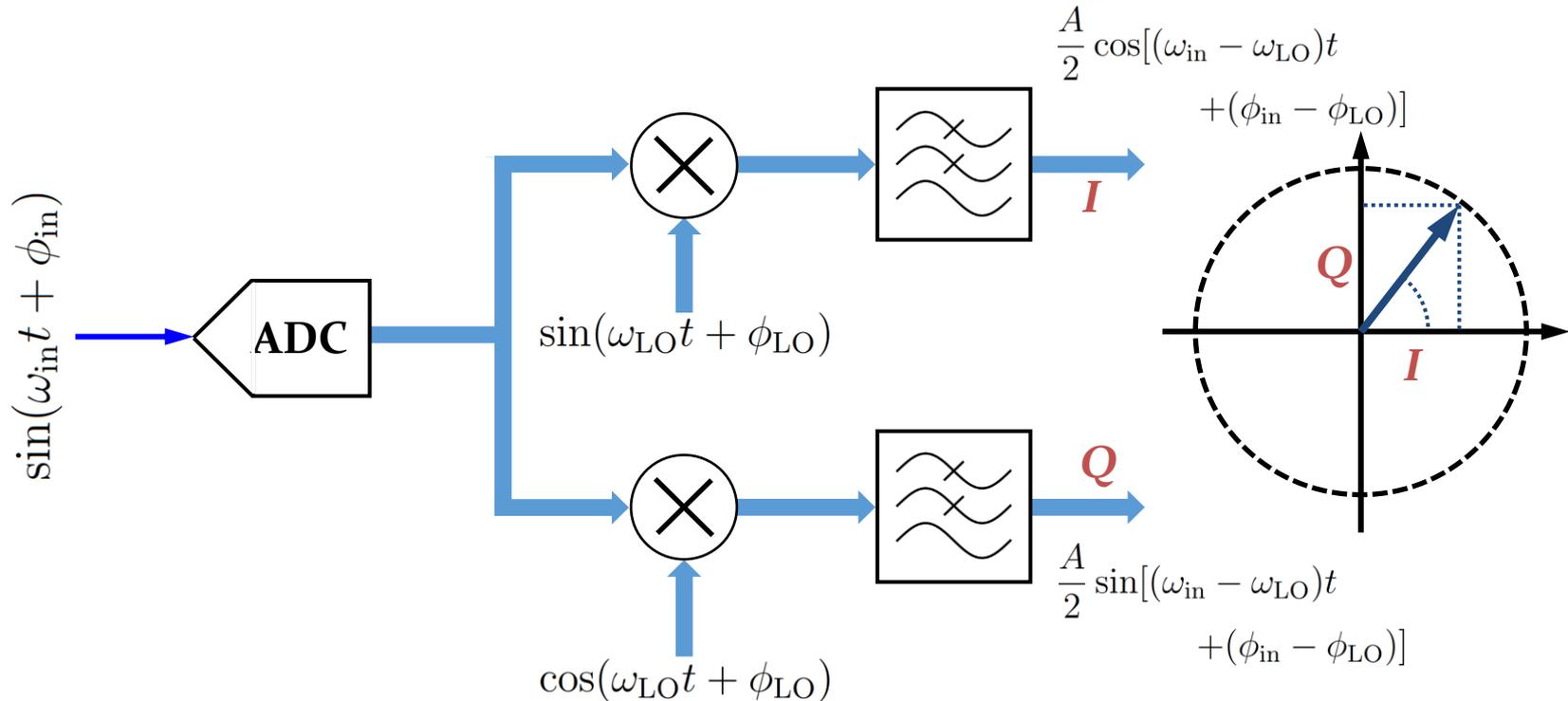
# Digital receivers

- No conceptual difference between analogue and digital
- Digitization can be performed at any level




- Analogue mixers become digital multipliers
- All digital receiver
- Theoretically **perfect I/Q symmetry**

# Vector modulator

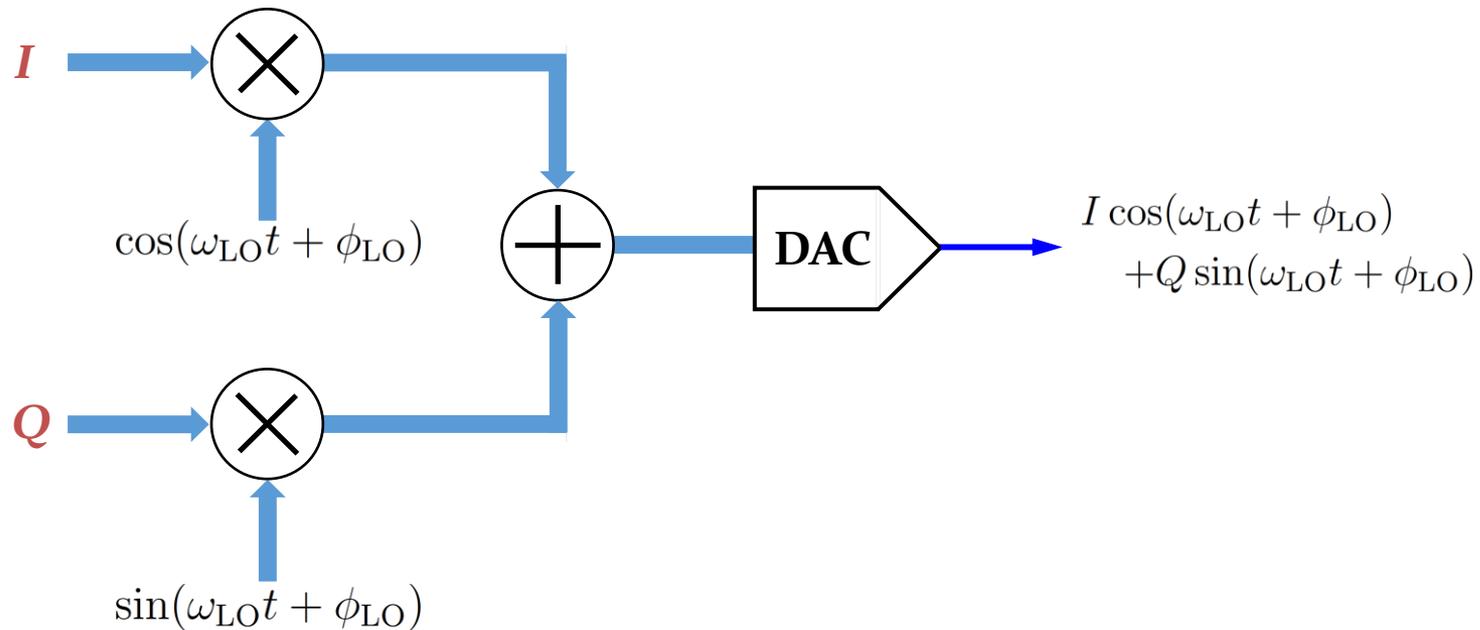
# Invers receiver: vector modulator

- Convert I/Q data into modulated RF signal


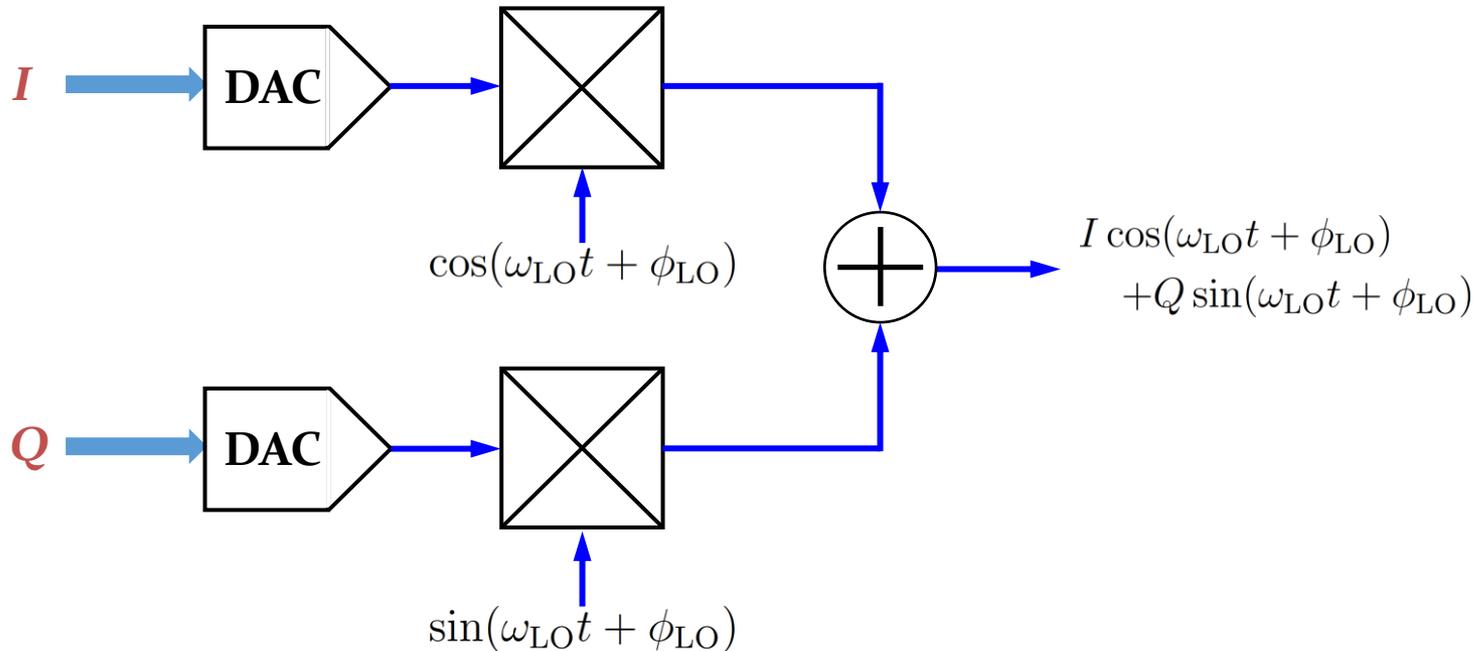
# Inverse receiver: vector modulator

- Convert I/Q data into modulated RF signal




→ Perfect **I/Q symmetry** difficult to achieve

→ Up-conversion of digital signal to a high RF frequency

# Beam phase loop
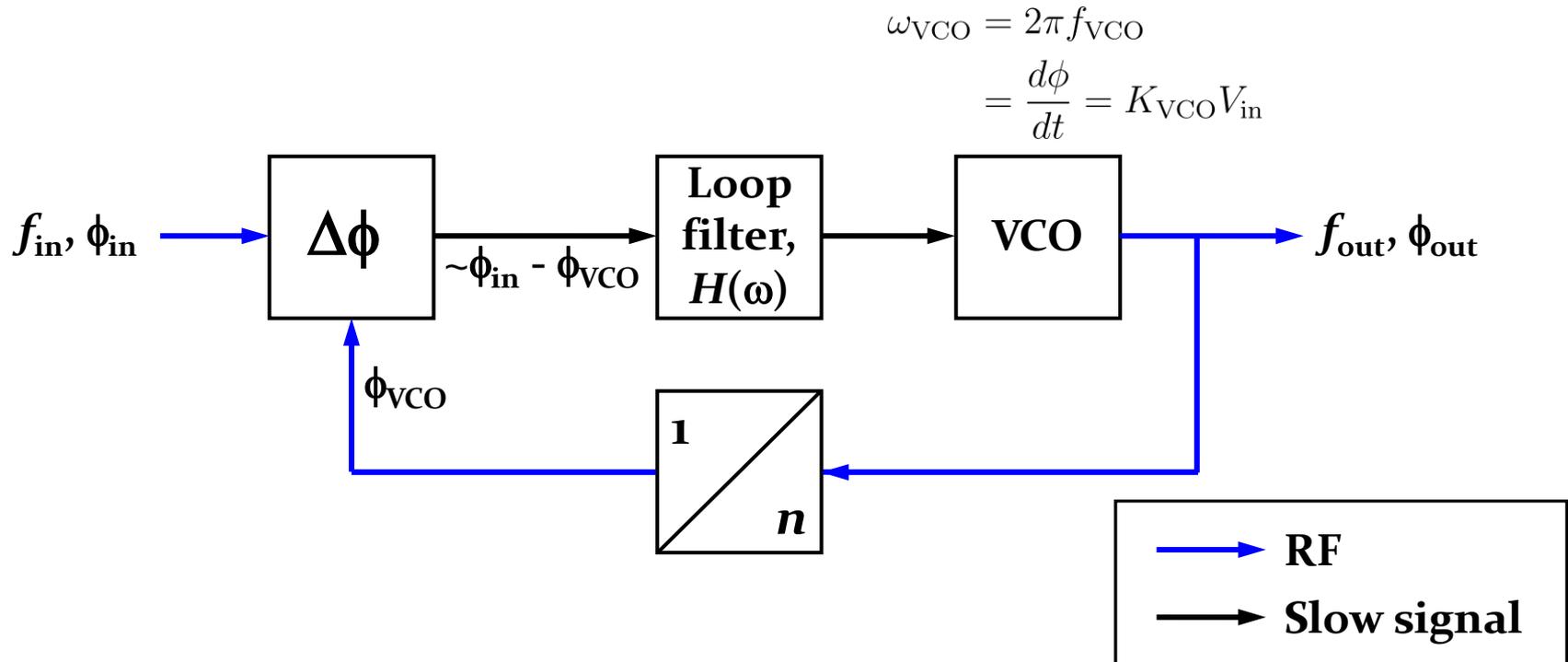
# Electronic phase-locked loop

- Frequency re-generation and multiplication
- Voltage controlled oscillator (VCO) locked in phase to input




→ Fixed phase relationship:

$$\phi_{\text{out}}/n - \phi_{\text{in}} = \text{const.}$$


→ Optional divider:

$$f_{\text{out}} = n \cdot f_{\text{in}}$$

# Beam phase loop

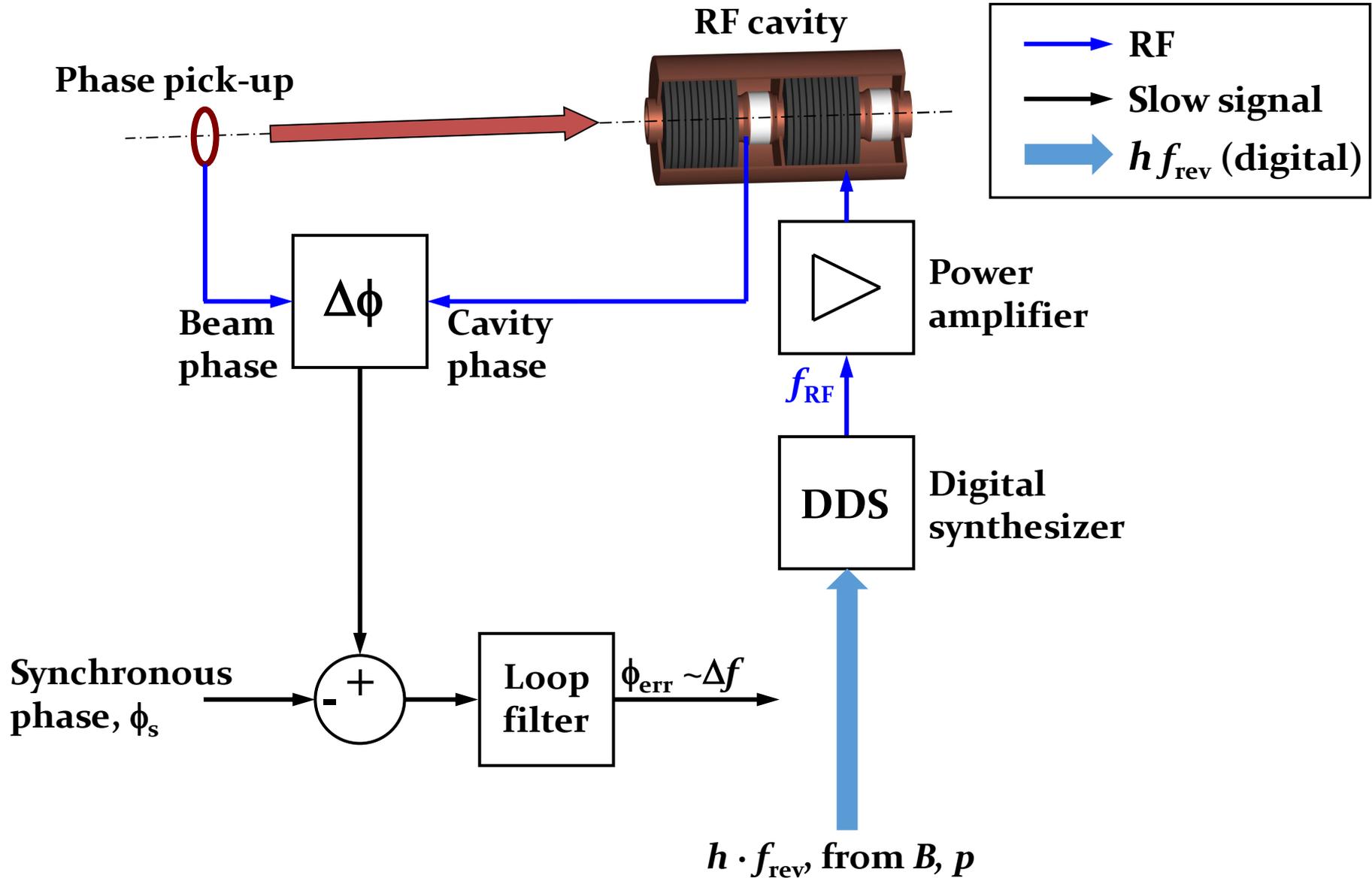


# Beam phase loop

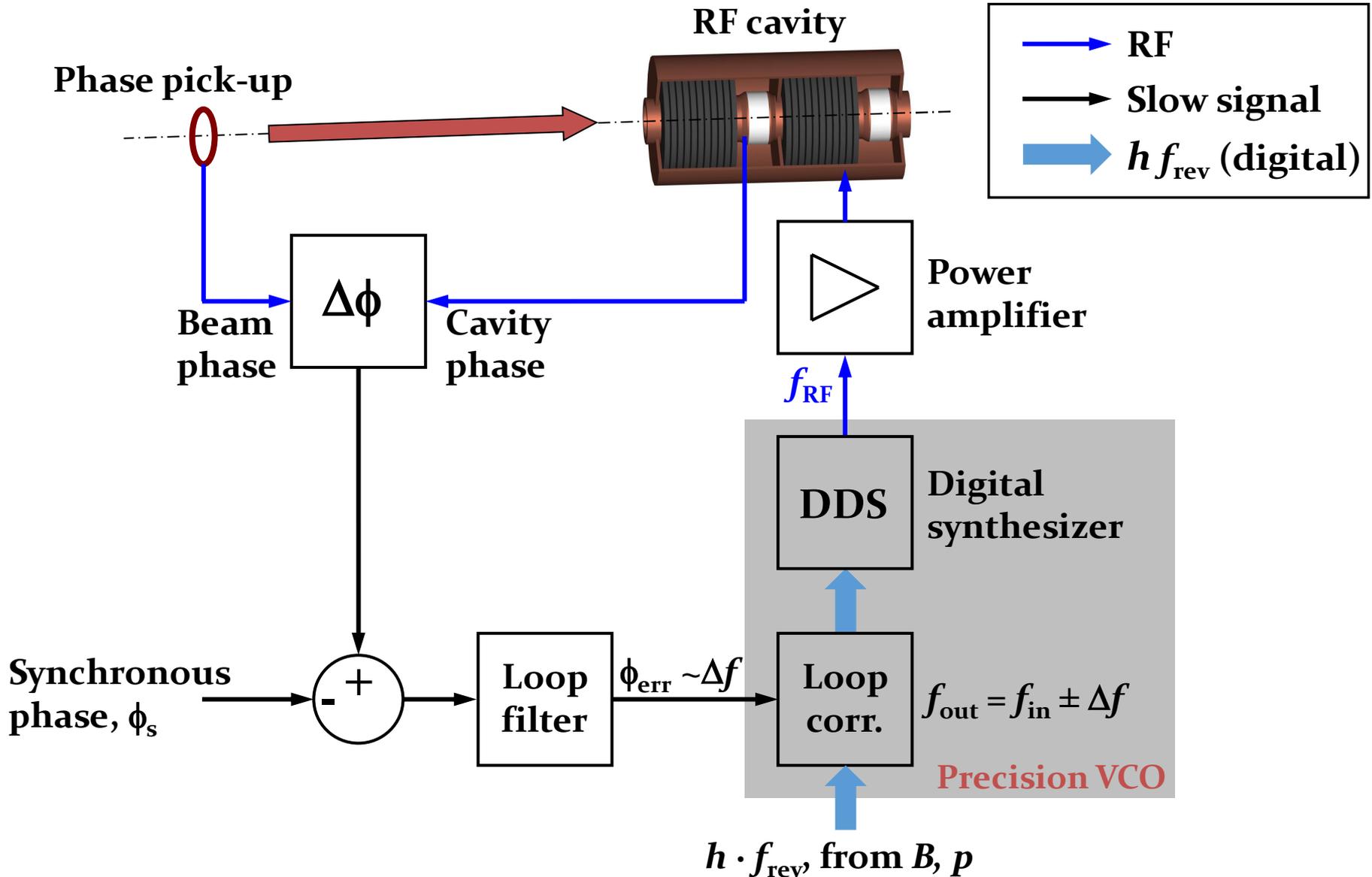

→ Phase-locked loop with beam phase as reference for RF system

# Beam phase loop

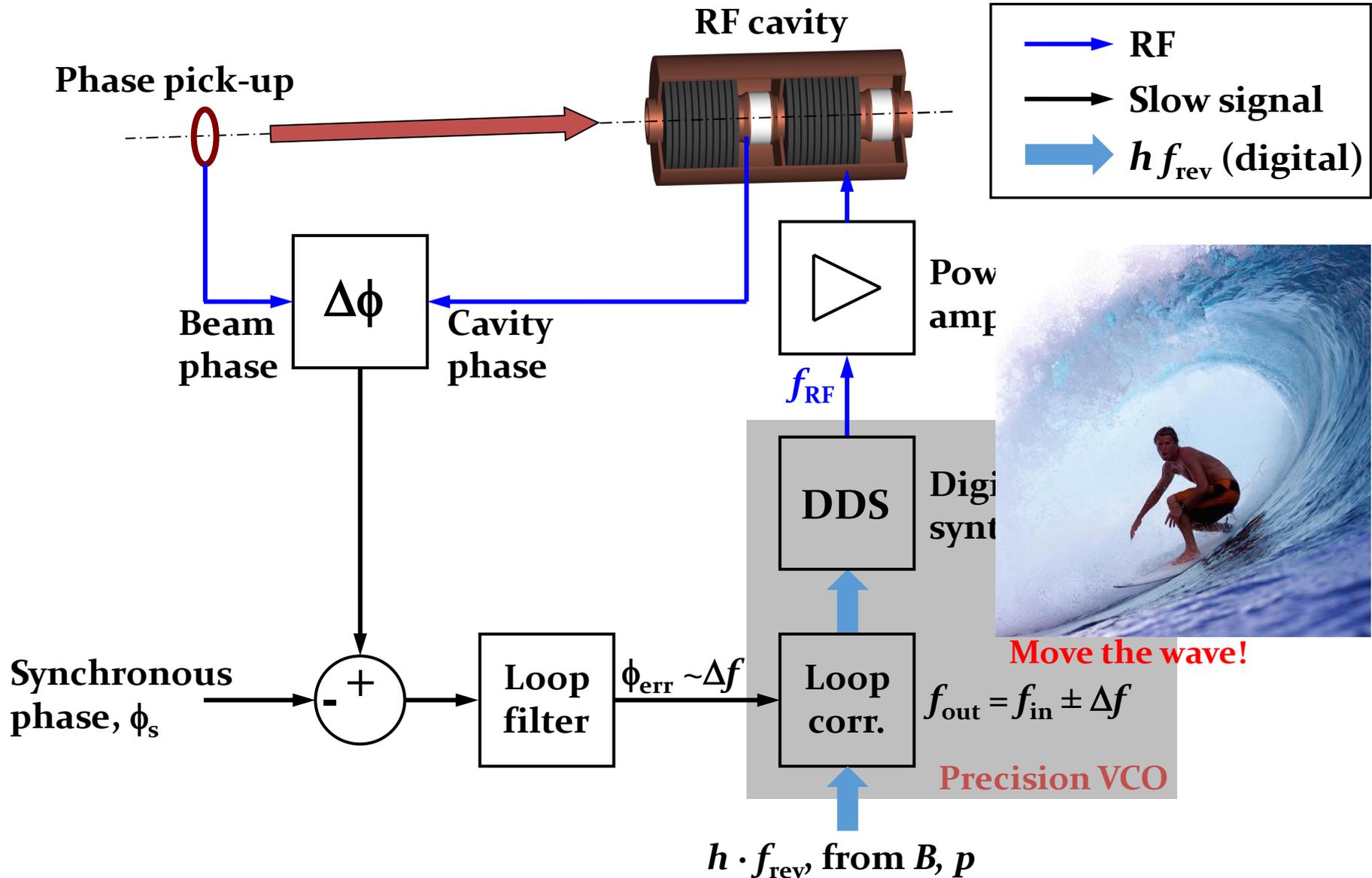


→ Fast control of RF frequency to cavities, **but no slow corrections**

# Effect of beam phase loop at injection

- **Example: Injection of a bunch from PS Booster into PS**


90° error, **phase loop off**

Turn# 0

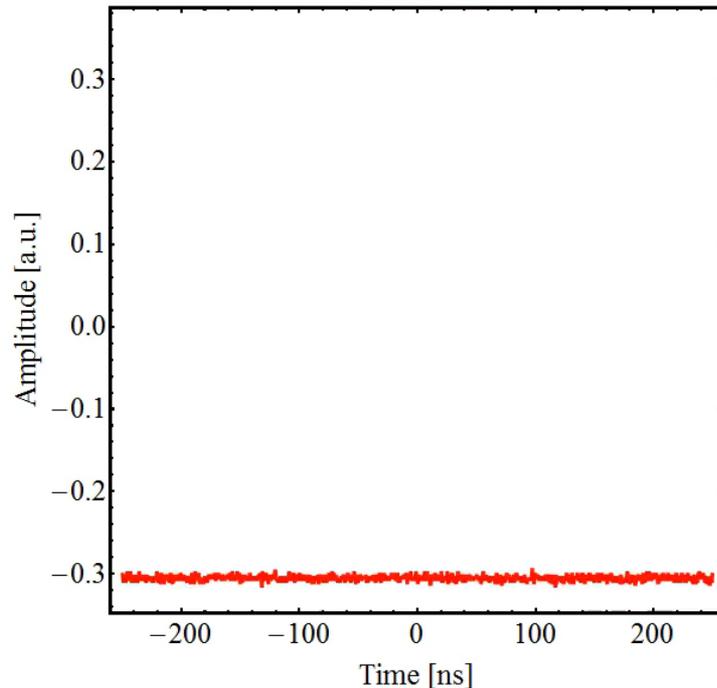

90° error, **phase loop on**



Turn# 0

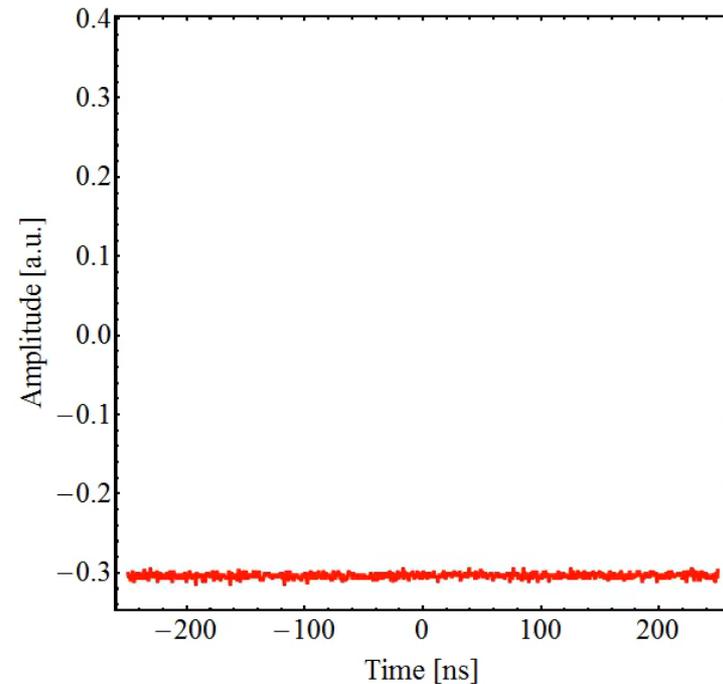

- **Essential in hadron accelerators to keep RF locked to beam**
- **How does this look like in longitudinal phase space?**
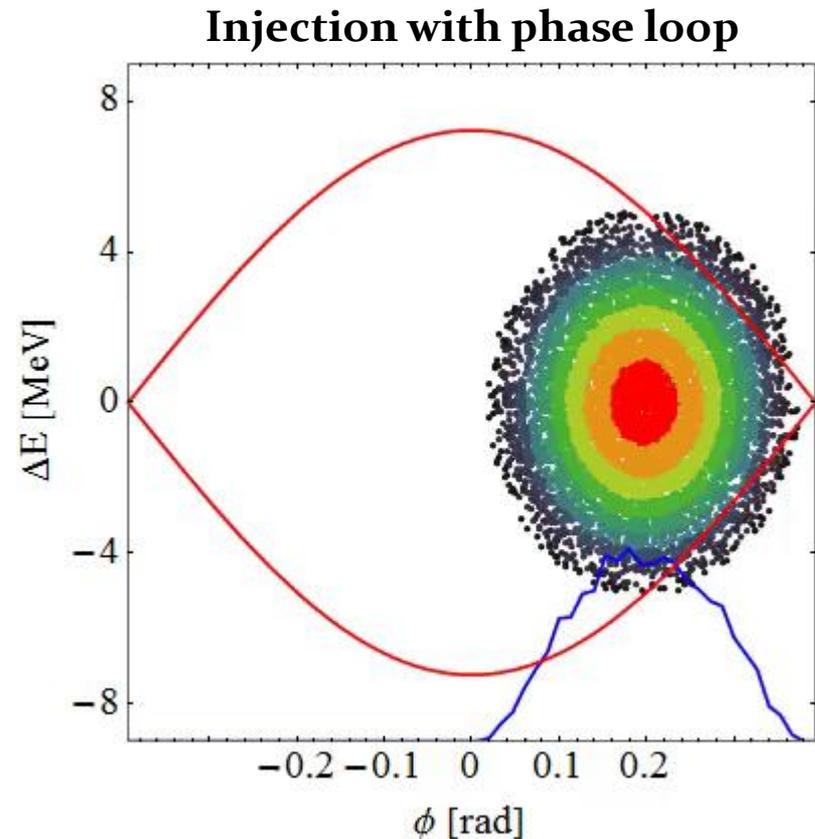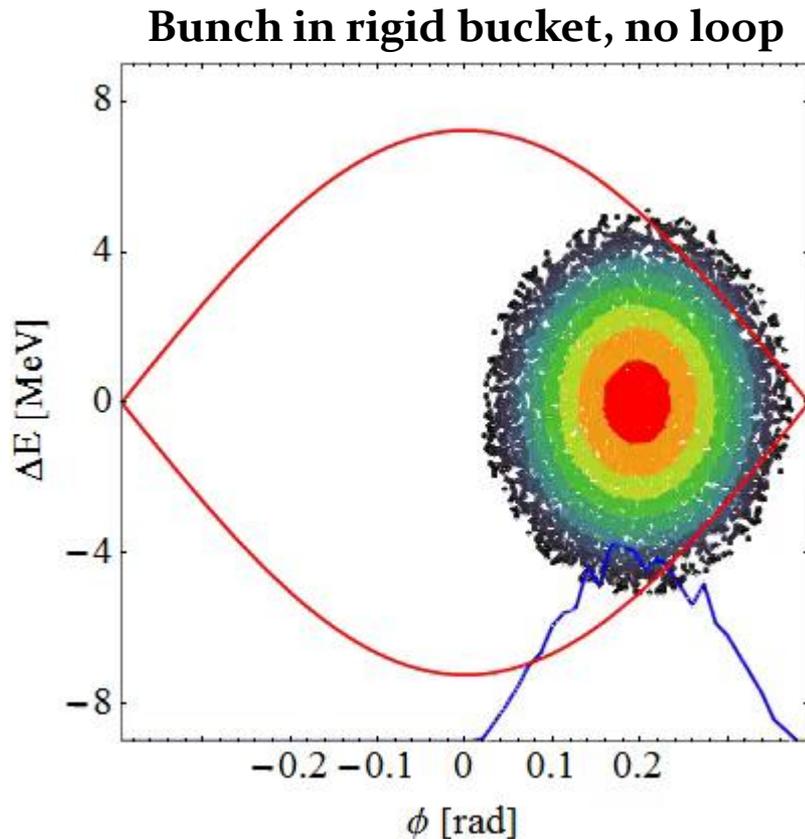
# Effect of beam phase loop at injection

→ Essential in hadron accelerators to keep RF locked to beam



- Even large transients (injection, transition) are controlled
- Only minor longitudinal perturbation


# Beam phase loop during acceleration

→ What happens with phase loop during acceleration?

→ During plateaus the phase between RF and beam is either  $0^\circ$  or  $180^\circ$


→ Fast phase changes well handled, but **need slow frequency correction**

→ **Radial or synchronization loop**

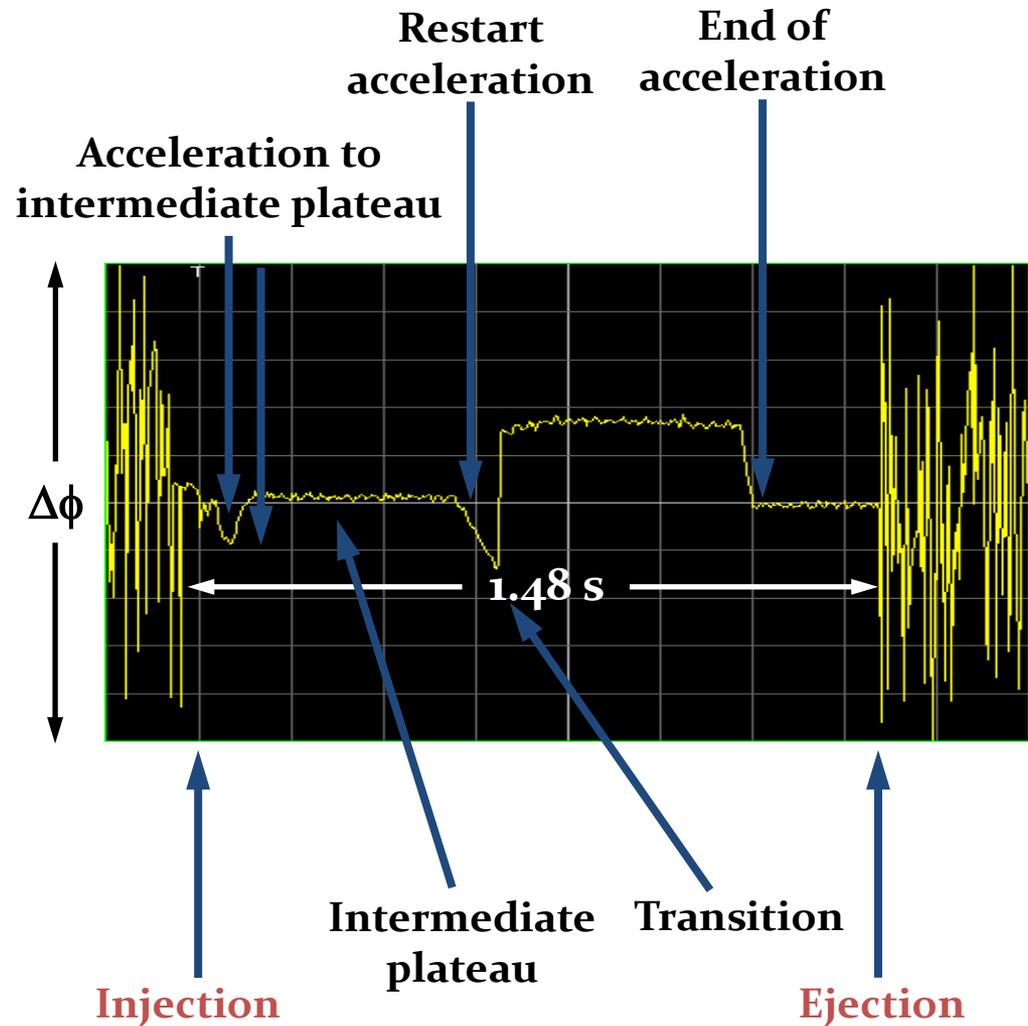

# Radial loop

# Radial loop

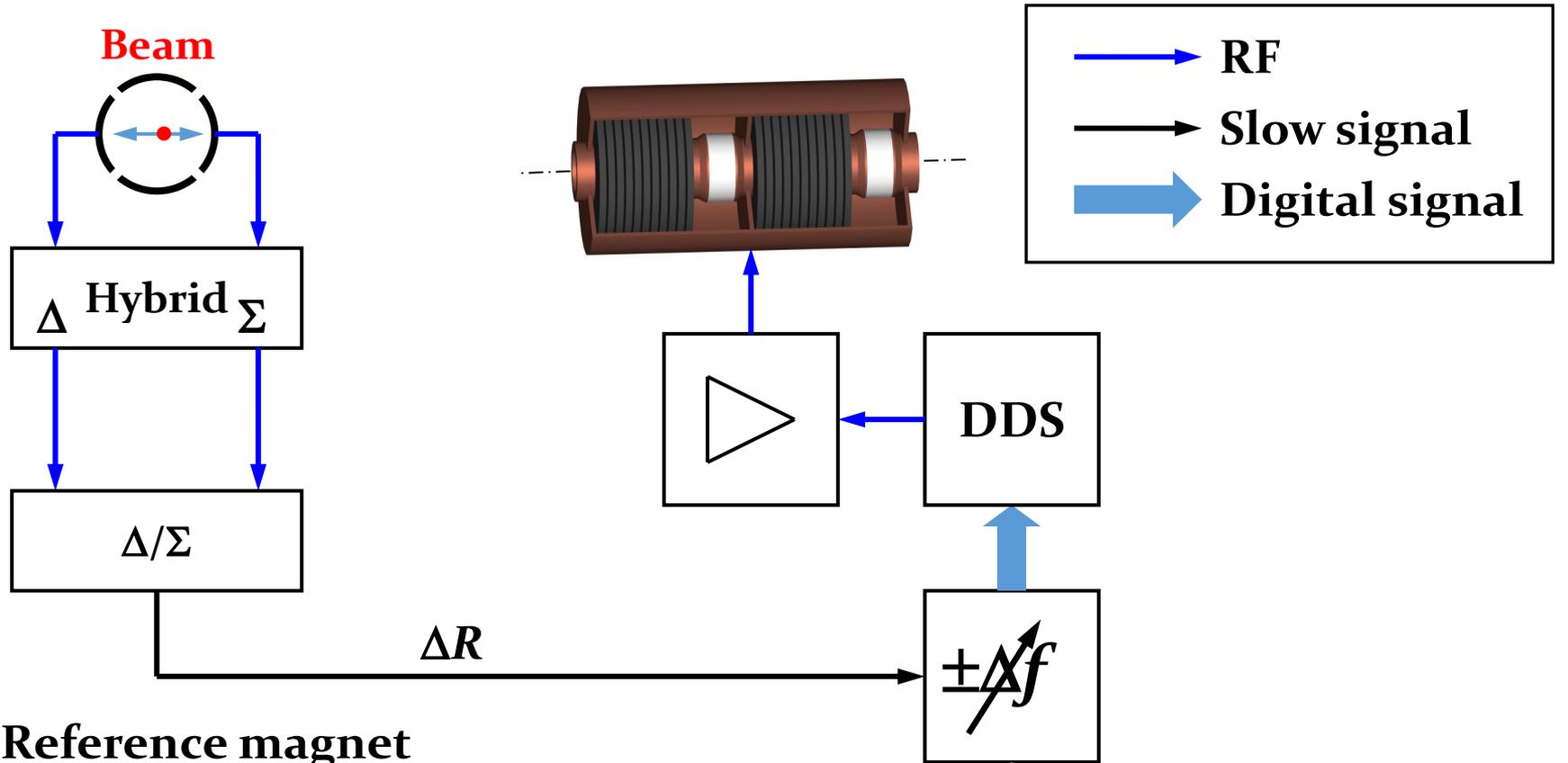

## Reference magnet



$B$   
 $f_{\text{rev}}$   
 Frequency program

$h \cdot f_{\text{rev}}$

→ Slow correction of average RF frequency

# Radial loop

- Slow correction of RF frequency to keep beam centred


Why needed at all with arbitrary precision synthesizers driving the RF system?

→ At transition energy

- Longer path of higher energy particle compensated by higher velocity
- No revolution frequency change for energy offset

$$\frac{\Delta R}{R} = \frac{\gamma^2}{\gamma_{tr}^2 - \gamma^2} \frac{\Delta f}{f}$$


→ Need beam-based frequency correction

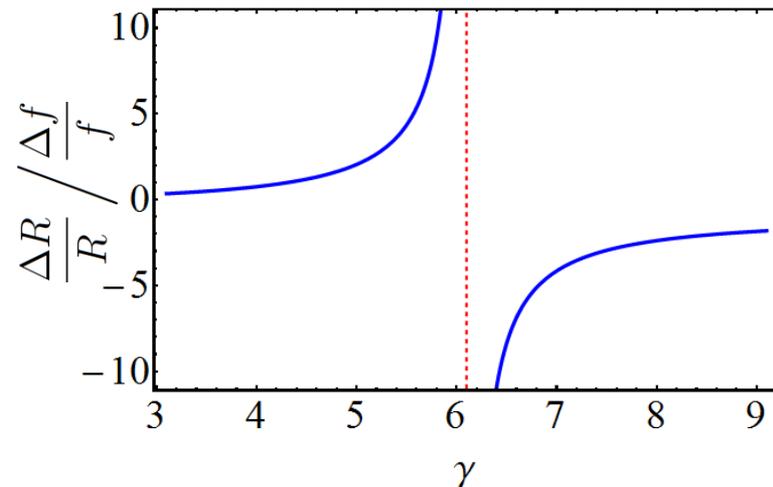

# Synchro(nization) loop



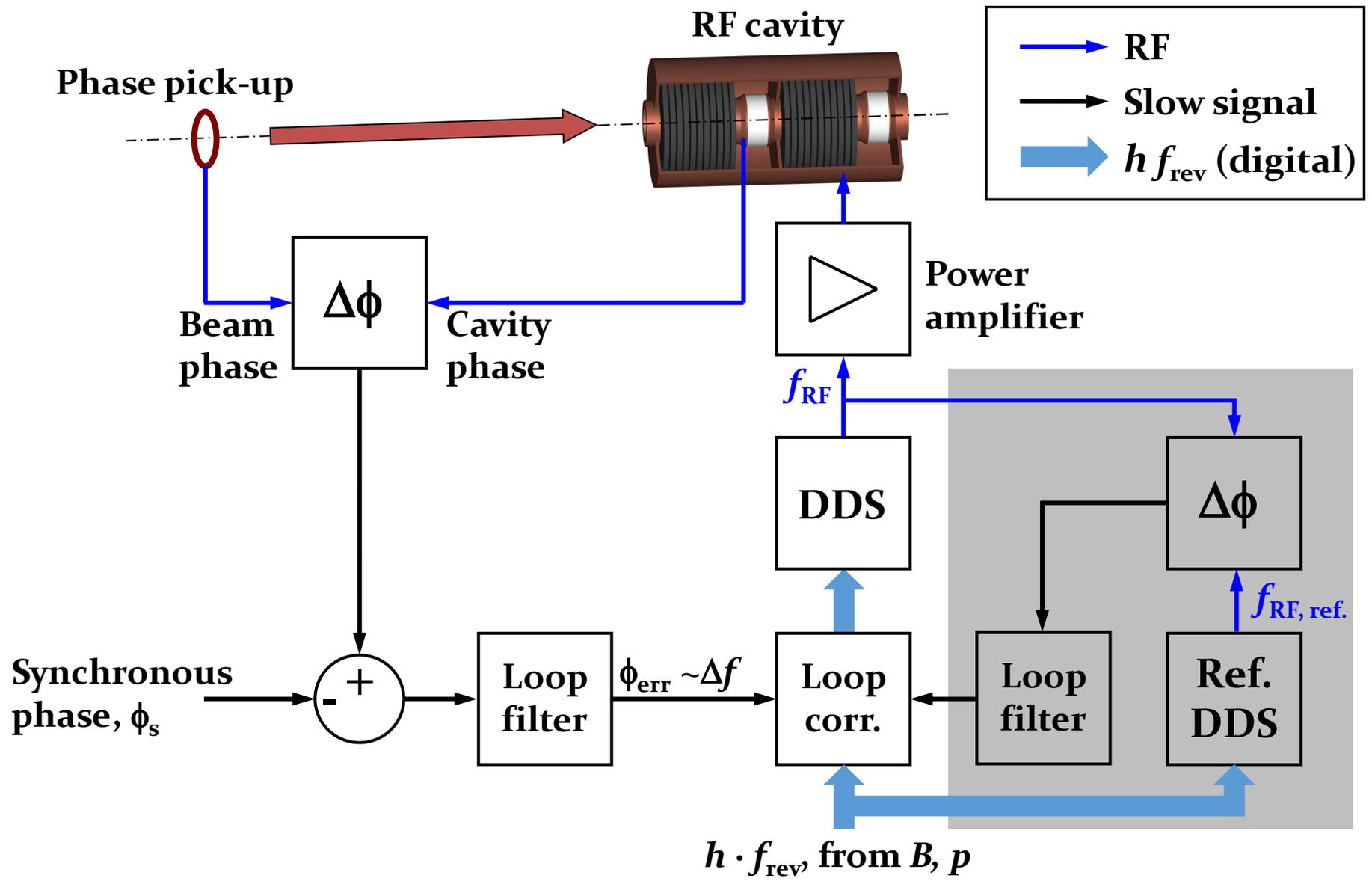
# Synchronization loop, **internal** reference



→ Avoids **noise from radial detection** when not crossing transition
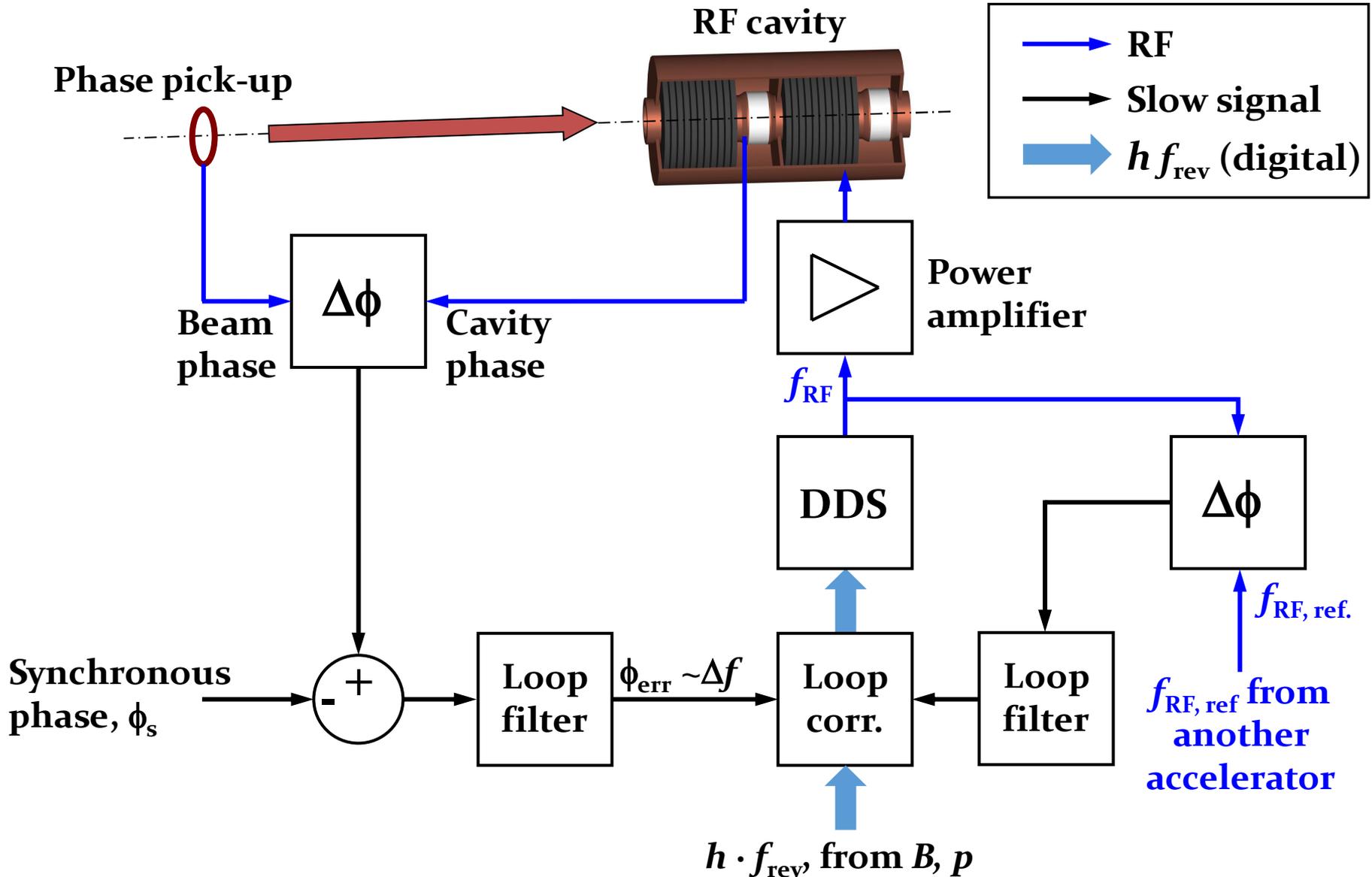
# Synchronization loop, external reference




→ Synchronize between accelerators for **transfer**

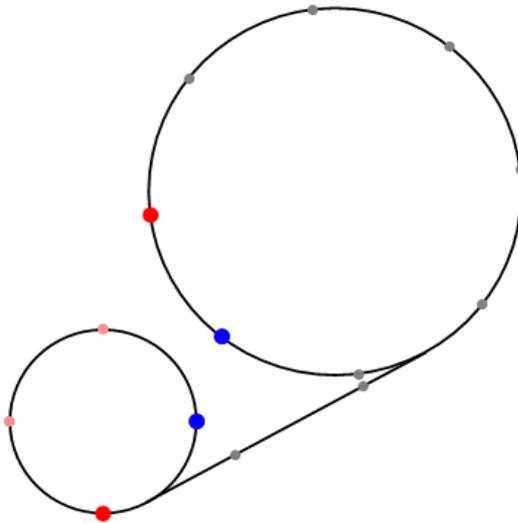
# Before synchronization

- Simple test case of circumference ratio 2:  $C_2 = 2C_1$

Target accelerator is  
master at transfer



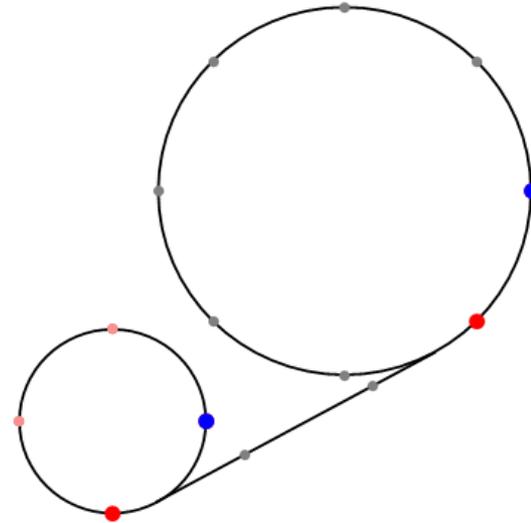Target accelerator is  
master at transfer




→ Synchronize both accelerator to force:  $f_{\text{rev},1} = 2f_{\text{rev},2}$
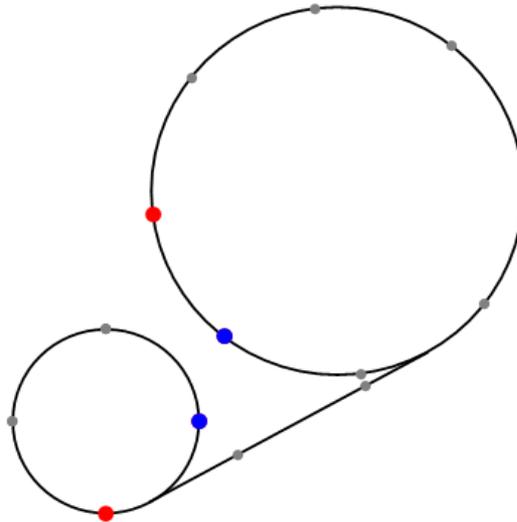
# After synchronization

- Simple test case of circumference ratio 2:  $C_2 = 2C_1$

Source or target accelerator  
is **master** at transfer



- Revolution frequencies coupled:  $f_{\text{rev},1} = 2f_{\text{rev},2}$
- **Ready to extract during every turn of the target accelerator**

# Summary

- RF system parameters
- Parameters of RF cavities
- Power amplifier
- **Local feedbacks**
  - **Direct and 1-turn delay feedback**
- **Building blocks of low-level RF systems**
  - **Phase comparison, RF sources and receivers**
- **Basic global feedback loops**
  - **Beam phase, radial and synchronization loops**
  - **Make the beam feel comfortable!**

# **A big Thank You**

**to all colleagues providing support, material and feedback**

**Maria-Elena Angoletta, Philippe Baudrenghien, Thomas Bohl,  
Giorgia Favia, Jörn Jacob, Erk Jensen, John Molendijk,  
Eric Montesinos, Gerry McMonagle, Mauro Paoluzzi,  
Damien Perrelet, Bernhard Schriefer, Lukas Stingelin,  
Fumihiko Tamura, Frank Tecker, Daniel Valuch and many  
more...**

**Thank you very much  
for your attention!**

# References

- D. Boussard, Design of a Ring RF System, CERN SL/91-2 (RFS, rev.), 1991, <http://cds.cern.ch/record/1023436/files/CM-P00065157.pdf>
- E. Montesinos, Accelerators for Medical Applications - Radio Frequency Powering, CERN-2017-004-SP, <http://cds.cern.ch/record/2315172/files/1804.08535.pdf>
- R. Garoby, Low level rf building blocks, CERN-1992-003, 1991, <http://cds.cern.ch/record/225609/files/CM-P00059483.pdf>
- J. W. Wang, G. A. Loew, Field Emission and RF Breakdown in High-Gradient Room-Temperature Linac Structures, SLAC-PUB-7684, 1997, <http://www.slac.stanford.edu/cgi-wrap/getdoc/slac-pub-7684.pdf>
- W. D. Kilpatrick, Criterion for vacuum sparking designed to include both rf and dc, Rev. Sci. Instrum. 28 (1957), 1957, <http://inspirehep.net/record/44645>

# Normalized Hamiltonian representation

- **For a single harmonic RF system**

$$H(\phi, \dot{\phi}) = \frac{1}{2} \dot{\phi}^2 + \frac{\omega_s^2}{\cos \phi_S} [\cos \phi_S - \cos \phi + (\phi - \phi_S) \sin \phi_S]$$

**with**  $\phi = \phi_S + \Delta\phi$  **it becomes**

$$H(\Delta\phi, \dot{\phi}) = \frac{1}{2} \dot{\phi}^2 + \frac{\omega_s^2}{\cos \phi_S} [\cos \phi_S - \cos(\phi_S + \Delta\phi) - \Delta\phi \sin \phi_S]$$


**using**  $\cos(\phi_S + \Delta\phi) = \cos \phi_S \cos \Delta\phi - \sin \phi_S \sin \Delta\phi$

$$\simeq \cos \phi_S \left( 1 - \frac{1}{2} \Delta\phi^2 \right) - \sin \phi_S \Delta\phi$$

**this simplifies to**  $H(\Delta\phi, \dot{\phi}) \simeq \frac{1}{2} \dot{\phi}^2 + \frac{1}{2} \omega_s^2 \Delta\phi^2$
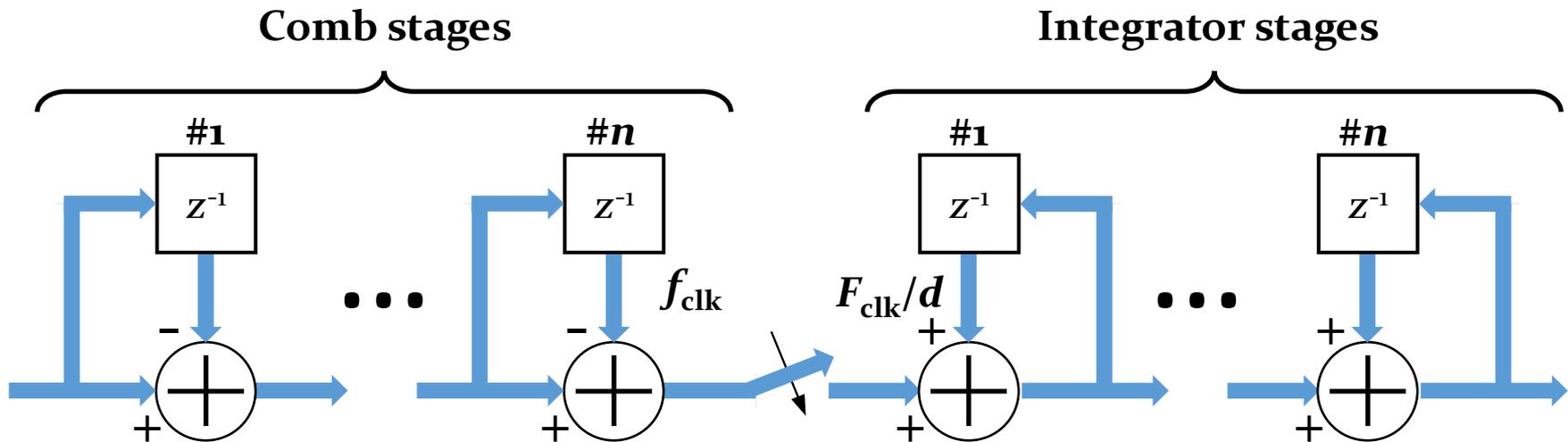
# Cascaded integrator-comb filter (CIC)

- Efficient implementation of low pass filter
- Standard form with sampling rate decimation:  $f_{\text{clk}} \rightarrow f_{\text{clk}}/d$



$$H(z) = \left( \frac{1 - z^{-d}}{1 - z^{-1}} \right)^n \quad \begin{array}{l} n: \text{filter order} \\ d: \text{decimation ratio} \end{array} \quad z = e^{2\pi i \cdot f / f_{\text{clk}}}$$

- Easy to implement in programmable logic: **no multipliers**
- **Only adders and shift registers**

# Cascaded integrator-comb filter (CIC)

Why particularly interesting for circular accelerators?


- Choose clock frequency,  $f_{\text{clk}} = 2^m f_{\text{rev}}$  and decimation  $d = 2^m$
- Notches at all multiples of  $f_{\text{rev}}$  **except zero**
- Linear phase  $\phi(f)$  → filter behaves like a constant delay

Example:

$$f_{\text{clk}} = 128f_{\text{rev}},$$

$$d = 128,$$

$$n = 3$$

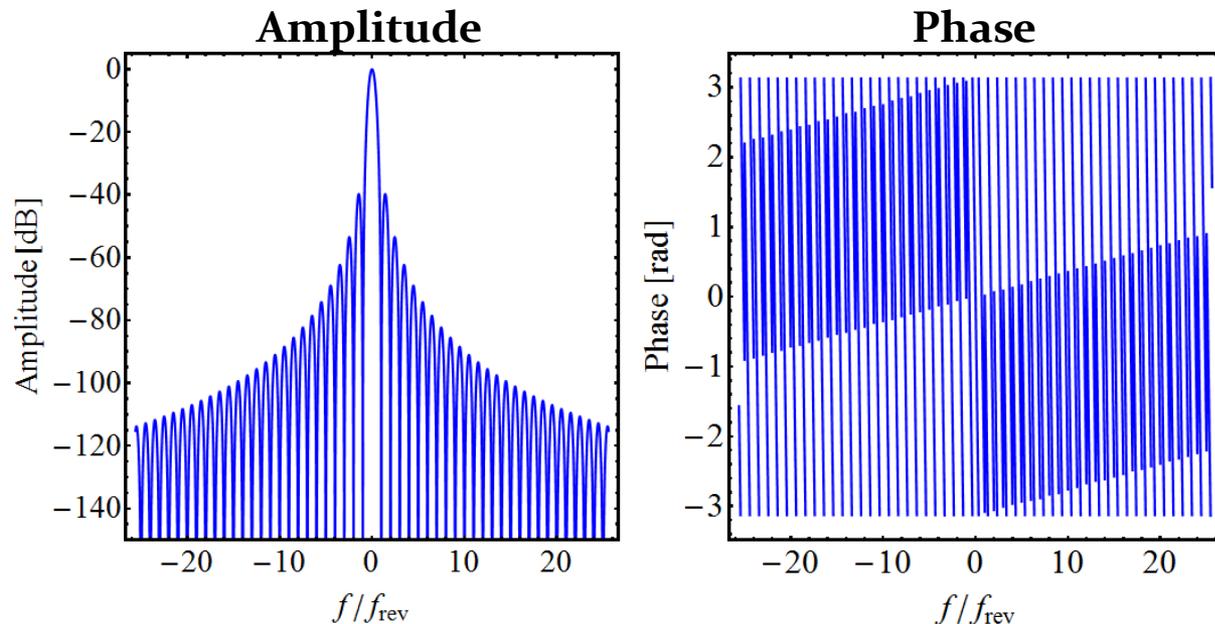

**Ideal low-pass filter in digital receivers**


→ Filter selected multiple of  $f_{\text{rev}}$  while suppressing all others

# Transmission of reference signals

- Thermal drift of long coaxial cables or optical fibres

- Thermal coefficient of delay:
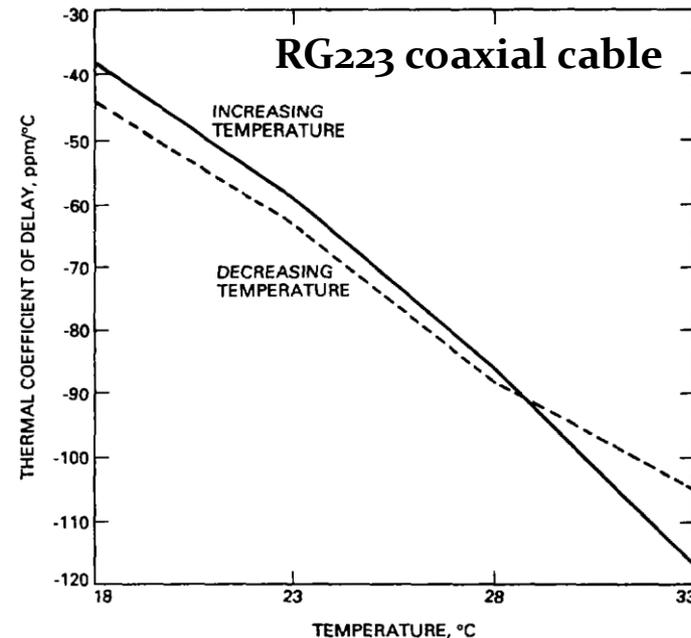
$$\text{TCD} = \frac{\Delta\tau}{\tau} \cdot \frac{1}{\Delta T} = \frac{\Delta\phi}{\phi} \cdot \frac{1}{\Delta T}$$



- Example: 2 km long RG223 cable with ~10 μs delay
  - ΔT of only 1° C (room temperature) changes delay by ~0.5 ns
  - 1.8° at 10 MHz (CERN PS), but 73° at 400 MHz (LHC)
- Optical fibres are typically 10...100 times more stable
- What to do if this is still not sufficient?

# Simple synchronization process

1. Move beam to off-momentum ( $B$  const.):  $\frac{df}{f} = \frac{\gamma_{tr}^2 - \gamma^2}{\gamma^2 \gamma_{tr}^2} \frac{dp}{p}$ 
  - Well defined frequency difference between accelerators
2. Measure azimuth error, when beam at correct azimuth
  - Close synchronization loop
  - Moves beam to ref. momentum

