

A CCD Based Vertex Detector

Konstantin Stefanov

STFC Rutherford Appleton Laboratory

On behalf of the Linear Collider Flavour Identification (LCFI) Collaboration

(Bristol U, Edinburgh U, Glasgow U, Liverpool U, Nijmegen U, Oxford U, RAL)


❖ Introduction

❖ Vertex Detector R&D at LCFI

- Column-Parallel CCDs
- In-situ Storage Image Sensors
- Low Mass Mechanical Support

❖ Conclusion

Introduction

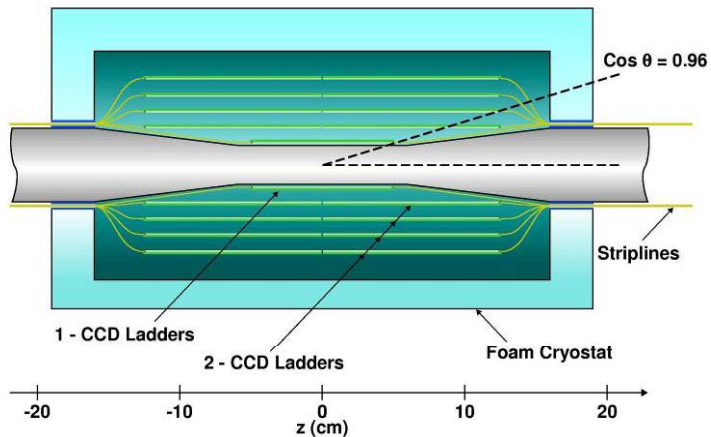


What is required for the vertex detector at ILC:

- Excellent point resolution ($3.5 \mu\text{m}$), small pixel size = $20 \mu\text{m}$, close to IP
- Low mass ($\leq 0.1\% X_0$ per layer), low power dissipation
- Fast (low occupancy) readout – **challenging, two main approaches**
- Tolerates Electro-Magnetic Interference (EMI)


What LCFI has done so far:

- Made 2 generations of Column Parallel CCDs: CPC1 and CPC2
- Proof-of-principle In-situ Storage Image Sensor (ISIS) designed and tested
- Bump bonded CMOS readout chips for CPC1 and CPC2
- Driver chip for CPC2 designed and manufactured
- Extensive tests of stand-alone devices and hybrid bump bonded assemblies
- Studies of low mass support structures

Our Second Generation CPCCD : CPC2

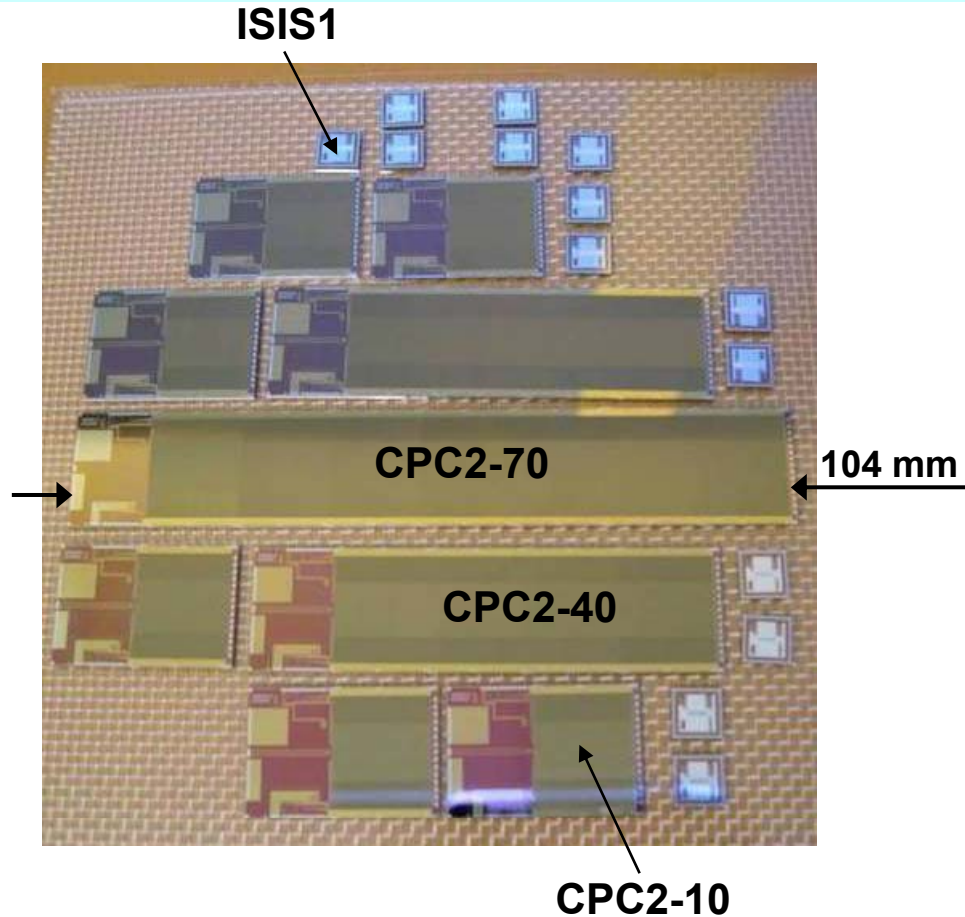

Busline-free CPC2

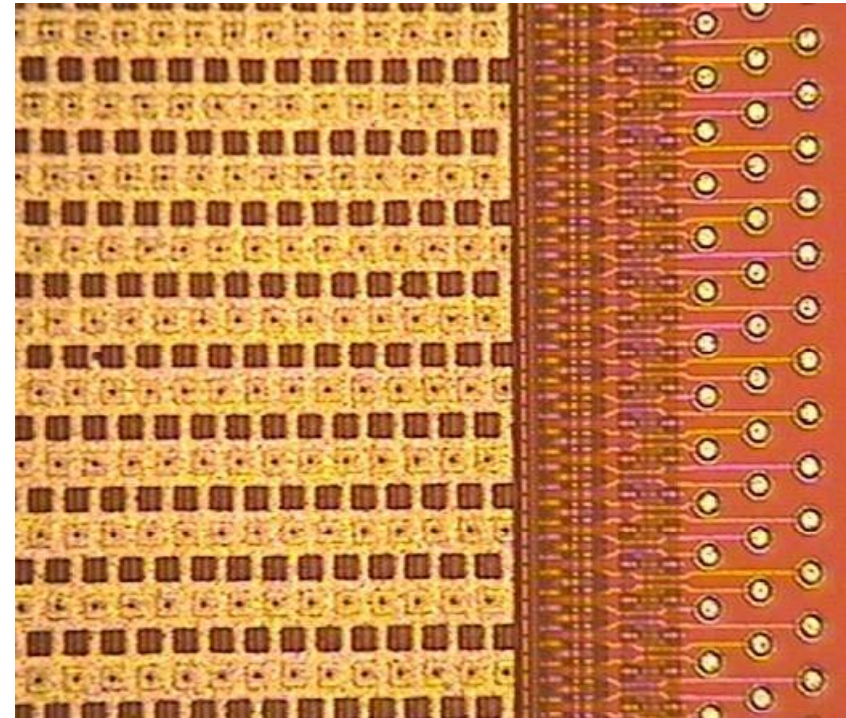


- CPC2 wafer (100 Ω .cm/25 μ m epi and 1.5k Ω .cm/50 μ m epi)
- Low speed (single level metallisation) and high speed versions



High speed (busline-free) devices with 2-level metal clock distribution:

- ❖ The **whole image area** serves as a distributed busline
- ❖ Designed to reach 50 MHz operation (needed to keep the occupancy < 1% in L1)



CPC2 – High Speed in Stand-alone Mode

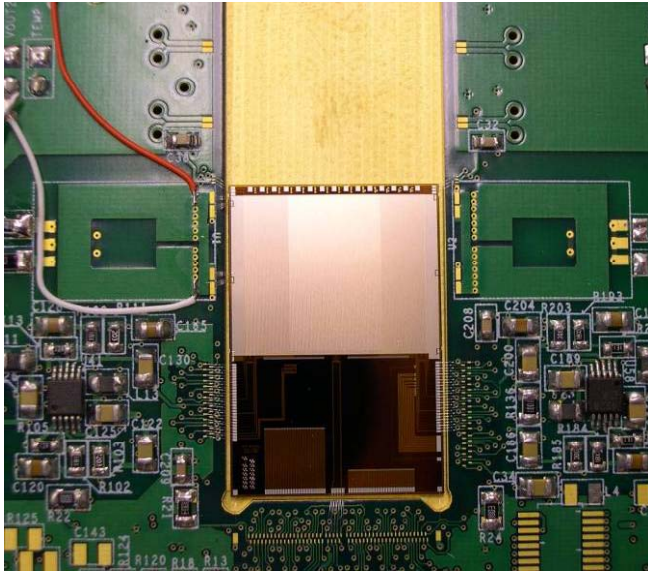

- Initially using a PCB transformer and a RF amplifier to clock the CCD
- **Busline-free CPC2-10 working at 45 MHz, important milestone**
- Numerous parasitics diminish transformer performance, high noise from the RF amplifier
- CMOS driver chip used as well
- Getting closer to prototype ladder

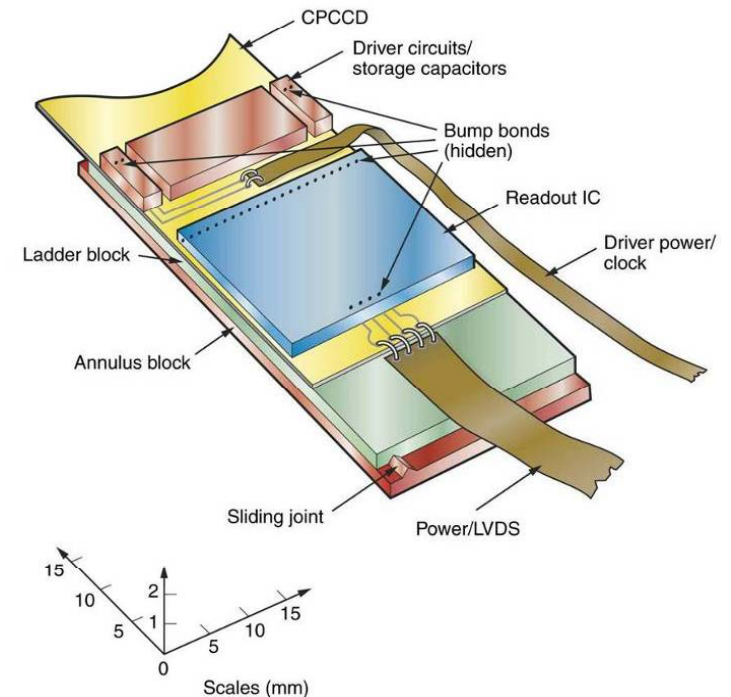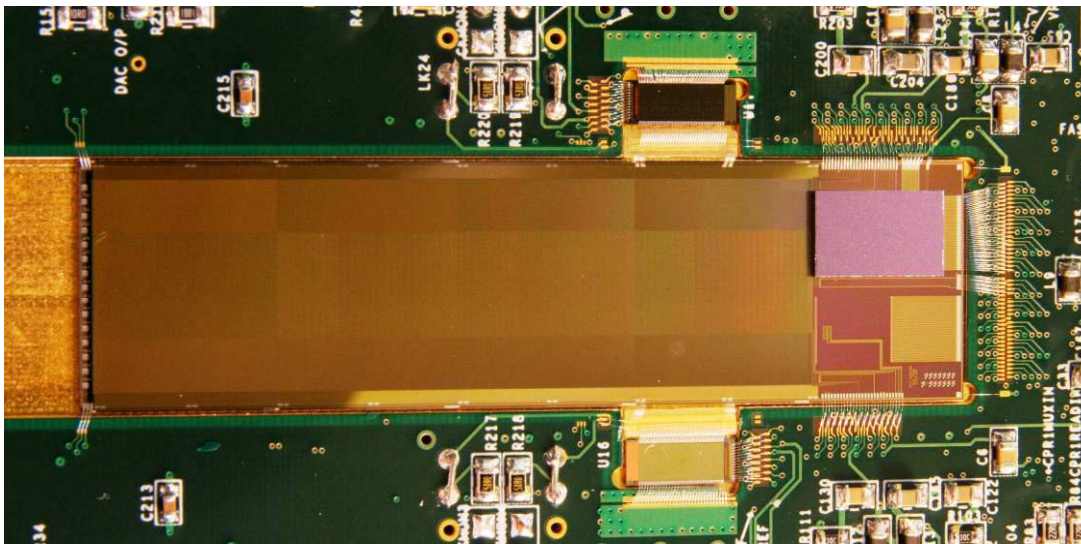


CPC2-10 BLF with CPD1 Clocking at 10 MHz

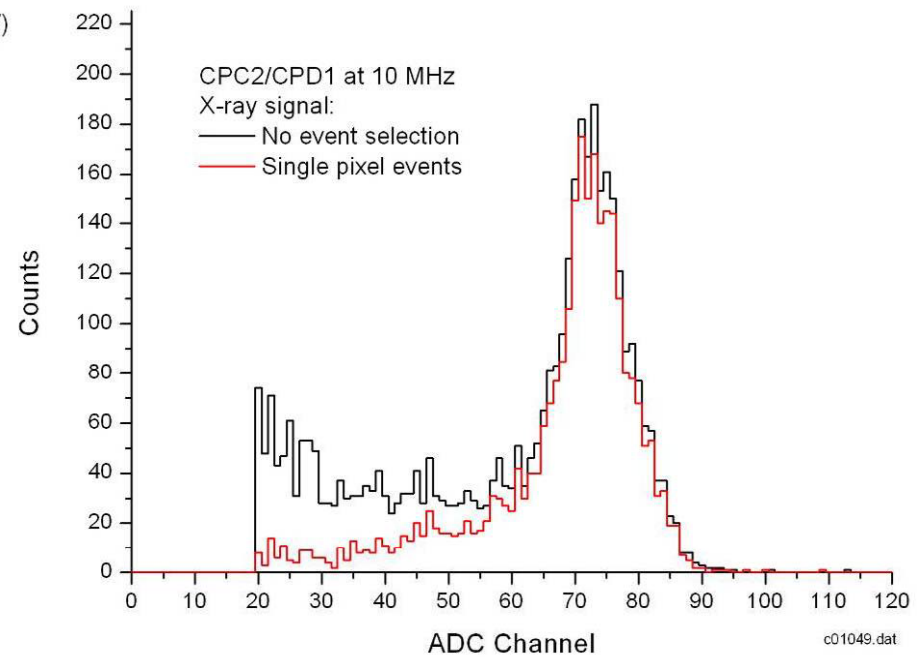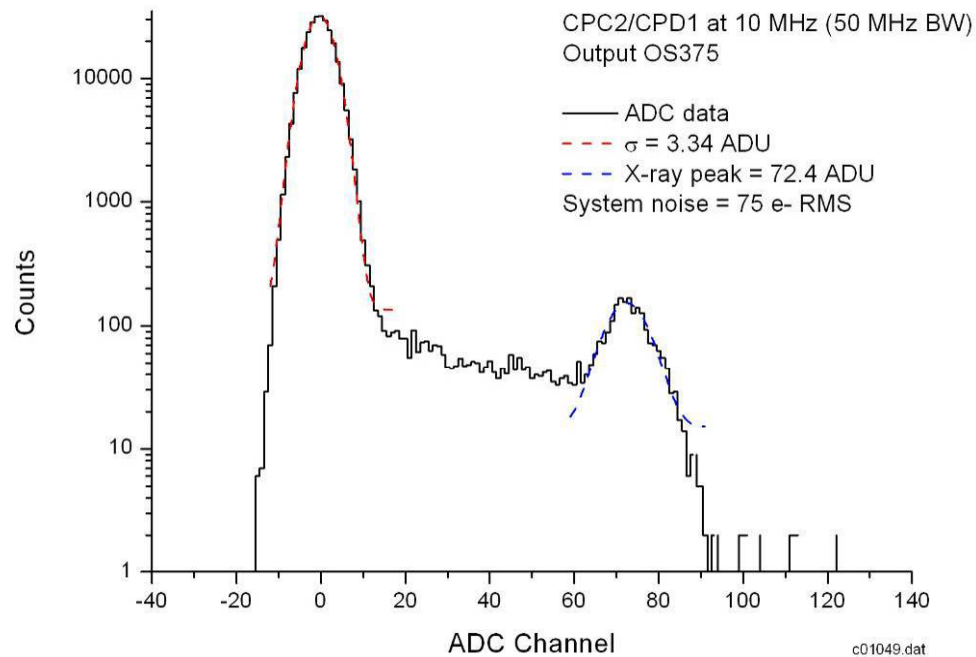


- Stand-alone 2-stage source follower outputs
- ^{55}Fe signal (1620 electrons, MIP-like)
- CPD1 producing clocks in the range 3.3 V to 1.2 V
- Noise **reduced** from 200e- (with transformer drive) to 75 e- (CMOS driver)
- CPC2 works with clock amplitude down to **1.35 Vpp**
- Tests are continuing

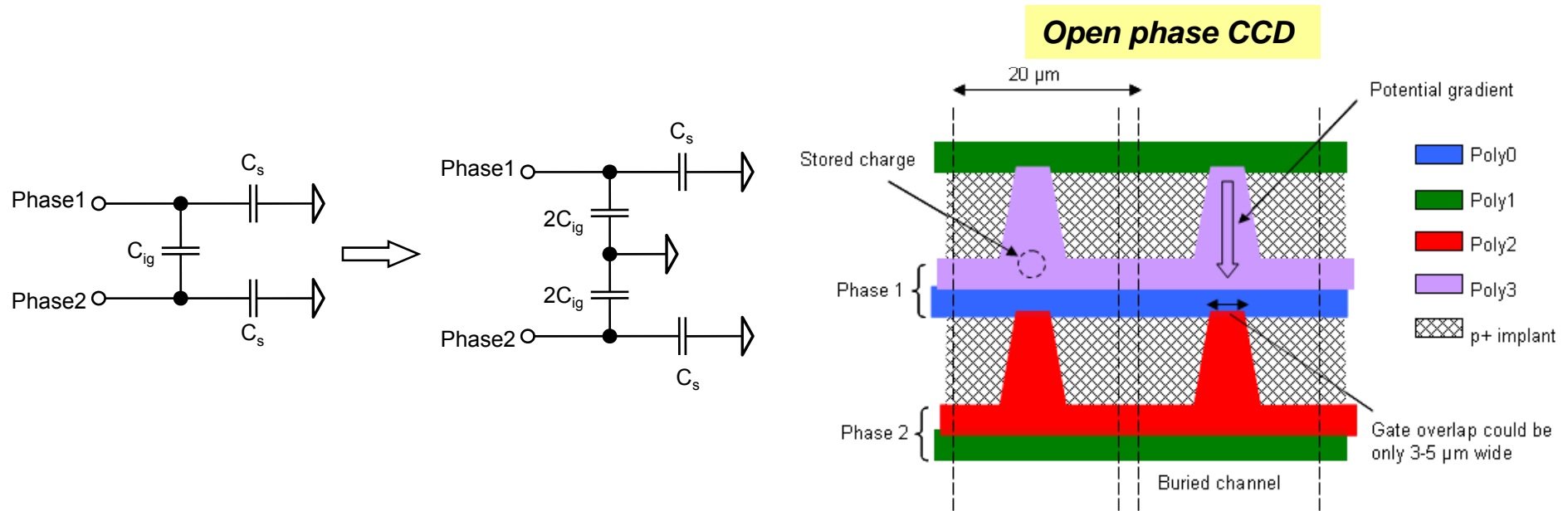New Ideas: CCDs for Capacitance Reduction



- High CCD capacitance is a challenge to drive because of the currents involved
 - ❖ Can we reduce the **capacitance** and the **clock amplitude**? (*both reduce power*)
 - ❖ Inter-gate capacitance C_{ig} is dominant, depends mostly on the size of the gaps and the gate area
 - ❖ Open phase CCD, “Pedestal Gate CCD”, “Shaped Channel CCD” – new ideas under development, could reduce C_{ig} by ~4!
- Together with e2V Technologies designed several small CCDs to test ideas for reduction of capacitance and clock amplitude, now in production


Readout Chips – CPR1 and CPR2

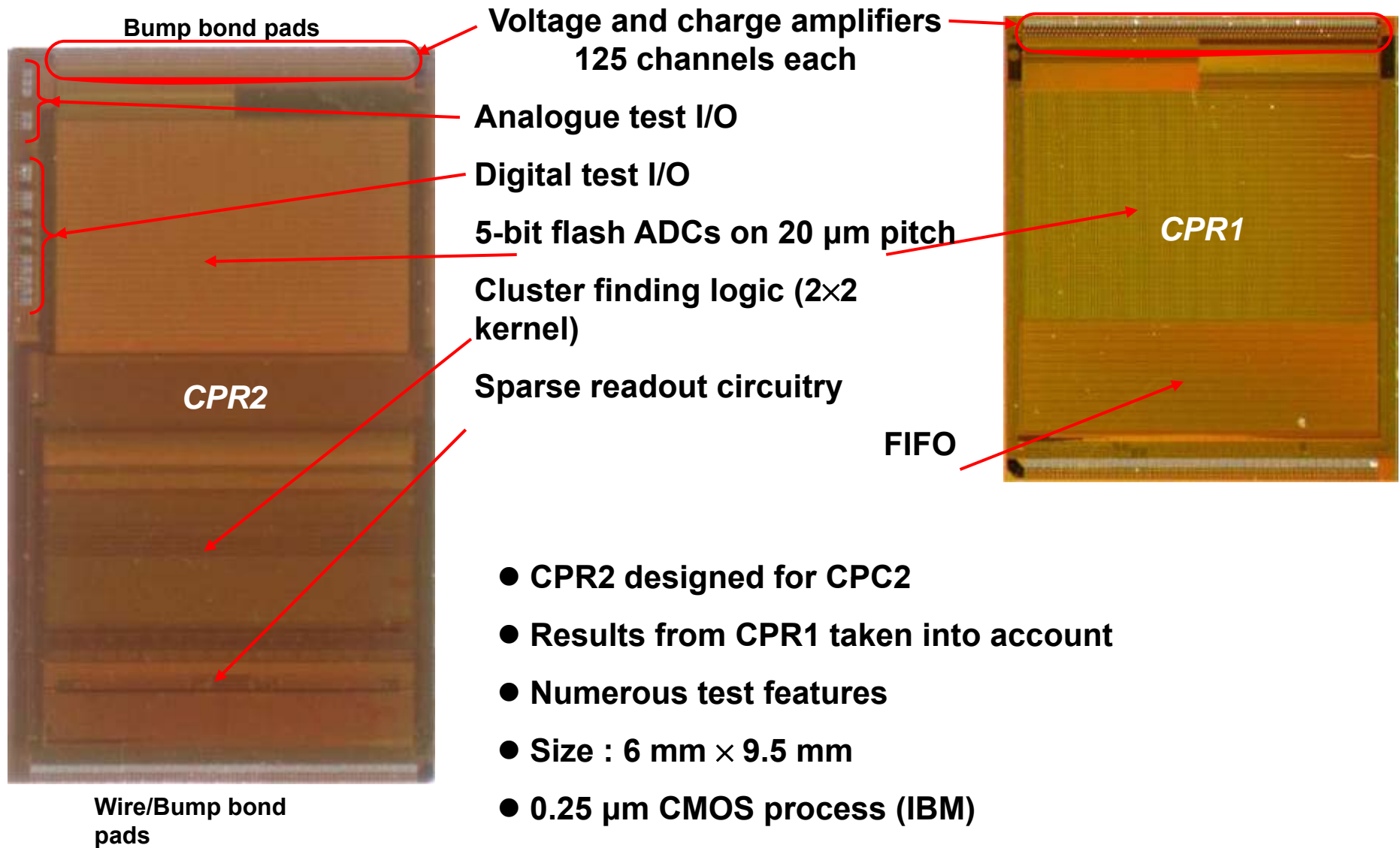



- CPR2 designed for CPC2
- Results from CPR1 taken into account
- Numerous test features
- Size : 6 mm × 9.5 mm
- 0.25 µm CMOS process (IBM)
- Manufactured and delivered February 2005

Steve Thomas/Peter Murray, RAL

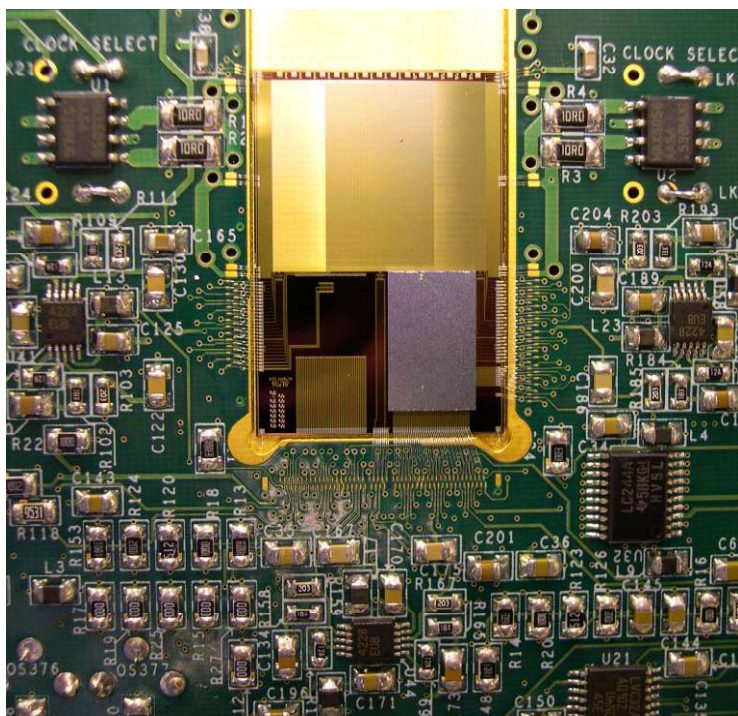CPR2 Bump Bonded to CPC2 – Test Results (1)




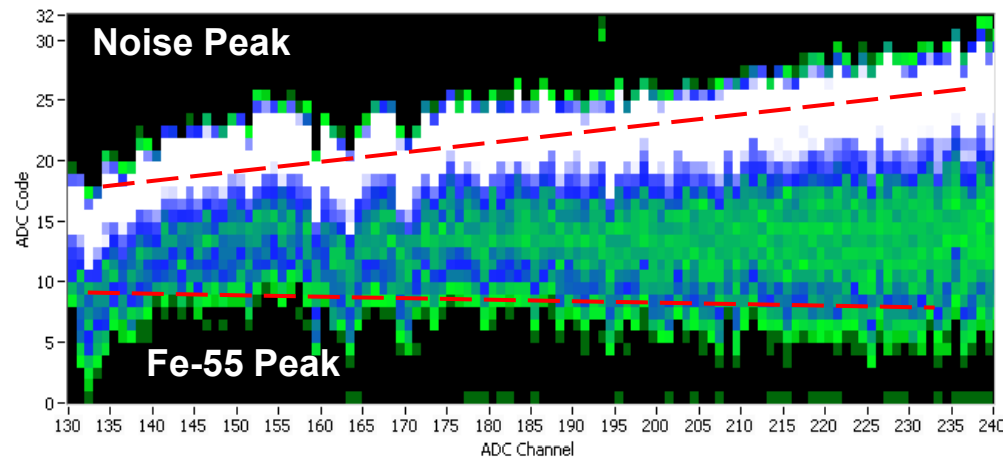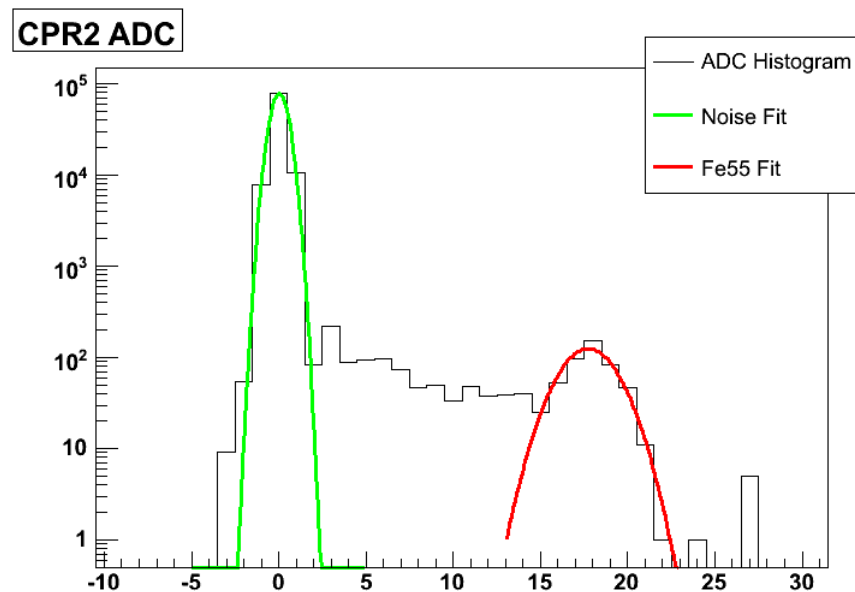- Signals from all voltage channels observed
- Works well at 2 MHz, deterioration at ≥ 5 MHz
- Gain decreases by 50% away from the chip edges
- Noise around 60-80 e-



Tim Woolliscroft, Liverpool U

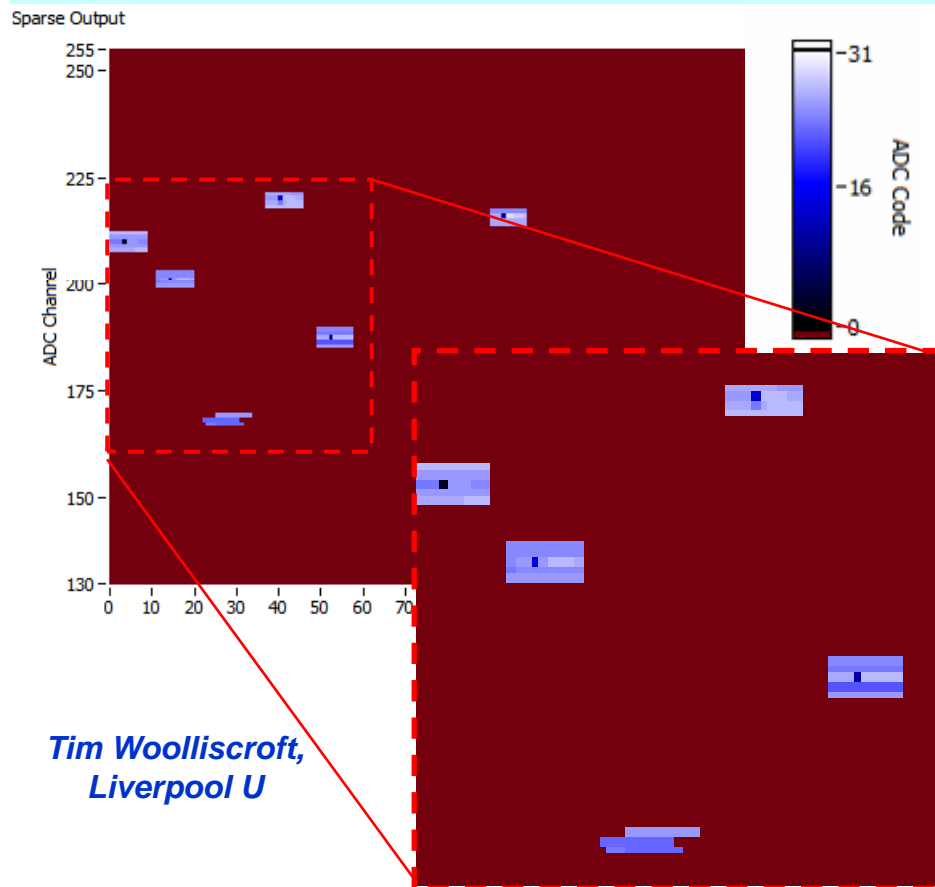
CPR2 Bump Bonded to CPC2 – Test Results (2)



- Parallel cluster finder with 2×2 kernel
- Global threshold
- Upon exceeding the threshold, 4×9 pixels around the cluster are flagged for readout
- Cluster finding with realistic X-ray data:
 - ❖ Dead time revealed: errors as the distance between the clusters decreases
 - ❖ Design occupancy is 1%, data overwritten at higher **peak** occupancy


- A range of improvements being implemented in the next version (CPR2A):
 - ❖ 3-fold increase in the column memory buffer – reduces dead time
 - ❖ Individual column threshold – deals with gain variations
 - ❖ Analogue calibration circuit – can be tested without bump bonding to a CCD
- Will be submitted next month

Clock Driver for CPC2 : CPD1

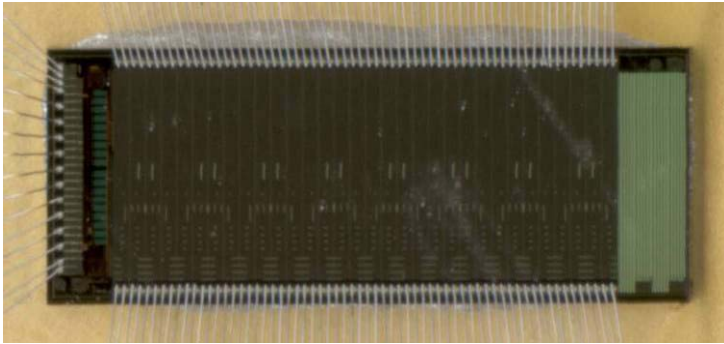

Steve Thomas, Peter Murray, RAL

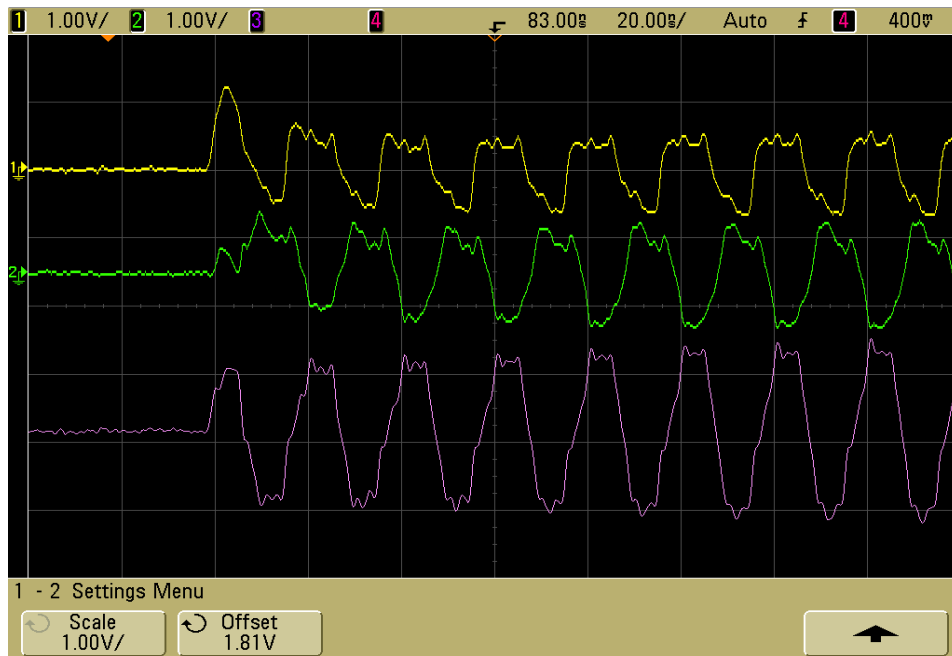- Designed to drive:
 - ❖ Outer layer CCDs (127 nF/phase) at 25 MHz
 - ❖ L1 CCD (40 nF/phase) at 50 MHz
 - ❖ CPC2 requires ~21 Amps/phase!
- One chip drives 2 phases, up to 3.3 V clock swing
- 0.35 μm CMOS process, chip size $3 \times 8 \text{ mm}^2$
- Careful layout on- and off-chip to cancel inductance




Tests:

- CPD1 driving 32 nF-equivalent internal load at 50 MHz
- Hope to maintain the same performance when bump-bonded to a CCD

$2 V_{pk-pk}$ differential clocks

Rui Gao, Andrei Nomerotski, Oxford U

In-situ Storage Image Sensor (ISIS)

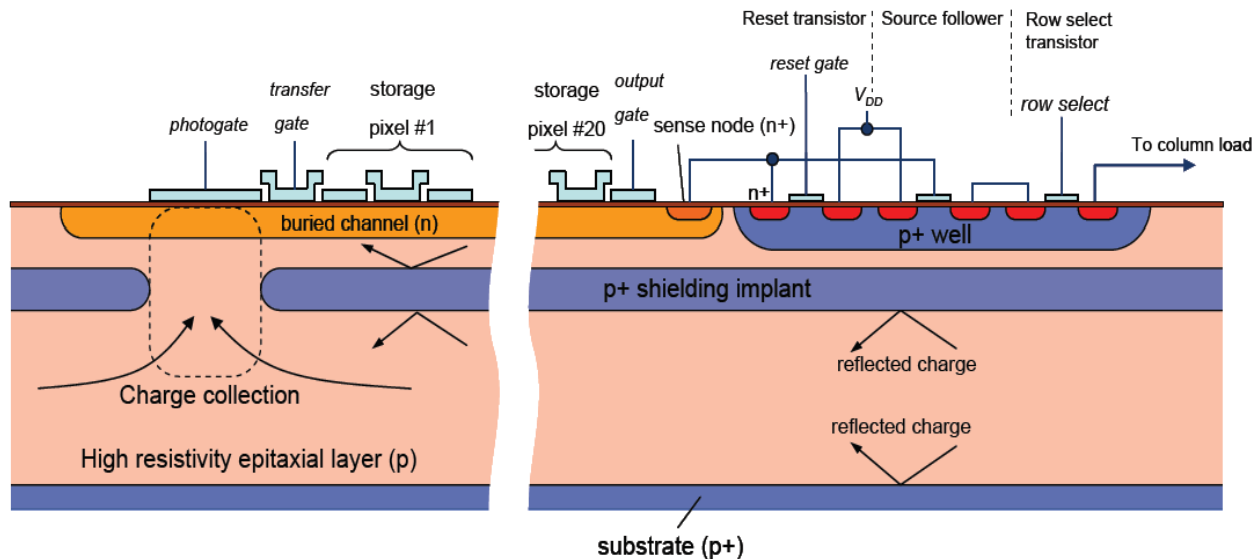


Chris Damerell, RAL

Operating principles of the ISIS:

1. Charge collected under a photogate;
2. Charge is transferred to 20-pixel storage CCD in situ, 20 times during the 1 ms-long train;
3. Conversion to voltage and readout in the 200 ms-long quiet period after the train (**insensitive to beam-related RF pickup**);
4. 1 MHz column-parallel readout is sufficient;

In-situ Storage Image Sensor (ISIS)

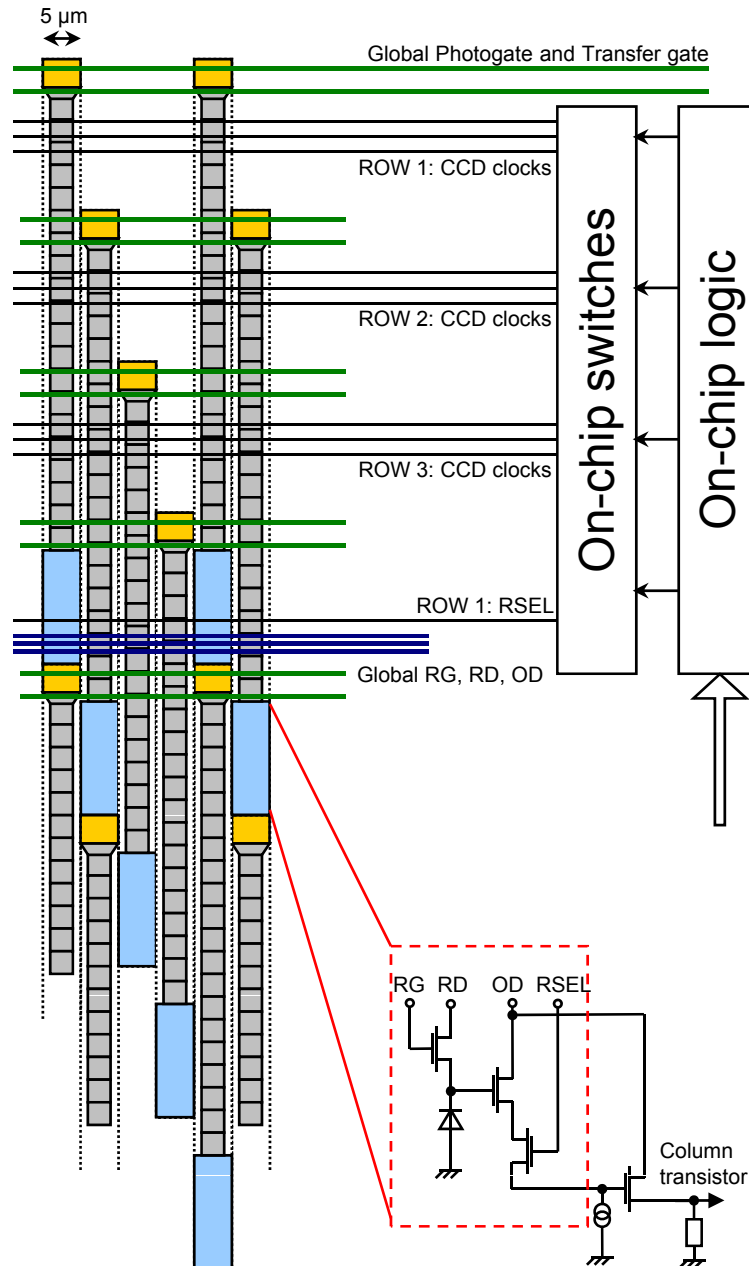

- The ISIS offers significant advantages:

- ❖ **Easy to drive** because of the low clock frequency: 20 kHz during capture, 1 MHz during readout

- ❖ ~100 times more **radiation hard** than CCDs (less charge transfers)


- ❖ **Very robust to beam-induced RF pickup**

- ISIS combines CCDs, active pixel transistors and edge electronics in one device: **specialised process**


- Development and design of ISIS is more ambitious goal than CPCCD

- Proof-of-principle device (ISIS1) designed and manufactured by e2V Technologies


The ISIS1 Cell

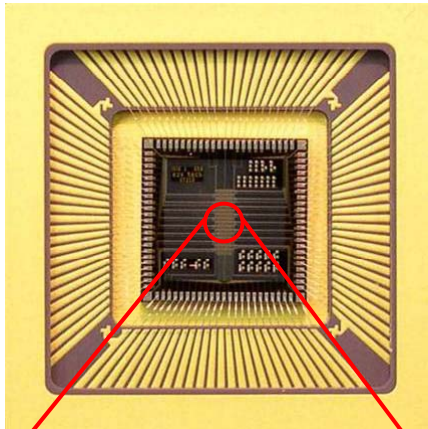

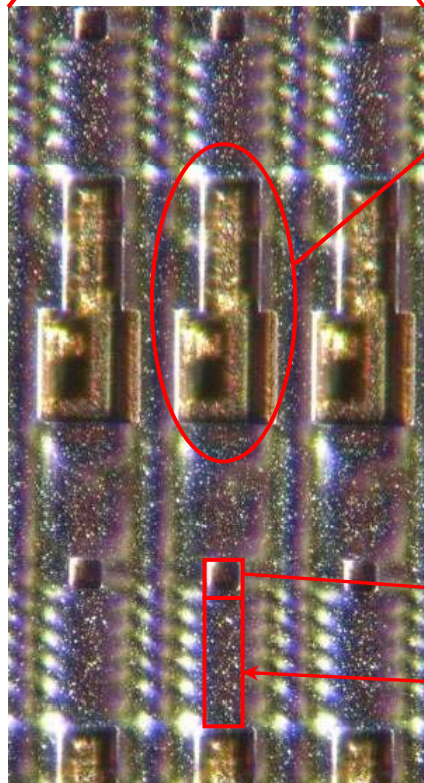- 16×16 array of ISIS cells with 5-pixel buried channel CCD storage register each;
- Cell pitch 40 μm × 160 μm, no edge logic (pure CCD process)
- Chip size ≈ 6.5 mm × 6.5 mm




Output and reset transistors

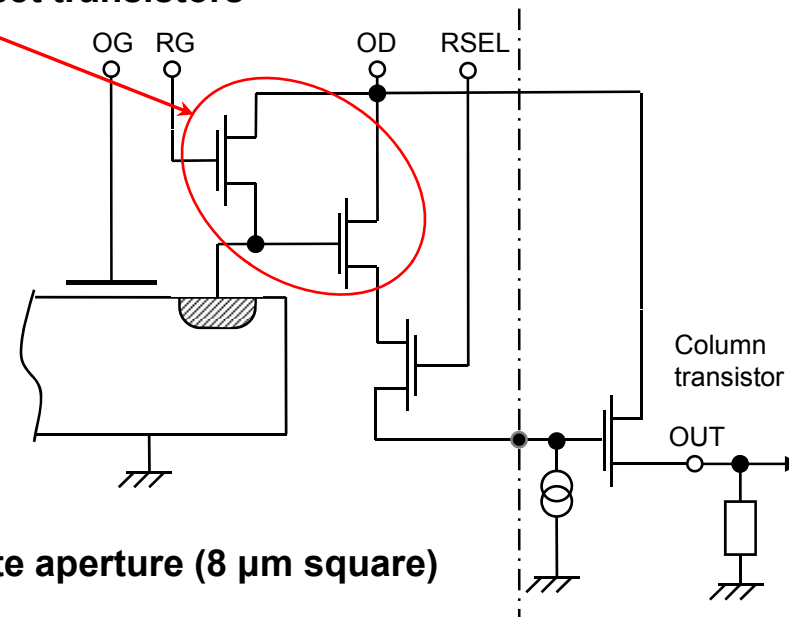

Photogate aperture (8 μm square)

CCD (5×6.75 μm pixels)

Tests of ISIS1

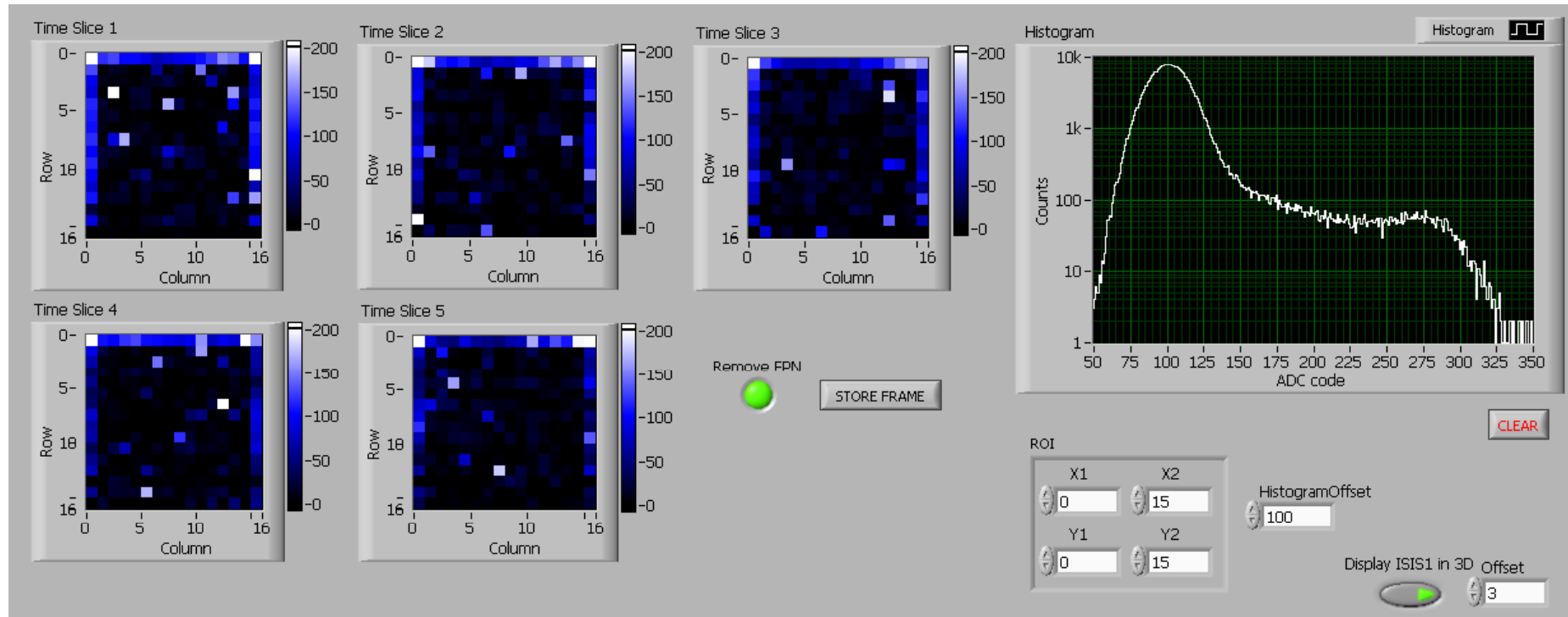


Tests with ^{55}Fe source

- The top row and 2 side columns are not protected and collect diffusing charge
- The bottom row is protected by the output circuitry
- ISIS1 without *p*-well tested first and works OK
- **New ISIS1** chips with *p*-well have been received, now under tests


Mechanical Support Studies

- Goal is 0.1% X_0 per ladder or better, while allowing low temperature operation (~170 K)
- Active detector thickness is only 20 μm
- Unsupported silicon
 - ❖ Stretched thin sensor (50 μm), prone to lateral deformation
 - ❖ Fragile, practically abandoned
- Silicon on thin substrates
 - Sensor glued to semi-rigid substrate held under tension
 - Thermal mismatch is an issue – causes the silicon to deform
 - Many studies done for Be substrate
- Silicon on rigid substrates
 - Shape maintained by the substrate
 - Materials with good thermal properties available
 - Foams offer low density and mass while maintaining strength

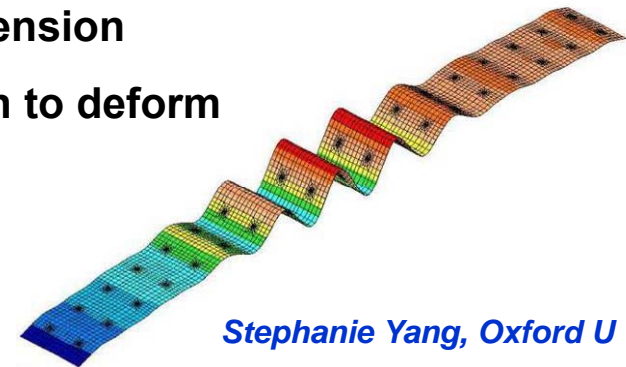


Mechanical Support Studies

- RVC (Reticulated Vitreous Carbon) and silicon carbide are excellent thermal match to silicon
- Silicon-RVC foam sandwich (~ 3% density)
 - Foam (1.5mm thick), sandwiched between two 25 μm silicon pieces – required for rigidity
 - Achieves 0.09% X_0
- Silicon on SiC foam (~ 8% density)
 - Silicon (25 μm) on SiC foam (1.5mm);
 - Achieves 0.16% X_0
 - 0.09% X_0 possible with lower density foams (< 5%)

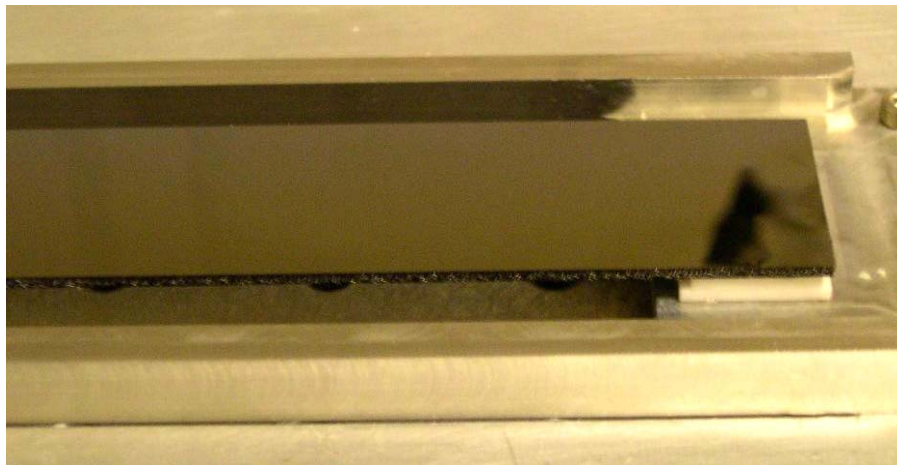

Thanks to Erik Johnson, RAL

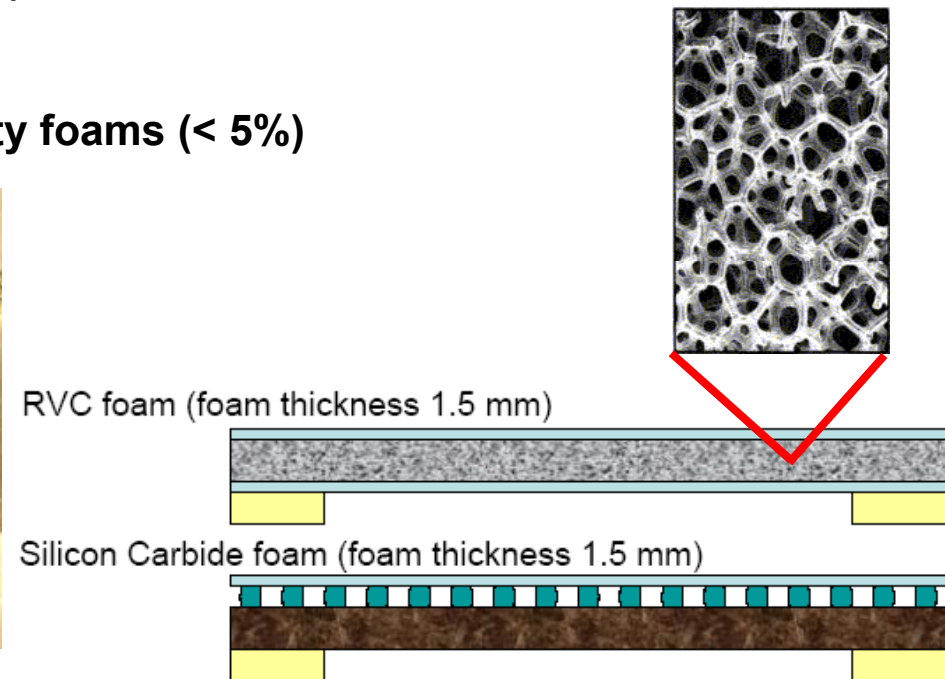


Conclusion

- **Detector R&D is progressing very well**
- **CPCCD program most advanced:**
 - ❖ **High speed CPC2 reaches 45 MHz operation stand-alone**
 - ❖ **Bump-bonded assemblies CPC2/CPR2 in final tests, results encouraging**
 - ❖ **Programme for capacitance and clock amplitude reduction underway**
 - ❖ **Driver system with CMOS ASICs or transformers**
 - ❖ **Third generation readout chip CPR2A in advanced design stage**
- **ISIS development:**
 - **“Proof of principle” device works**
 - **Actively pursuing small pixel ISIS2**
- **Mechanical support aims at $\leq 0.1\%$ X_0 using modern materials**


Extra Slides

CPC1/CPR1 Performance

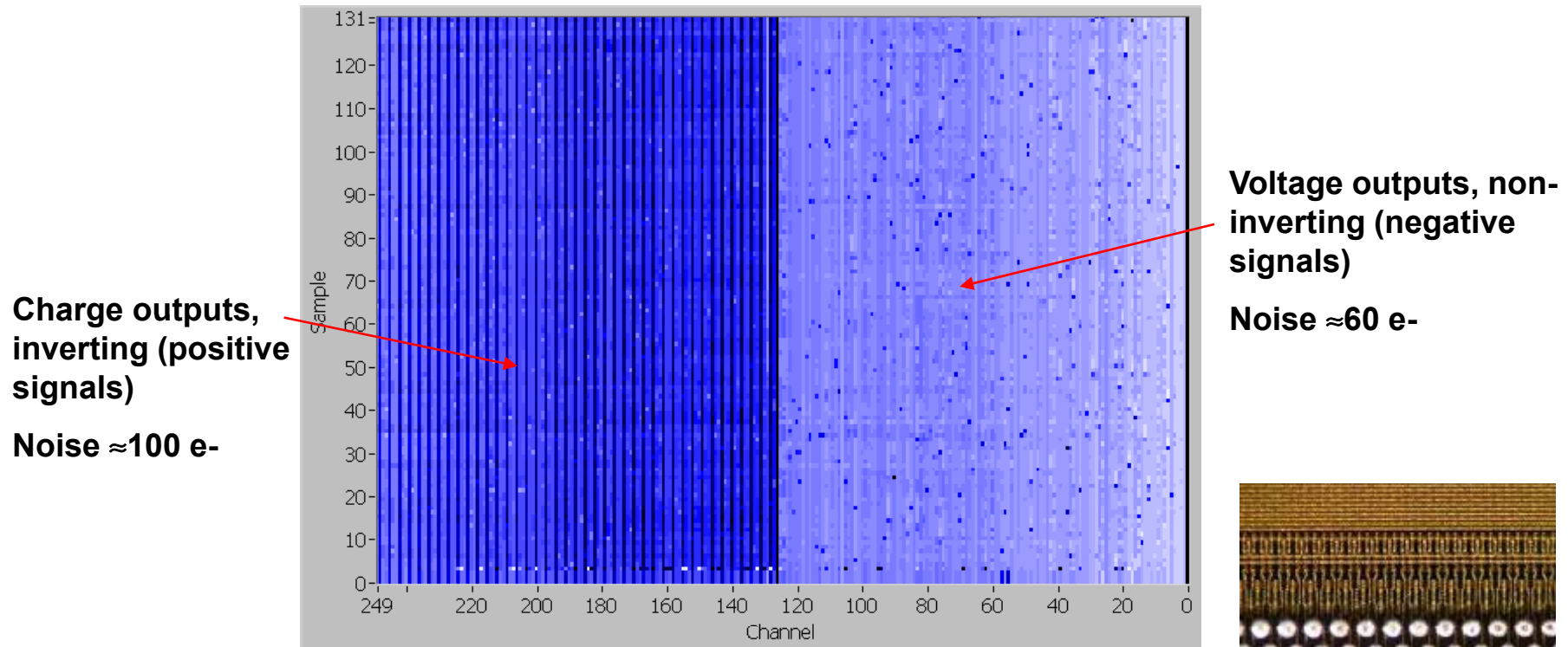5.9 keV X-ray hits, 1 MHz column-parallel readout





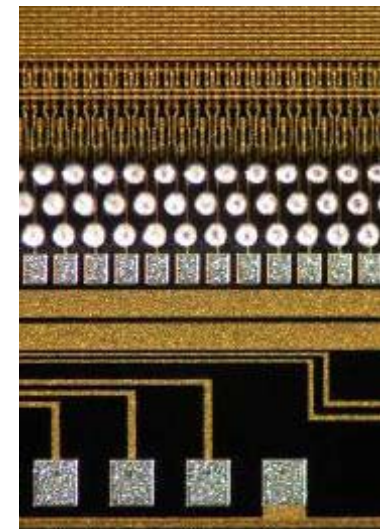
- First time e2V CCDs have been bump-bonded
- High quality bumps, but assembly yield only 30% : mechanical damage during compression suspected
- Differential non-linearity in ADCs (100 mV full scale) : addressed in CPR2




Bump bonds on CPC1 under microscope

The Column Parallel CCD

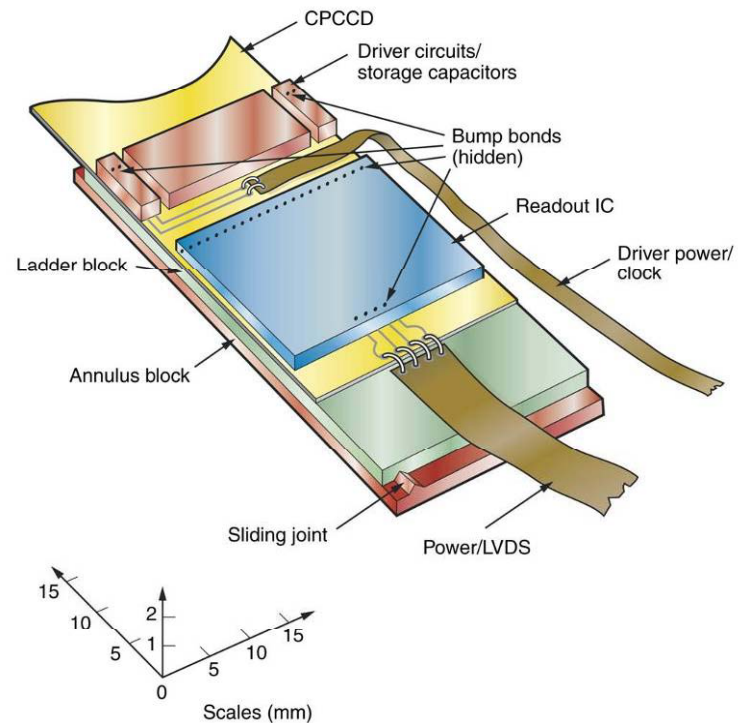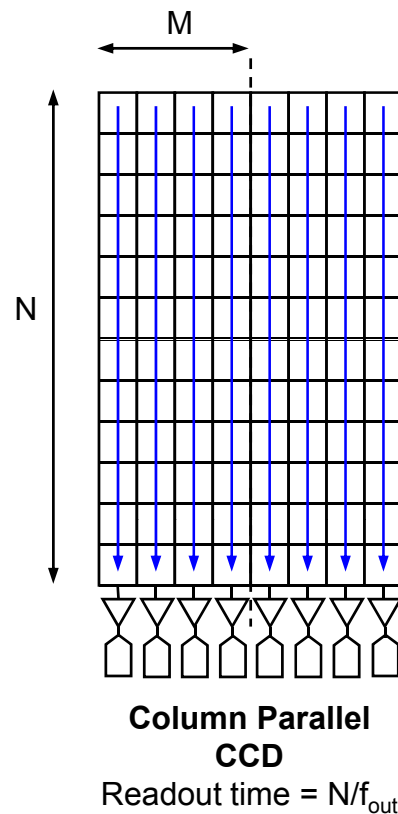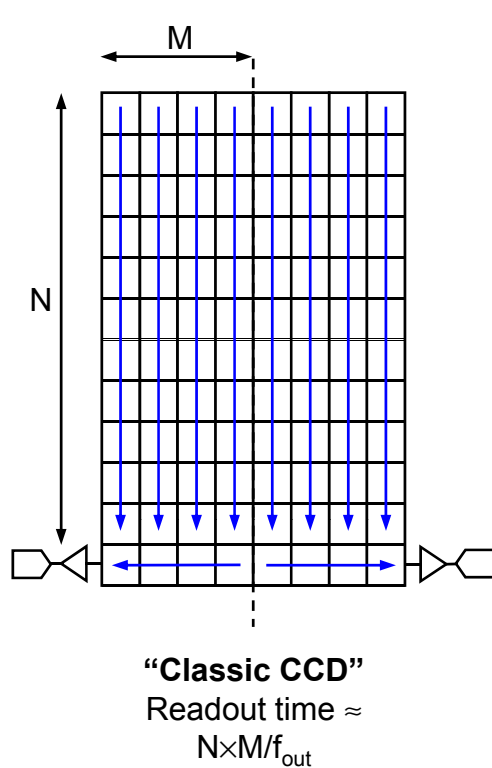- Main detector work at LCFI
- Every column has its own amplifier and ADC – requires readout chip
- Readout time shortened by orders of magnitude
- All of the image area clocked, complicated by the large gate capacitance
- Optimised for low voltage clocks to reduce power dissipation



CPC2, CPR2 and CPD1 All Together

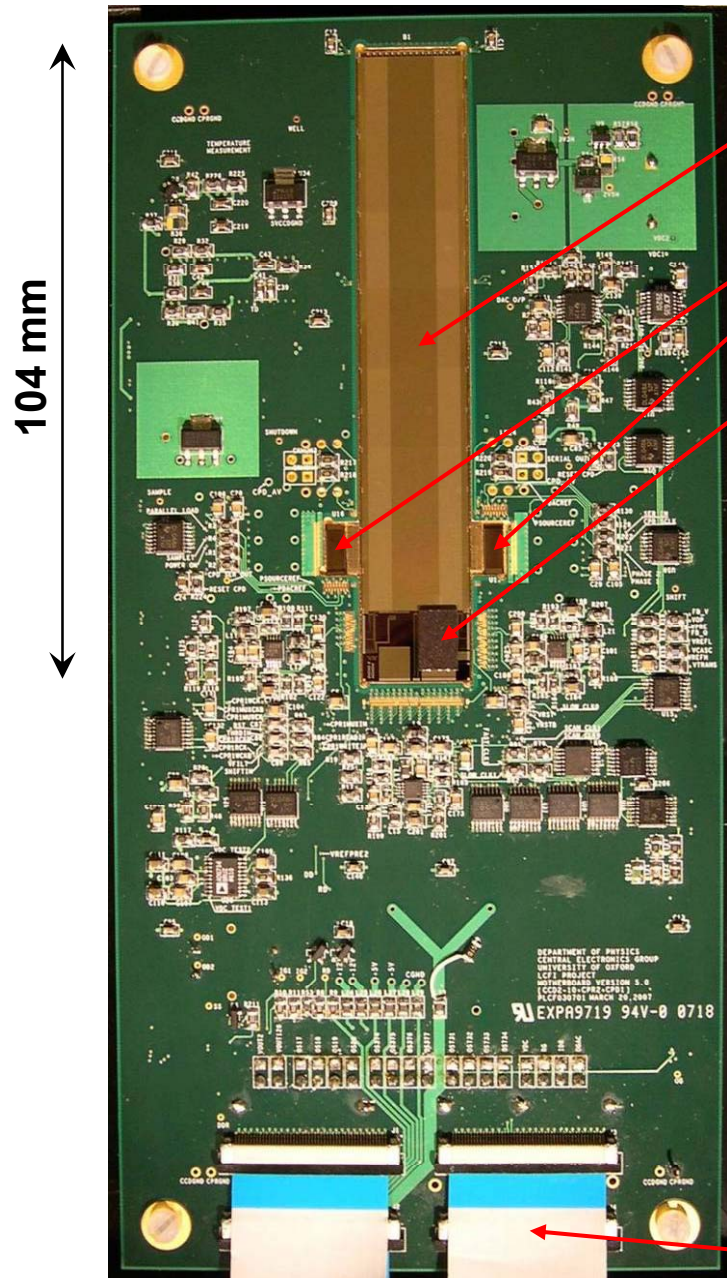


CPC2-70

Two driver chips CPD1

Bump-bonded CPR2

Flexible cables

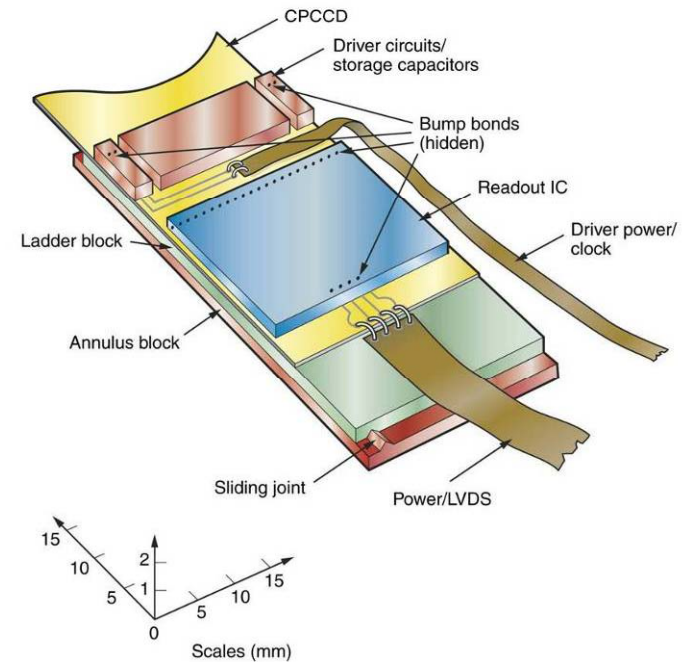

- All ingredients are in place – intensive testing ahead in the next months
- Getting closer to prototype ladder
- Next generation CPR2A should make this board much smaller