



AGH UNIVERSITY OF SCIENCE
AND TECHNOLOGY

Development of a low power PLL and DLL in 130nm CMOS technology

Mirostaw Firlej

T. Fiutowski, M. Idzik, J. Moroń, K. Świentek

Faculty of Physics and Applied Computer Science
AGH University of Science and Technology

TWEPP Topical Workshop on Electronics for Particle Physics 2015, 28 September – 2 October, Lisbon, Portugal

This work was supported by Polish National Science Centre (NCN), grant reference number DEC-2012/07/B/ST7/01456



Agenda

- Motivation
- Specifications for PLL and DLL in CMOS 130 nm
- PLL Architecture and Design in process A and B
- DLL Architecture and Design in process A and B
- Prototype ASIC Board and Measurement Setup
- PLL measurements results in process A and B
- DLL measurements results in process A and B
- Summary



Motivation

- Main motivation - Silicon ASIC for LHCb Tracking (SALT) at LHC collider
 - Phase -Locked Loop (PLL) for data serialization and transmission
 - Delay-Locked Loop (DLL) for clock phase alignment for ADC sampling
- Additional motivation - both PLL, DLL are designed with additional features allowing their use as general purpose blocks
 - ultra-low power
 - low jitter
 - multiphase outputs



Specifications


Phase-Locked Loop (PLL)

- Operating frequencies: 80MHz, 160MHz, 240MHz, and 320MHz
- Dividers by: 2, 4, 6, and 8
- Default reference frequency 40 MHz and output 160MHz
- Multi-phase clock output
- Power consumption < 2mW @ 160MHz
- Jitter < 10ps @ 160MHz

Delay-Locked Loop (DLL)

- Operating frequency: 40MHz
- 64 clock phases
- Power consumption < 2mW @ 40MHz
- Jitter < 15 ps @ 40MHz

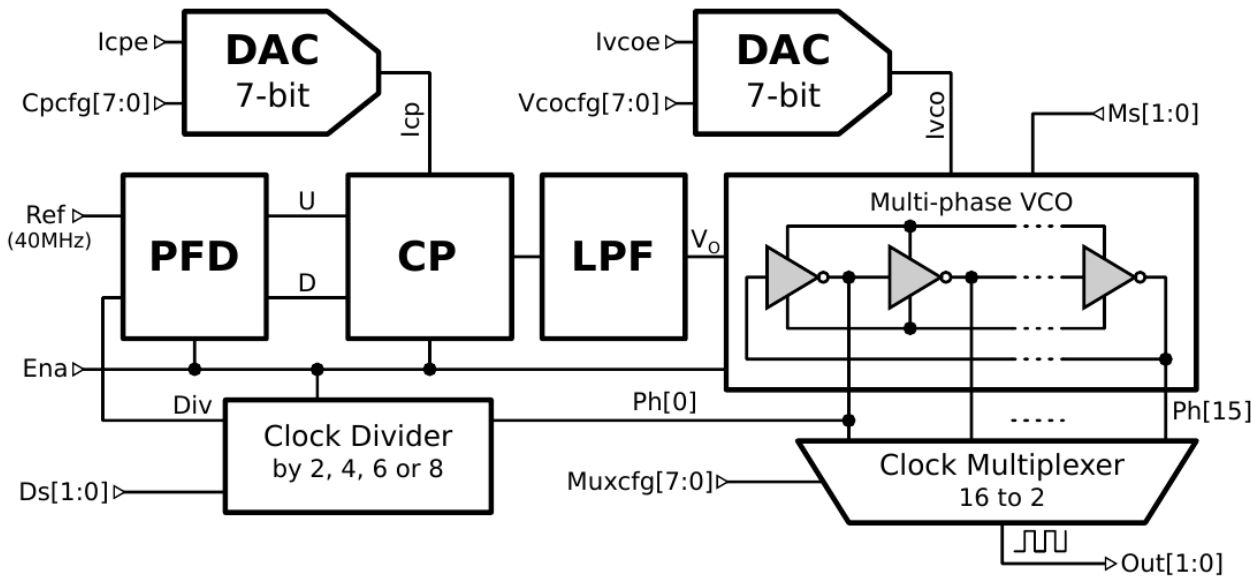Phase-Locked Loop Architecture and Design in CMOS 130 nm process A and B



Differences

Process A:

- Single-ended VCO
- External VCO bias

Process B:


- Differential VCO
- External/Internal DAC

- VCO - core block of PLL - generates 16 output square waves
- PFD compares VCO signal (divided by **N**) to reference signal
- PFD output signals, after processing in CP and filtering, give negative feedback to control VCO frequency
- Output wave (**N** times faster) is synchronized with reference clock


PLL Architecture and Design

Voltage Controlled Oscillator (VCO)

VCO block diagram in process A and B

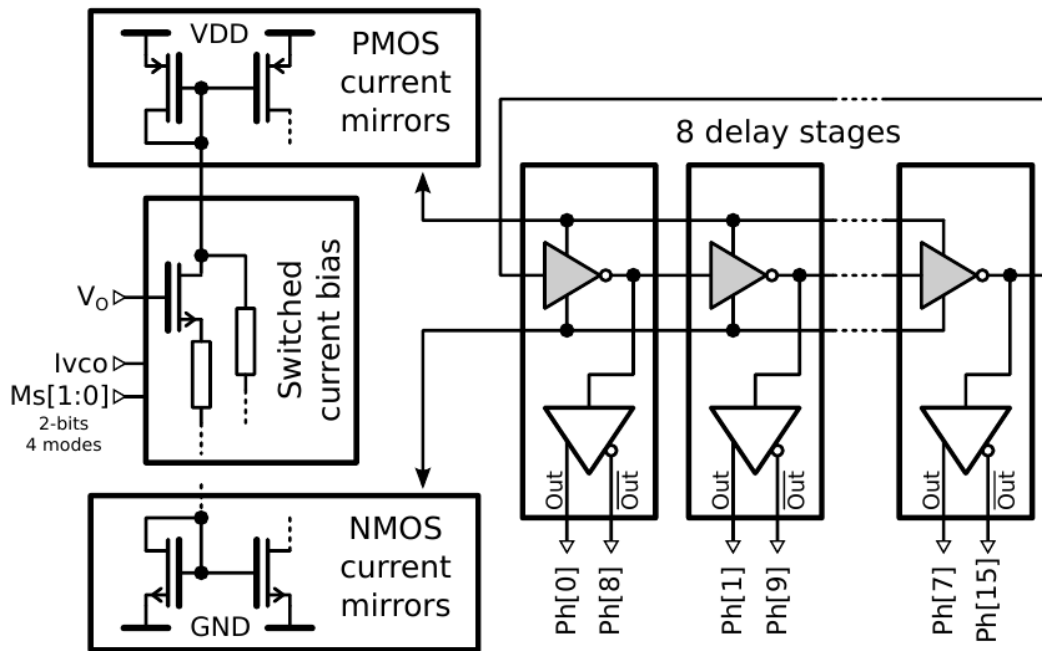

Example simulation

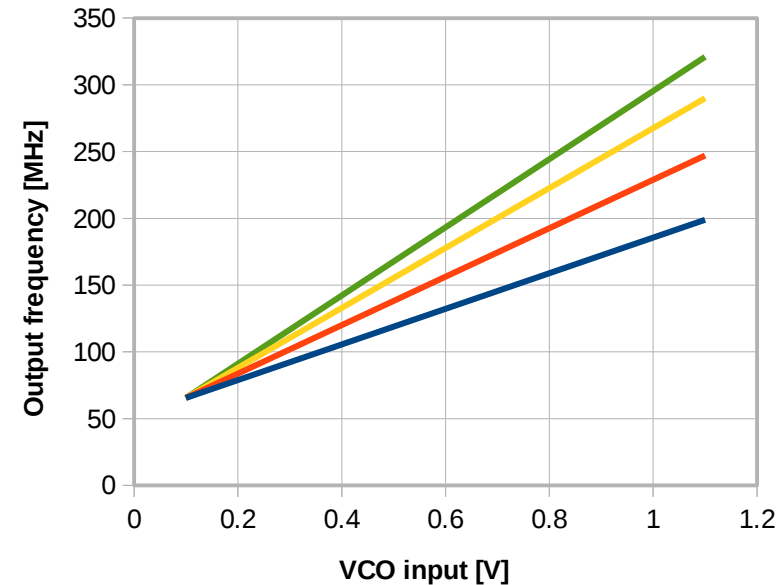


- Common PMOS/NMOS current sources for all delay stages
- Switched current bias - four different VCO gains available

PLL Architecture and Design


VCO delay stages

Process A

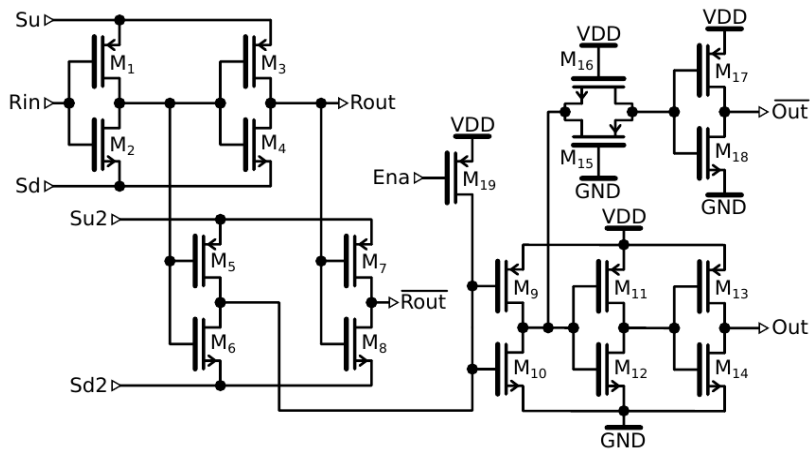

- Single-ended delay cell
- Delay of complementary output compensated by transmission gate
- Enable/Disable provided by M_{19}

Process B

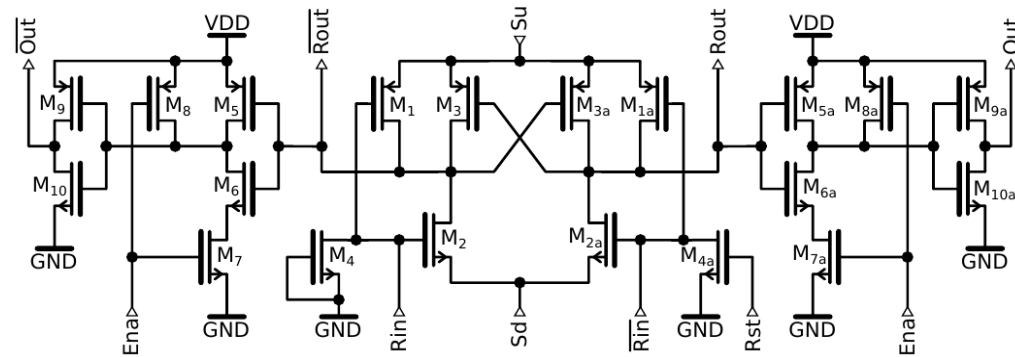


- Differential delay cell
- Complementary output given by differential design
- Enable/Disable provided by $M_{5(a)} - M_{8(a)}$

PLL (DLL) Architecture and Design


PFD and CP

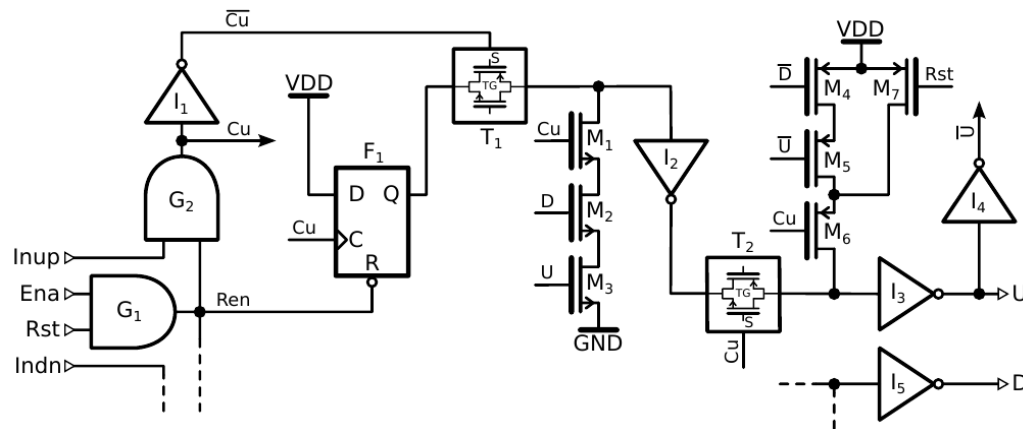Phase and Frequency Detector (PFD) (only half of PFD is shown)




- The same PFD for PLL and DLL in process A and B
- Very simple architecture based on two flip-flops and one NAND gate
- Dynamic flip-flops are used to improve switching speed
- NAND gate integrated inside flip-flop structure

Charge Pump (CP)

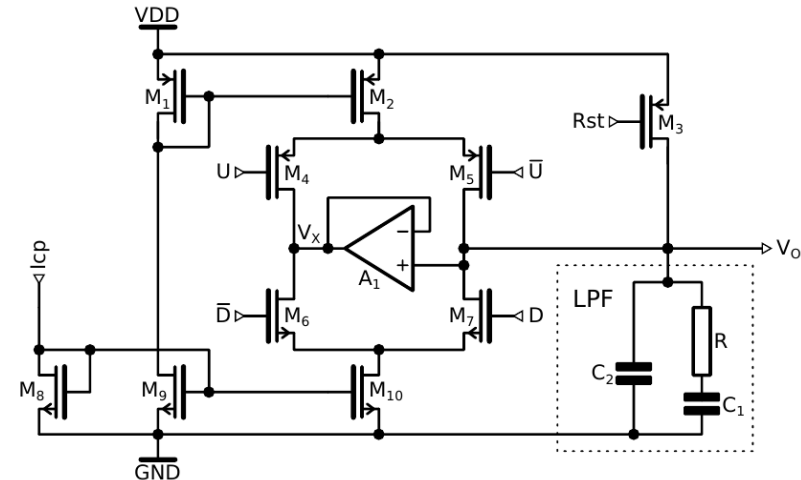

- The same CP for PLL and DLL in process A and B
- Typical CP architecture with two current mirrors and four switches
- Additional transistor M₃ to precharge LPF to VDD at the beginning - needed for DLL

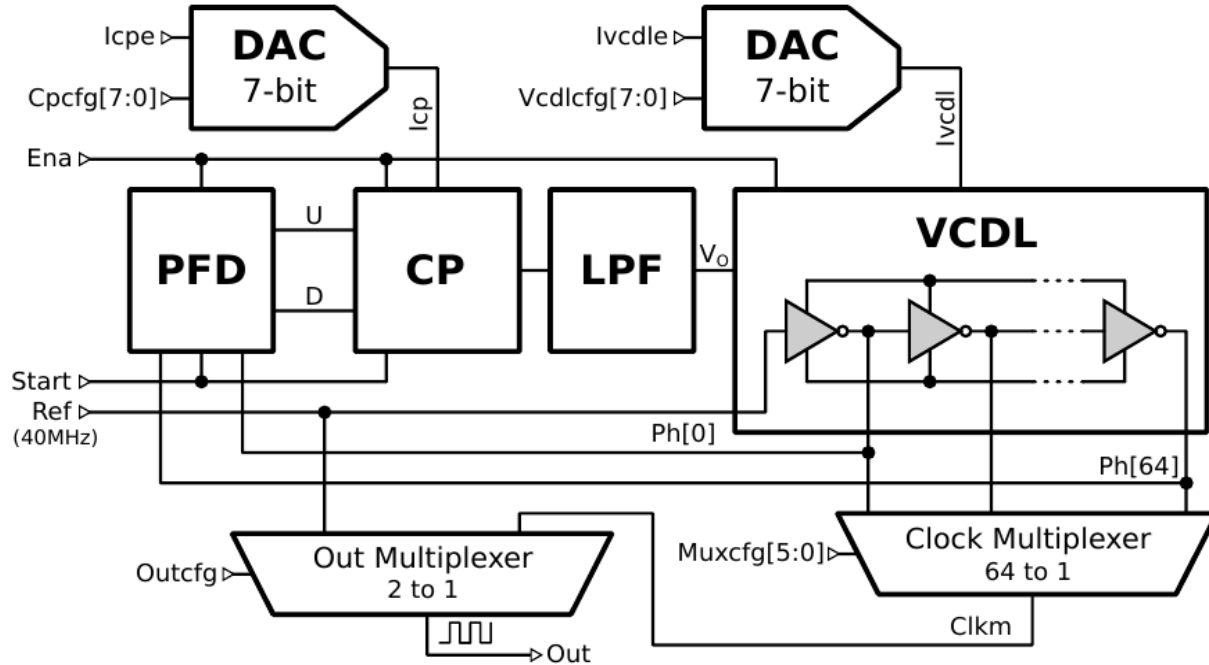Delay-Locked Loop (DLL) Architecture and Design in CMOS 130 nm process A and B



Differences

Process A:

- External bias


Process B:

- External/Internal DAC
- Additional Output Multiplexer

- Single-ended VCDL provides 64 output clock phases
- PFD compares two VCDL output signals (Ph[0] and Ph[64])
- PFD output signals, after processing in CP and filtering, give negative feedback to control VCDL delay
- Output clock phase selected by multiplexer


DLL Architecture and Design

Voltage Controlled Delay Line (VCDL)

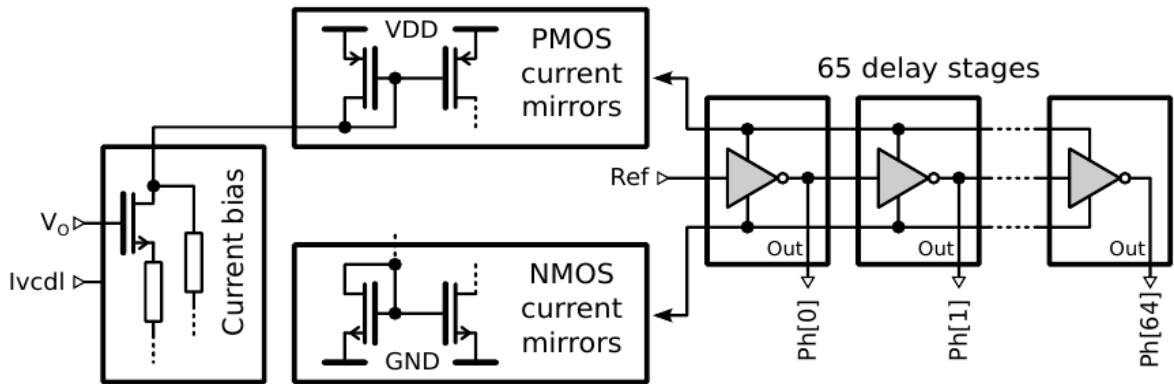



- The same VCDL in process A and B
- 65 delay stages
 - 64 outputs
 - extra output for PFD

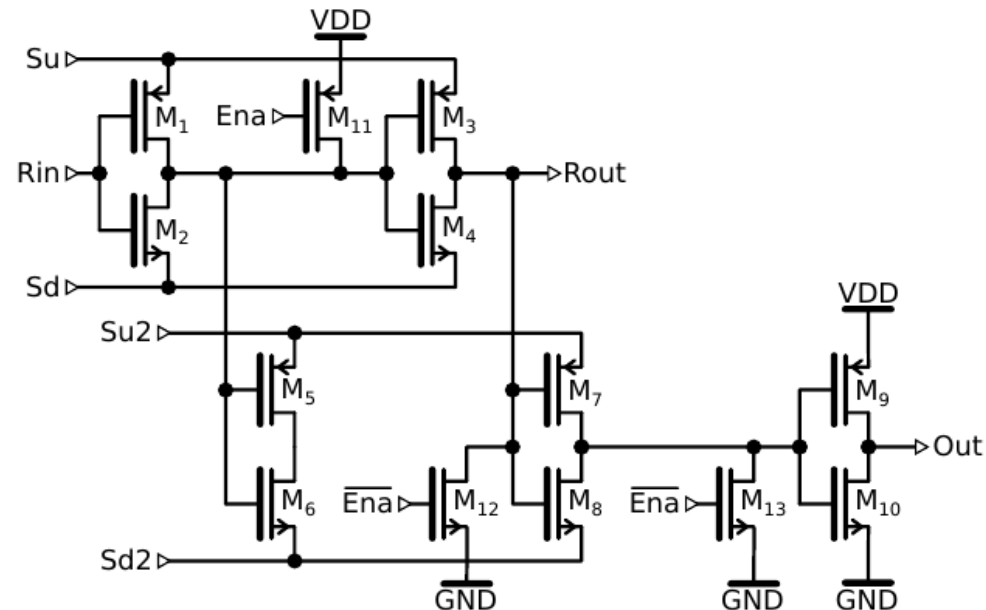- Single-ended delay cell
- Additional pair of current-starved inverters works as signal buffer - improves PSRR
- Enable/Disable provided by $M_{11} - M_{13}$




Prototype ASIC board and Measurement Setup

ASIC Floorplan and prototype PCB

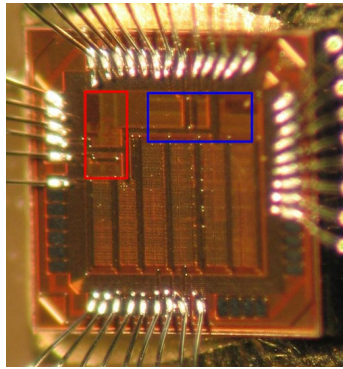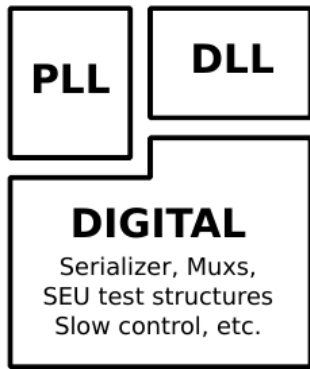

Main features:

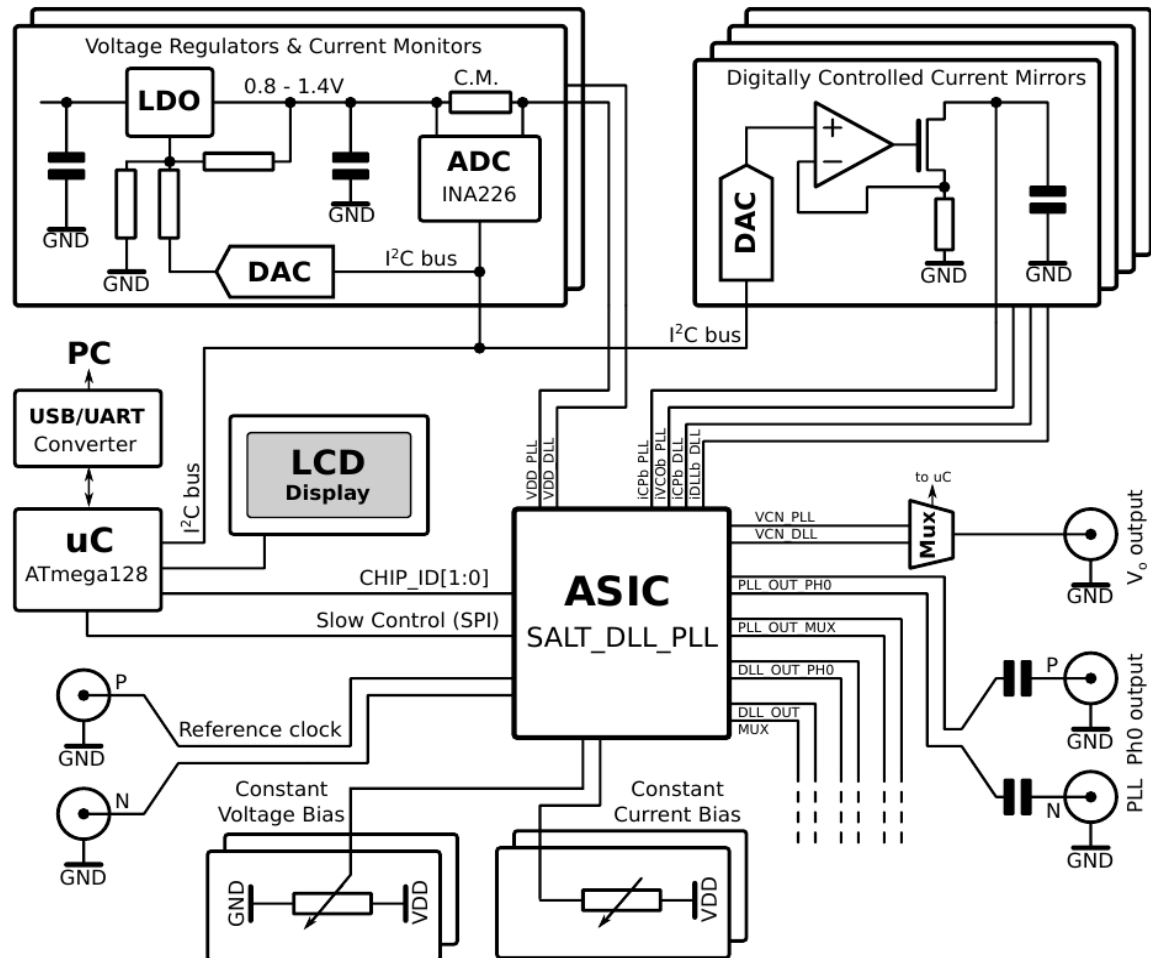- Digitally controlled Voltage Regulators
- Current/Voltage monitoring
- Digitally controlled current mirrors
- Board controlled by uC
- Communication with PC via USB/UART





Prototype ASIC board and Measurements Setup

Laboratory equipment

Instrumentation:

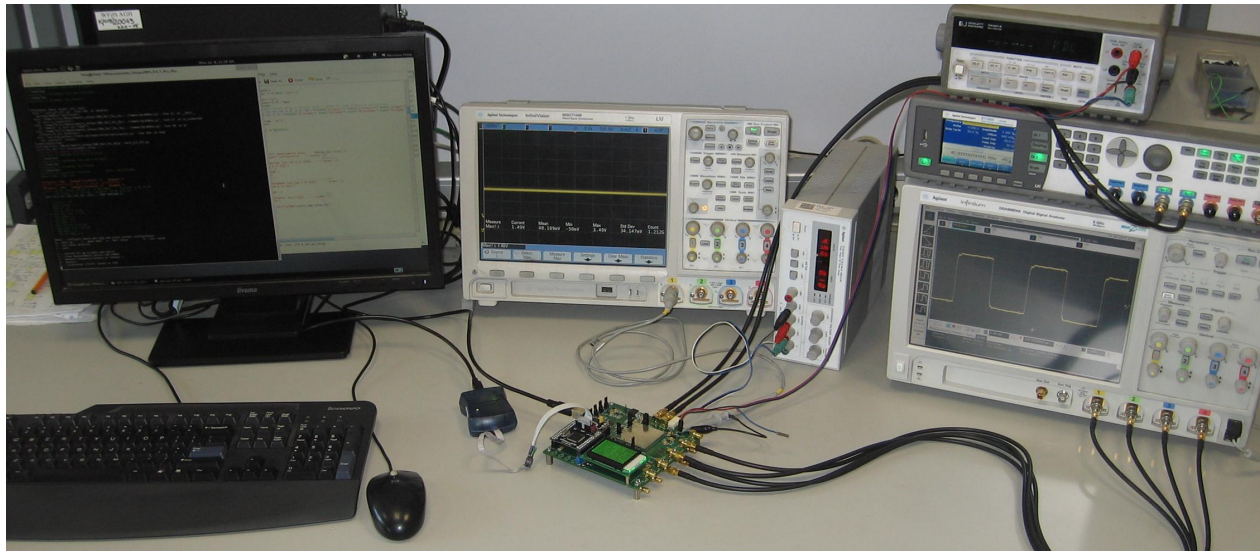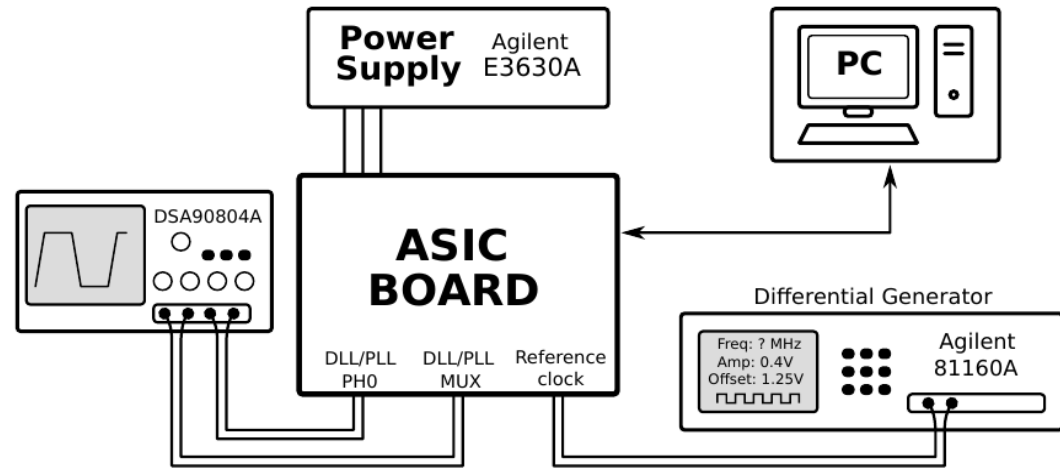- Power supply (E3630A)
- Differential Generator (81160A)
- 40GS/s scope (DSA90804A)
- PC computer





Laboratory equipment and ASIC board are controlled by dedicated software



PLL Measurements results in process A and B

Transfer function and Power consumption

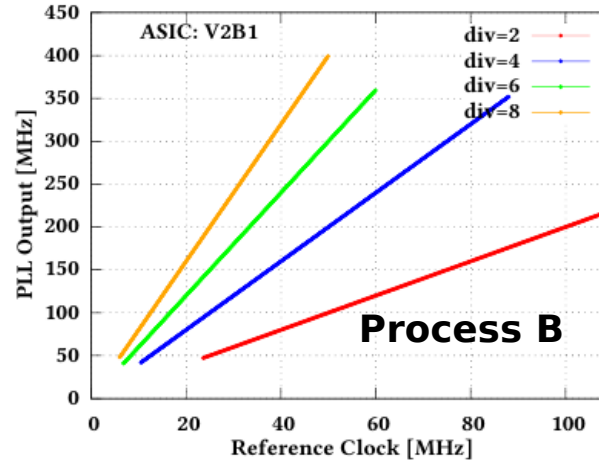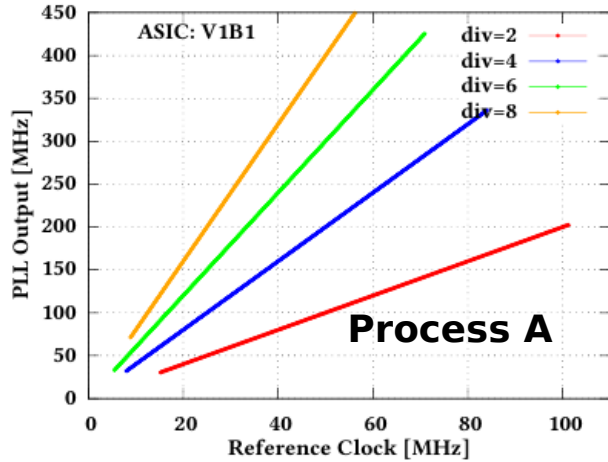

Transfer function

Process A:



30 - 450 MHz

Dividers: 2, 4, 6, and 8

Process B:

40 - 400 MHz

Dividers: 2, 4, 6, and 8

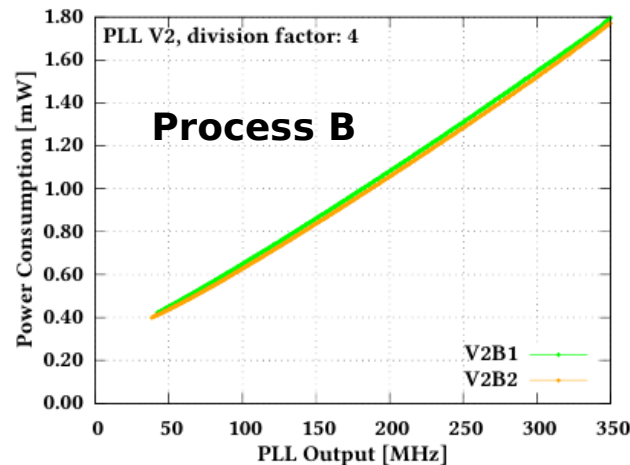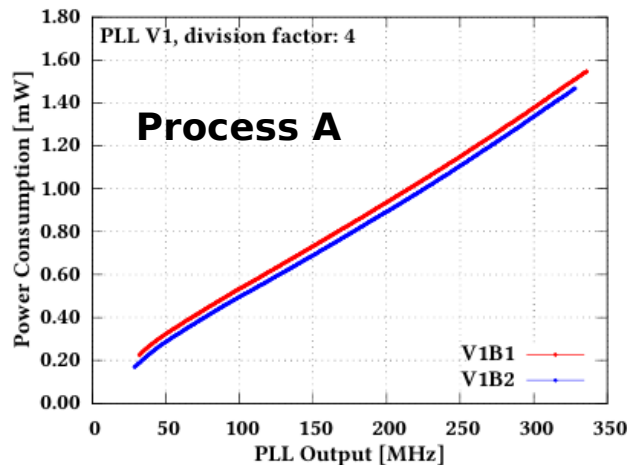

Power consumption

Process A:

0.8mW @ 160MHz

Process B:



0.95mW @ 160MHz

Both PLLs consume very low power and work well in wide frequency range



PLL Measurements results in process A and B

Period Jitter

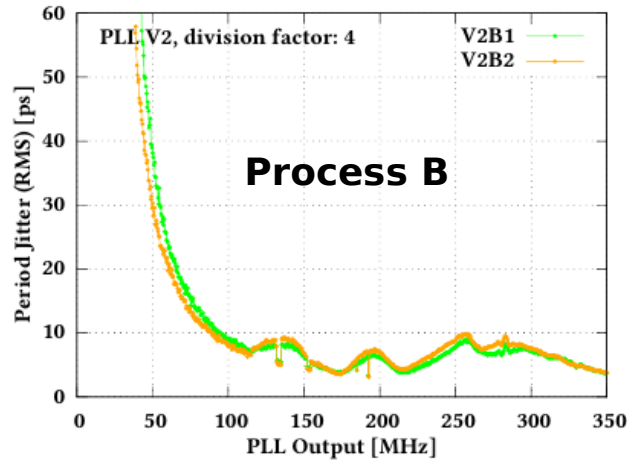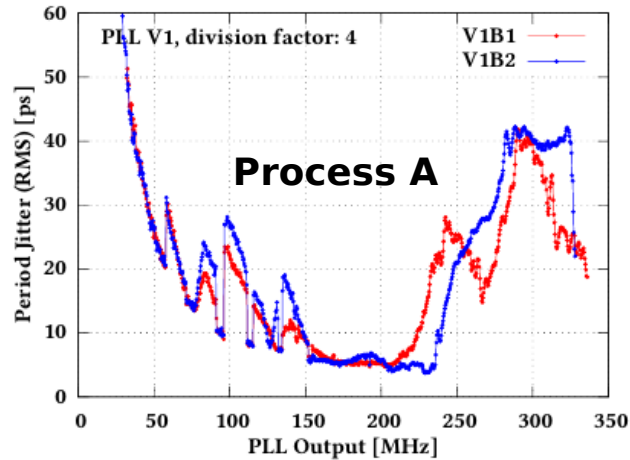



Period Jitter RMS

Process A:

<10ps @ 150 - 220MHz

Process B:

<10ps @ 100 - 350MHz

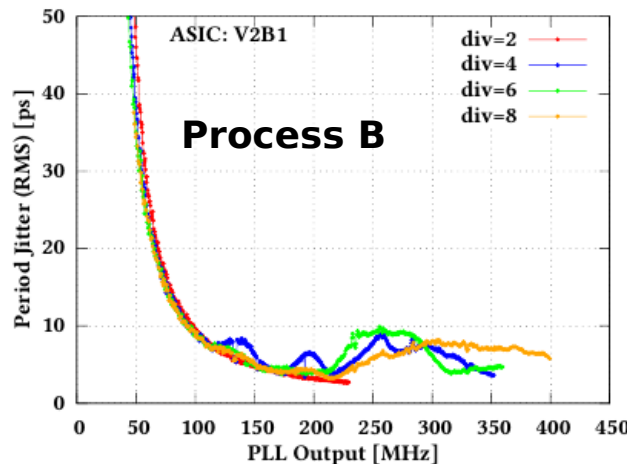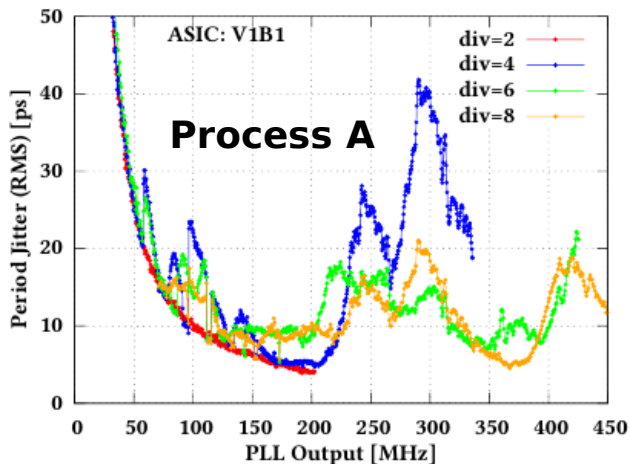

Jitter vs Divider

Process A:

Jitter fluctuates and depends on selected PLL divider

Process B:

Jitter smaller, stable, and weakly depends on divider

Low jitter in wide frequency range - for process B lower and more stable



DLL Measurements Results in process A and B

Transfer function and Power consumption





Transfer function

Process A:

Frequency range: 18 - 62 MHz
64 phases, delay: 355 - 445 ps

Process B:

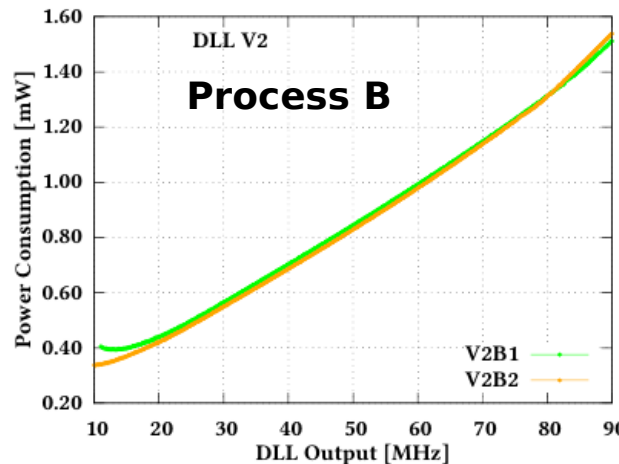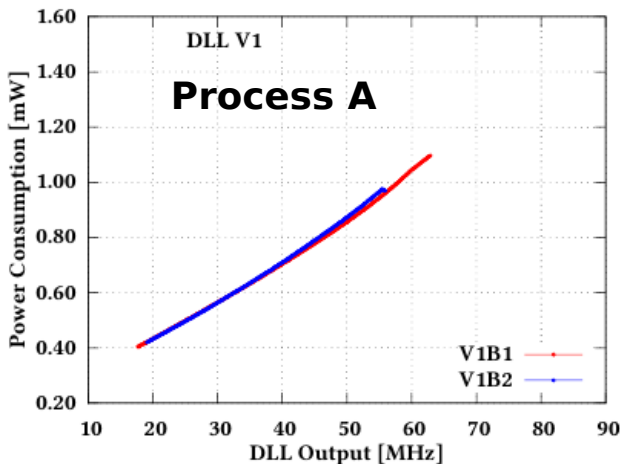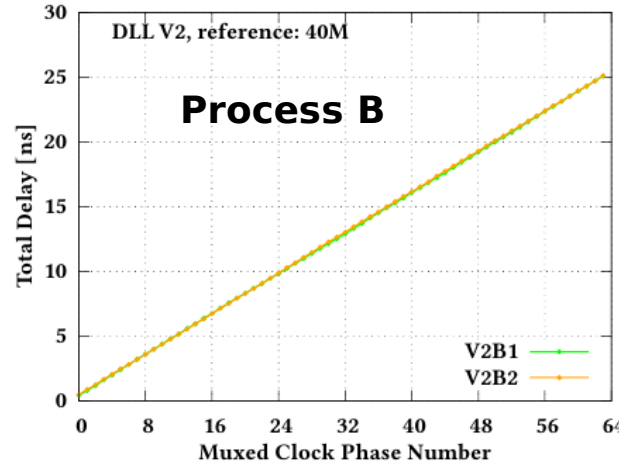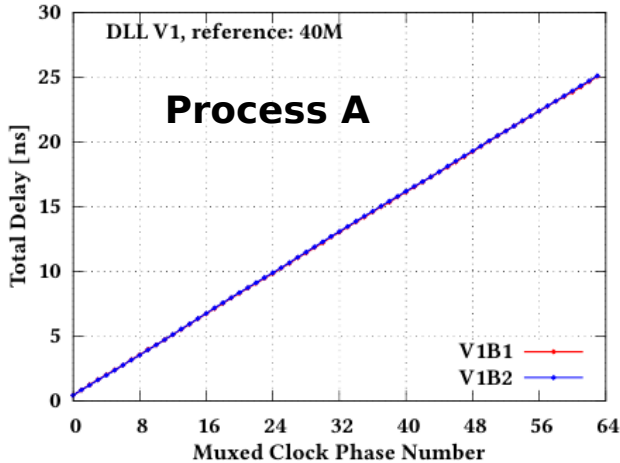Frequency range: 10 - 90 MHz
64 phases, delay: 350 - 448 ps



Power Consumption

- Similar for process A and B
- Scales linearly with frequency

Very good linearity and very small power consumption



DLL Measurements Results in process A and B

Period Jitter





Jitter at phase 0

Process A:

<7 ps @ 18 - 62 MHz

Process B:

<7 ps @ 18 - 90 MHz

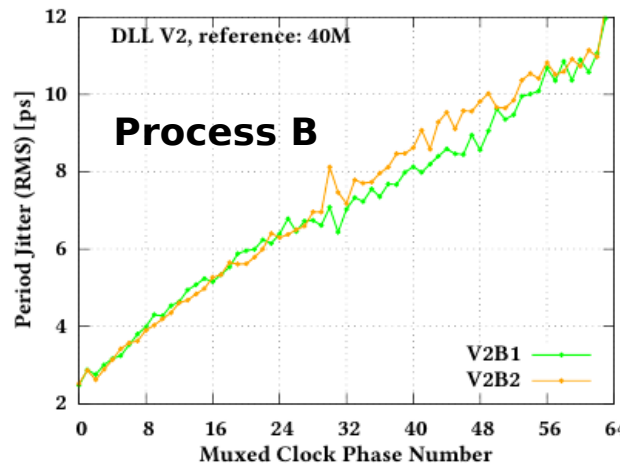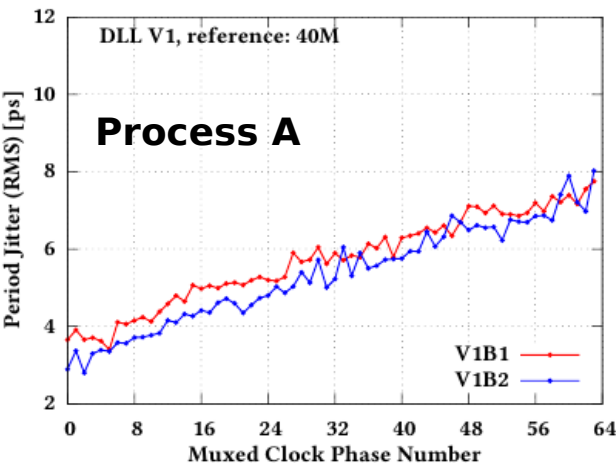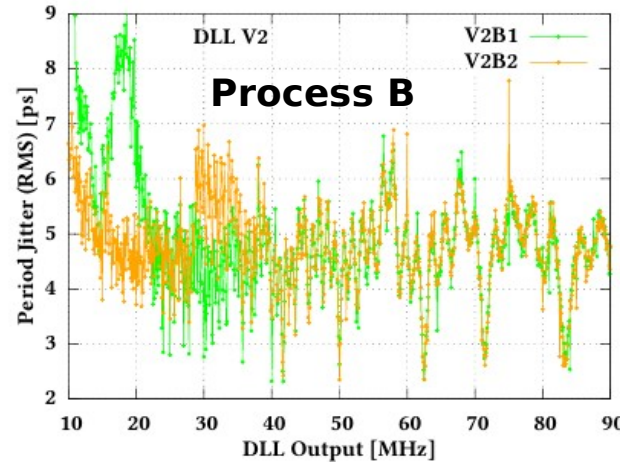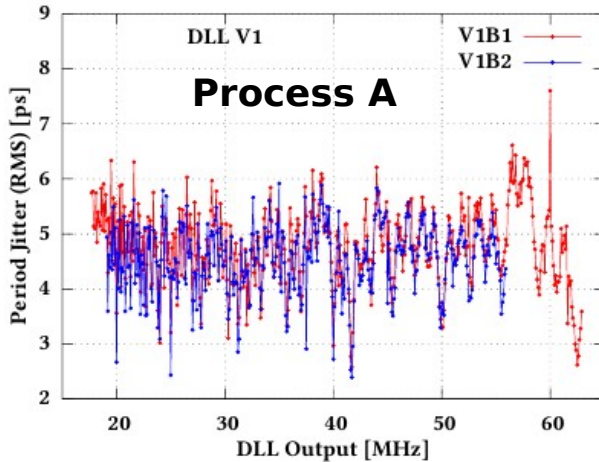

Jitter vs phase

Process A:

Period jitter: 3.8 - 7.8 ps

Process B:

Period jitter: 2.5 - 12.1 ps

Very low jitter, grows with selected clock phase

Summary

	Parameter	Process A	Process B
PLL	Frequency	30 - 450 MHz	40 - 400 MHz
	Dividers	2, 4, 6, and 8	2, 4, 6, and 8
	Power consumption	0.8 mW @ 160 MHz	0.95mW @ 160MHz
	Jitter (RMS)	<10 ps @ 150 - 220 MHz	<10ps @ 100 - 350MHz
	Clock phases	16	16 (fully uniform)
	Area	450 × 260 μm^2	300 × 210 μm^2
DLL	Phase delay	355 - 445 ps	350 - 448 ps
	Clock phases	64	64
	Power consumption	0.7 mW @ 40 MHz	0.7 mW @ 40 MHz
	Jitter vs phase	3.8 - 7.8 ps @ 40 MHz	2.5 - 12.1 ps @ 40 MHz
	Jitter Ph0 (RMS)	<7 ps @ 18 - 62 MHz	<7 ps @ 18 - 90 MHz
	Area	680 x 210 μm^2	430 x 190 μm^2

Ultra-low power, small area, PLL and DLL for SALT and other (general purpose) applications designed, fabricated, and successfully tested



Thank You for your attention