

134 SMD

LIST OF USED MODULES AND SINGLE COMPONENTS IN CONTROL SUBRACKS

CONTROL UNITS POWER SUPPLY – CPUS-01

| COMPONENT NAME | TYPE | FUNCTION |
|----------------------------|--------------------|-----------------------------------|
| 1. AC/DC 30W power module | TRACO, TML 30212 | Sensors & control part powering |
| 2. AC/DC 30W power module | TRACO, TML 30105 | Sensors & control part powering |
| 3. LED diode | φ 3mm, solder type | Status indication |
| 4. Metal rezistor 2W | Metal | Basic load for 5VDC power voltage |
| 5. Capacitors | Tantal | Power voltage bypass |
| 6. Fuse | Glass, 5x20mm | Input power line protection |
| 7. Bus connector – HARTING | DIN 41612 | Backplane interconnection |

STEPPER MOTOR POWER SUPPLY – SMPS-01

| COMPONENT NAME | TYPE | FUNCTION |
|-----------------------------|-----------------------|----------------------------|
| 8. AC/DC 320W power module | SUNPOWER, SPS-320P-48 | Motor power stage powering |
| 9. LED diode | φ 3mm, solder type | Status indication |
| 10. Metal rezistor 0,6W | Metal | LED powering |
| 11. Bus connector – HARTING | DIN 41612 | Backplane interconnection |

STEPPER MOTOR POWER STAGE – ZMX 93-70

| COMPONENT NAME | TYPE | FUNCTION |
|-------------------------------|-------------------------|----------------|
| 12. Stepper motor power stage | PHYTRON, ZMX 93-70 MINI | Motor powering |

STEPPER MOTOR MOTOR CONTROLLER BOARD – SMCB-01

| COMPONENT NAME | TYPE | FUNCTION |
|----------------------------------|-------------------------------|--|
| 13. DC/DC 2W power module | TRACO, TMA 1212S | Emergency stop line powering |
| 14. DC stabilizator | LP 2950-3,3V | DC power for control circuits |
| 15. LED diode | φ 3mm, solder type | Status indication |
| 16. SMD rezistor 0,125W | YAEGO, 0805 | Basic circuits functions |
| 17. Metal rezistor 1W | Metal | Auxiliary function (not used) |
| 18. Capacitors | Tantal | Power voltage bypass |
| 19. Bus connector – HARTING | DIN 41612 | Backplane interconnection |
| SEMICONDUCTORS | | |
| 20. Mixed signal procesor | Silabs, C8051F020 | Main control function |
| 21. Logic IC, Schmit-trigger | 7S14 | u-processor reset |
| 22. Resolver convertor | DDC, RD-19230FG | Absolut position of driver |
| 23. Sinus generator | AD, AD2S99A | Resolver reference signal |
| 24. Digital potentiometer | Analog Devices, AD 7376 A10 | Amplitude control of sinus generator |
| 25. Power aplifier | ST, L165 | Resolver powering |
| 26. Operational amplifier | Texas instrument, TL 082C | Analogue measuring |
| 27. Operational amplifier | MAXIM, MAX 4080 TAU A | Analogue measuring |
| 28. Temperature sensor | National Semiconductors, LM35 | Temperature measuring |
| 29. RS-232 convertor | MAXIM, MAX 232 | External communication |
| 30. RS-422 convertor | Linear Technology, LTC 491CS | Internal control bus connection |
| 31. Optocoupler | CPC1008N | Emergency stop line rele control |
| 32. Optocoupler | PC 357 | Discrete input/output signals processing |
| 33. Zener overvoltage protection | MOTOROLA, P6SMB18 | Resolver lines protection |
| 34. Zener overvoltage protection | MOTOROLA, P6SMB6,8 | Communication lines protection |
| 35. Transistor | BSS 138, BSS 83P | Logic circuits |

WORLDFIP/RS-422CONVERTOR – WFRSC-01

| COMPONENT NAME | TYPE | FUNCTION |
|----------------------------------|-------------------------------|--|
| 36. LED diode | φ 3mm, solder type | Status indication |
| 37. SMD rezistor 0,125W | YAEGO, 0805 | Basic circuits functions |
| 38. Capacitors | Tantal | Power voltage bypass |
| 39. Bus connector – HARTING | DIN 41612 | Backplane interconnection |
| SEMICONDUCTORS | | |
| 40. WORLDFIP module | CC130A | WorldFip communication |
| 41. DC stabilizator | LP 2950-3,3V | DC power for control circuit |
| 42. Mixed signal procesor | Silabs, C8051F021 | Main control function |
| 43. Logic IC, Schmit-trigger | 7S14 | u-processor reset |
| 44. Temperature sensor | National Semiconductors, LM35 | Temperature measuring |
| 45. RS-232 convertor | MAXIM, MAX 232 | External communication |
| 46. RS-422 convertor | Linear Technology, LTC 491CS | Internal control bus connection |
| 47. Optocoupler | CPC1008N | Emergency stop line rele control |
| 48. Optocoupler | PC 357 | Discrete input/output signals processing |
| 49. Zener overvoltage protection | MOTOROLA, P6SMB6,8 | Communication lines protection |
| 50. Transistor | BSS 138 | Logic circuits |